

# **Analogue and digital electronics for engineers**

*AN INTRODUCTION*

**H. AHMED**

*Reader in Microelectronics, Cavendish Laboratory,  
University of Cambridge*

**P. J. SPREADBURY**

*Lecturer in Engineering, University of Cambridge*

*THE SECOND EDITION OF 'ELECTRONICS FOR ENGINEERS'*



**CAMBRIDGE**  
UNIVERSITY PRESS

PUBLISHED BY THE PRESS SYNDICATE OF THE UNIVERSITY OF CAMBRIDGE  
The Pitt Building, Trumpington Street, Cambridge CB2 1RP, United Kingdom

CAMBRIDGE UNIVERSITY PRESS  
The Edinburgh Building, Cambridge CB2 2RU, United Kingdom  
40 West 20th Street, New York, NY 10011-4211, USA  
10 Stamford Road, Oakleigh, Melbourne 3166, Australia

© Cambridge University Press 1973, 1984

This book is in copyright. Subject to statutory exception  
and to the provisions of relevant collective licensing agreements,  
no reproduction of any part may take place without  
the written permission of Cambridge University Press.

First published 1973  
Reprinted 1974 1977 1978 1981 1982  
Second edition 1984  
Reprinted 1987 1989 1992 1997

Typeset in Times

*A catalogue record for this book is available from the British Library*

*Library of Congress Cataloguing in Publication data*

Ahmed, H.

Analogue and digital electronics for  
engineers.—2nd ed.—(Electronics texts  
for engineers and scientists)

I. Electronic circuits

I. Title II. Spreadbury, P. J.

III. Electronics for engineers IV. Series  
621.3815'3 TK7867

ISBN 0 521 26463 4 hardback  
ISBN 0 521 31910 2 paperback

Transferred to digital printing 2002

# Contents

<i>Preface to the second edition</i>	<i>page xi</i>
<i>Preface to the first edition</i>	<i>xiii</i>
<b>1 Principles of amplifiers</b>	<b>1</b>
1.1 Introduction	1
1.2 Coupling between voltage amplifiers	3
1.3 Worked example	5
1.4 Logarithmic expression for gain: the decibel	6
1.5 Coupling between current amplifiers	8
1.6 Loading of a source for maximum power output	9
1.7 Frequency characteristics of coupling circuits and amplifiers	11
1.8 Coupling circuits at low frequency	13
1.9 Coupling circuits at high frequency	18
1.10 Pulses and digital signals	22
1.10.1 Terminology	22
1.10.2 Rise-time, decay-time and time constants	24
1.10.3 Resistance–capacitance coupling network	25
1.10.4 Square wave applied to an <i>RC</i> network	27
1.10.5 Capacitance–resistance circuit	28
1.10.6 Square wave applied to the capacitance–resistance network	29
1.11 Worked example	31
1.12 Summary	32
1.13 Problems	33
<b>2 The p–n junction and the field-effect transistor</b>	<b>36</b>
2.1 Introduction	36
2.2 The p–n junction	36
2.3 Forward and reverse biased p–n junctions	39
2.4 Depletion layer width and junction capacitance	40

## **Contents**

2.5	The field-effect transistor (unipolar transistor)	<i>page</i> 43
2.6	Principle of operation	43
2.7	Characteristics of the field-effect transistor	47
2.8	The field-effect transistor amplifier	48
2.9	Amplification of signals	51
2.10	Small signal parameters of the f.e.t.	52
2.11	The common-source amplifier (AC analysis)	54
2.12	A simple bias circuit for the f.e.t.	55
2.13	Input and output impedance	56
2.14	Coupling of f.e.t. amplifiers and amplification of low frequency signals	57
2.15	Amplification of high frequency signals	59
†2.16	The source follower	60
2.17	The metal oxide semiconductor transistor (MOST)	62
	2.17.1 Complementary MOS (CMOS) transistors	66
2.18	Worked example	68
2.19	Summary	70
2.20	Problems	70
<b>Quiz 1 (chapters 1 and 2)</b>		<b>74</b>
<b>3 The bipolar transistor</b>		<b>76</b>
3.1	Introduction	76
3.2	Principle of operation	76
3.3	Current relationships	79
3.4	Typical common-emitter characteristics	80
3.5	Data for a typical npn transistor	83
3.6	Ratings and selection of operating point	83
†3.7	Operating point stability	85
3.8	Graphical estimates of circuit gain	88
3.9	Small-signal equivalent circuits for the bipolar transistor	91
	†3.9.1 T-network	92
	3.9.2 Hybrid-parameter network	93
	†3.9.3 Hybrid- $\pi$ network	95
3.10	Calculation of amplifier performance	96
3.11	Frequency response	99
†3.12	Emitter follower performance	100
†3.13	Coupling between amplifier stages	104
3.14	Manufacture of planar transistors	106

† Sections so marked may be omitted on first reading.

## **Contents**

3.15	Worked example	<i>page</i> 106
3.16	Relative merits of bipolar and field-effect transistors	110
3.17	Summary	110
3.18	Problems	111
<b>4</b>	<b>Operational amplifiers and linear integrated circuits</b>	<b>114</b>
4.1	Introduction	114
4.2	A review of the properties of real and ideal amplifiers	114
4.3	The terminology of integrated circuit differential amplifiers	115
4.4	The inverting operational amplifier	117
4.4.1	Gain	117
4.4.2	Input and output impedances of the inverting amplifier	121
4.5	The non-inverting operational amplifier	123
4.5.1	Gain and output impedance	123
4.5.2	Input impedance	125
4.6	The differential operational amplifier	126
4.7	Some applications of operational amplifiers	128
4.7.1	The voltage follower	128
4.7.2	The adder amplifier	129
4.7.3	Integrating and differentiating amplifiers	131
4.7.4	Simulation of an inductance	132
4.7.5	A band-pass filter	134
4.7.6	Current-to-voltage converter	136
4.8	Frequency response of operational amplifiers	137
4.9	The differential amplifier	140
4.9.1	Gain from a symmetrical differential amplifier	142
4.9.2	The common-mode rejection ratio (CMRR) of the differential amplifier	143
4.9.3	Bipolar transistor differential amplifier	145
4.10	Some practical considerations	146
4.10.1	Input bias currents and input offset current	146
4.10.2	Offset voltage	148
4.10.3	Common-mode rejection ratio	149
4.10.4	Slewing rate and full power response	150
4.11	Linear integrated circuits	152
4.12	Worked examples	154
4.13	Summary	158
4.14	Problems	158
	<b>Quiz 2 (chapters 3 and 4)</b>	<b>162</b>

## Contents

<b>5</b>	<b>Negative feedback</b>	<i>page</i> 164
5.1	Introduction	164
5.2	Definitions of feedback	164
5.3	Realisation of $A$ and $B$	166
5.3.1	Voltage feedback applied to a voltage amplifier	167
5.3.2	Voltage feedback applied to a differential amplifier	168
5.3.3	Current feedback applied to a current amplifier	169
5.4	Stabilisation of gain	171
5.5	Increase in frequency response	172
5.6	Reduction of the effect of internal disturbances in the amplifier	173
5.7	Effect on the input and output impedances of the amplifier	174
5.7.1	Voltage amplifier with voltage feedback	175
5.7.2	Current amplifier with current feedback	176
†5.7.3	Trans-conductance or trans-resistance amplifiers	177
†5.8	Factors for and against feedback over several stages	180
5.9	Instability	181
†5.10	Interpretation of the Nyquist diagram	183
5.11	Worked example	185
5.12	Summary	186
5.13	Problems	187
<b>6</b>	<b>Positive feedback and oscillators</b>	190
6.1	Introduction	190
6.2	Theoretical requirements for oscillation	190
6.3	Sinusoidal oscillators	192
6.4	Realisation of phase-shifting networks	193
6.4.1	Ladder networks	194
6.4.2	Wien networks	195
†6.4.3	Tuned networks	196
†6.5	Frequency stability	199
6.6	Stabilisation of oscillator output amplitude	200
6.6.1	Voltage sensitive amplifier using a thermistor	203
†6.6.2	Voltage sensitive amplifier using a bulb or a field-effect transistor	204
†6.7	Oscillator using operational amplifiers as integrators	206
6.8	Worked example	207
6.9	Summary	209
6.10	Problems	209

## Contents

<b>Quiz 3 (chapters 5 and 6)</b>	page 212
<b>7 Digital fundamentals</b>	214
7.1 Introduction	214
7.2 Transistor as a switch – the simple inverter	214
7.3 Simple gates – NAND, AND, NOR, OR, Exclusive-OR and NOR	216
7.4 Number systems – binary, hexadecimal and BCD	218
7.5. Definitions of combinational and sequential logic	220
7.6 Combinational logic identities – Boolean algebra	220
7.7 Karnaugh maps for logic simplification	224
†7.8 Hazards and their elimination (using the Karnaugh map)	227
7.9 Memory – two inverting gates with feedback	228
†7.10 Realisation of gates with MOS or bipolar devices – 3-state or open collector devices	229
7.11 Comparison of logic families	232
7.12 Worked examples	234
7.12.1 Analysis of address decoder	234
7.12.2 Synthesis of month-length detector	234
7.12 Summary	235
7.14 Problems	236
<b>8 Digital circuits and applications</b>	239
8.1 Introduction	239
8.2 Bistable circuit ( $S$ – $R$ type, latch, $J$ – $K$ , $M$ – $S$ and clocked types)	239
8.3 Counters – ripple and synchronous types	243
8.4 Registers, accumulators and arithmetic ICs	245
†8.5 State diagrams and sequential design	246
†8.6 Voltage level detector, Schmitt trigger IC	251
8.7 Digital to analogue converters (DACs)	254
8.8 Analogue to digital converters (ADCs)	257
8.9 Memories; RAM, ROM, EPROM	259
8.10 Applications	261
†8.10.1 Use of LSI circuits as combinational logic elements	261
†8.10.2 Multiplexers and transmission gates	263
8.10.3 Random and pseudo-random sequences	264
8.11 Capabilities of microprocessors	265
8.12 Summary	268
8.13 Problems	268
<b>Appendix A</b> A list of useful textbooks	271
<b>Appendix B</b> Device data and characteristics	272
<b>Answers to problems</b>	280
<b>Index</b>	284

---

## Principles of amplifiers

### 1.1 Introduction

The amplifier is a basic building block of electronic systems. The contents of the block may change over the years but we will always need to know how one amplifier will load another when they are connected in series (cascade). Also we will need to know how an amplifier will be affected by the capacitance of the wires bringing its input to it and taking its output from it.

Consider the amplifier shown in fig. 1.1. We will assume that the input  $X_i$  is related to the output  $X_o$  by a constant. The stage is said to have a gain,  $A$ , given by:

$$A = \frac{\text{amplifier output}}{\text{amplifier input}} = \frac{X_o}{X_i}.$$

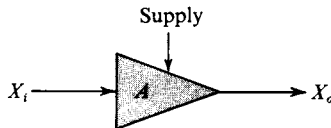


Fig. 1.1. Amplifier symbol.

Note that, in fig. 1.2, as the input  $X_i$  is increased, there will come a time when  $X_o$  cannot rise any more due to limitations of the supply. Thus every amplifier will become non-linear for very large output demands, as shown in fig. 1.2. Also all amplifiers will be non-linear to some extent, even for small signals: i.e. the ratios  $X_{o1}/X_{i1}$  and  $X_{o2}/X_{i2}$  may be different. However there will be a restricted working range of the amplifier where the ratios are nearly constant, say within a few per cent of each other. In this chapter, we consider amplifiers working in their linear range and we take  $A$  to be a constant.

Having said that the gain of an amplifier is  $A = X_o/X_i$ , we can write  $X_o = AX_i$ . If this is so, what is the output in the arrangement in fig. 1.3? Or what is the output of the mechanical system with levers shown in



**Principles of amplifiers**

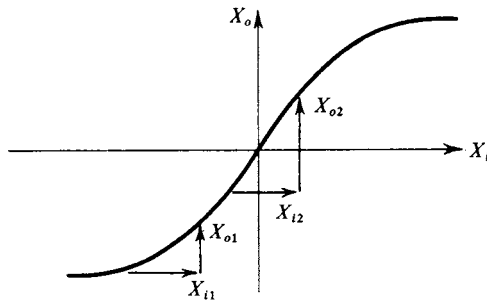


Fig. 1.2. Linearity of gain.

fig. 1.4? Is the output always  $16x$  for an input  $x$ ? It is clear that the output will be  $16x$  sometimes; but if the output point is not entirely free to move, i.e. the output could be compressing a spring, then the beams may bend and some deflection less than 16 times the input will result. The lever example shows a realisation of  $A = -4$  on no load.

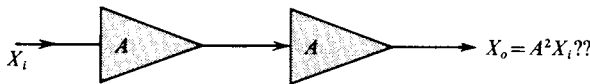


Fig. 1.3. Two amplifiers in cascade.

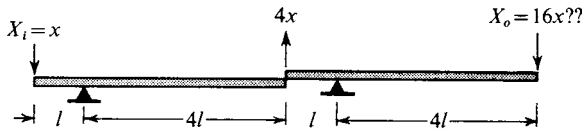


Fig. 1.4. Lever system.

Returning to the amplifiers, let us assume that they are voltage amplifiers each of gain  $= -4$ . That is, for a unit voltage *rise* at the input, there will be a 4 unit voltage *fall* at the output. It is again clear that the output could be  $16v$  for an input  $v$ , but it may be less. This will be caused by the second amplifier drawing current by having a path of impedance  $Z_i$  at its input terminal. If the first amplifier has an impedance  $Z_o$  in its output path then a voltage drop will occur across  $Z_o$  and something less than  $-4v$  will be the input of the second amplifier of fig. 1.5.

Thus we are interested in the 'coupling' between stages. Every amplifier has these input and output impedances. Can we say what are desirable values for best voltage, or current or power coupling? These impedances may be reactive; for instance,  $Z_i$  may be  $10^5 \Omega$  in parallel with a capacitor

## Introduction

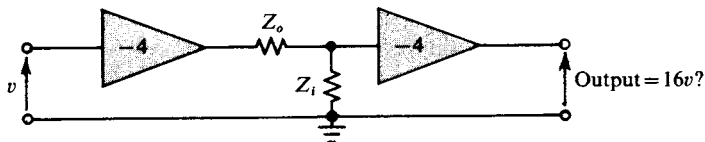


Fig. 1.5. Amplifiers showing coupling circuit.

of  $10^{-10}$  F. We wish to know what such a value for  $Z_i$  will do to the coupling between amplifiers or between an amplifier and some signal source.

### 1.2 Coupling between voltage amplifiers

The circuit of fig. 1.6 contains the following parts:

(a) is a source of voltage  $v_1$  and internal impedance  $Z_1$ . We know that the source may be a circuit including many devices, but Thévenin's theorem says that this can be reduced to a single voltage generator and a series impedance. We could have reduced the source to the Norton form of a single current generator and a parallel impedance; identical answers would be obtained, but less easily.

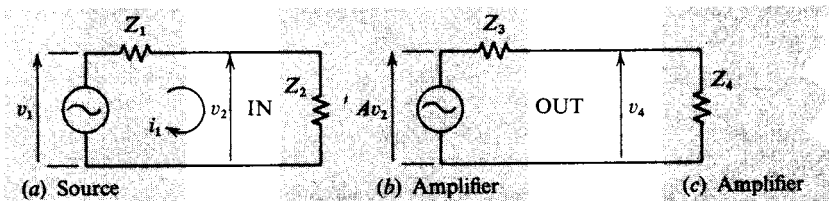


Fig. 1.6. Voltage coupling.

(b) is an amplifier whose input draws some current. One side of the input may be ground, or may be a power supply voltage rail which would be in common with one side of the amplifier output but, in this general case, this is not assumed. The two terminals are shown at which the input voltage  $v_2$  may be developed and the impedance  $Z_2$  across these terminals is the input impedance of the amplifier.

Again the amplifier may contain many components but the Thévenin representation is used whereby the output circuit is reduced to one voltage generator  $Av_2$  and one series impedance  $Z_3$ . If no load current flows and so no voltage drop occurs in  $Z_3$ ,  $Av_2$  will be the output for an input  $v_2$ . So  $A$  is the no-load voltage gain of the amplifier and  $Z_3$  is the amplifier's output impedance.

## Principles of amplifiers

(c) is either a load of impedance  $Z_4$ , or is a further amplifier which may draw current from the amplifier (b) and which we represent as having an input impedance  $Z_4$ . The voltage developed across this load is  $v_4$ .

Considering the input circuit of the first amplifier, we wish to know what voltage  $v_2$  is developed there compared to  $v_1$  which is the voltage that would be available from the source if no current was drawn from it.

Kirchhoff's laws allow us to solve circuit problems in two ways. The first way is to label the voltages appearing between different points of a circuit and some reference point. We can then write the currents in each path of the circuit to be equal to the voltage difference between the ends of the path divided by the impedance of the path. Lastly we write down that the currents into any point of a circuit must equal the currents out of that point. Thus we end with as many equations as points and we can solve these equations. The second way is to mark in the unknown circulating currents in each loop and write down that the voltage drops round a loop must equal the source voltages.

In our circuit the voltages are already labelled, and at the upper input terminal of the amplifier, the current out of the source must equal that flowing into the amplifier (we have shown no other paths) thus:

$$\frac{v_1 - v_2}{Z_1} = \frac{v_2}{Z_2}$$

or

$$v_1 Z_2 = v_2 Z_1 + v_2 Z_2,$$

so

$$v_2 = v_1 \left( \frac{Z_2}{Z_1 + Z_2} \right). \quad (1.1)$$

Note that this could have been obtained by putting in  $i_1$  as an unknown circulating current and from

$$v_1 = i_1 Z_1 + i_1 Z_2 \quad \text{and} \quad v_2 = i_1 Z_2$$

the same relation for  $v_2$  and  $v_1$  results.

Equation (1.1) is sometimes called the potential divider expression for the circuit of fig. 1.7.

The output voltage is a fraction  $Z_2/(Z_1 + Z_2)$  of the input voltage; but note that this is only true when no other current is drawn from the point joining  $Z_1$  and  $Z_2$ . This equation is easy to remember and can be used

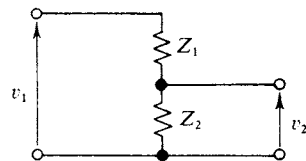


Fig. 1.7. Potentiometer.

### Coupling between voltage amplifiers

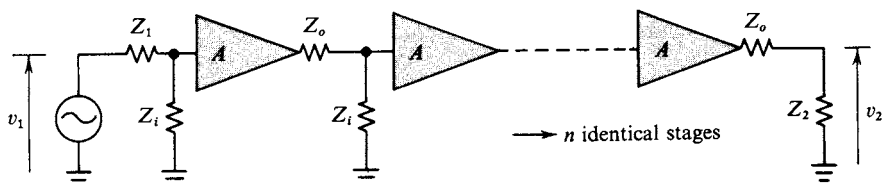


Fig. 1.8. Multistage voltage amplifier.

if all the circuits across which  $v_2$  is developed are combined to give one effective impedance  $Z_2$  which is used in the equation.

Under some circumstances, we may want perfect voltage coupling or  $v_2 \rightarrow v_1$ . From (1.1) this is achieved if

$$\frac{Z_2}{Z_1 + Z_2} \rightarrow 1 \quad \text{or} \quad Z_1 \ll Z_2.$$

Note that we do not want  $Z_1$  to be 0 but merely very much smaller than  $Z_2$ , the input resistance of the amplifier. A factor making  $Z_1$  from 20 to 100 times smaller than  $Z_2$  is suitable for most engineering purposes although for high quality instrumentation and computing, a factor making  $Z_1$  from  $10^3$  to  $10^6$  smaller may be appropriate.

Referring again to the circuit, fig. 1.6, we can write an equation similar to (1.1) for the second part of the circuit:

$$v_4 = A v_2 \left( \frac{Z_4}{Z_3 + Z_4} \right) = A \left( \frac{Z_2}{Z_1 + Z_2} \right) \left( \frac{Z_4}{Z_3 + Z_4} \right) v_1;$$

or for the multistage amplifier with  $n$  identical stages shown in fig. 1.8, we may write generally:

$$v_2 = A^n \left( \frac{Z_i}{Z_i + Z_1} \right) \left( \frac{Z_i}{Z_i + Z_o} \right)^{n-1} \left( \frac{Z_2}{Z_o + Z_2} \right) v_1, \quad (1.2)$$

where  $Z_i$  is the input impedance and  $Z_o$  is the output impedance of each amplifier.

Thus as a general method of working out the overall relation, we have separated the 'attenuation' (which is a gain of less than unity) of each coupling section between amplifier blocks from the gain of the amplifier blocks.

### 1.3 Worked example

A sine wave generator whose internal source is represented by a phasor of voltage  $10 \angle -10^\circ$  at a certain instant has an output impedance  $600 - j100 \Omega$ . It is connected to a circuit of impedance  $4000 - j700 \Omega$ ; what input will be developed there?

## Principles of amplifiers

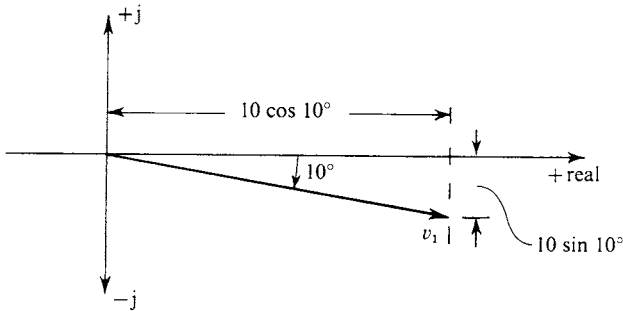


Fig. 1.9. Phasor diagram of  $v_1$ .

These data refer to a circuit similar to the left-hand part of fig. 1.6 where:

$$v_1 = 10 \angle -10^\circ \text{ or } 10 \cos 10^\circ - j10 \sin 10^\circ \text{ volts (see fig. 1.9),}$$

$$Z_1 = 600 - j100 \Omega,$$

$$Z_2 = 4000 - j700 \Omega.$$

Equation (1.1) gives:

$$\begin{aligned} v_2 &= \frac{v_1 Z_2}{Z_1 + Z_2} = 10 \angle -10^\circ \frac{4000 - j700}{4600 - j800} \\ &= 10 \angle -10^\circ \frac{4061 \angle -9^\circ 56'}{4669 \angle -9^\circ 51'} \\ &= \frac{10 \times 4061}{4669} \angle \{-10^\circ + (-9^\circ 56') - (-9^\circ 51')\} \\ &= 8.70 \angle -10^\circ 5' \text{ volts.} \end{aligned}$$

This is 87 per cent of the unloaded output of the generator and lags it by 5'.

This arithmetic, which consists of taking the *product* and *quotient* of complex quantities, is more easily handled in polar form. Each step can be checked roughly and numerical mistakes are less likely to creep in, i.e. one would expect an impedance to 4000  $\Omega$  resistance and 700  $\Omega$  capacitive reactance to have a magnitude of a little over 4000  $\Omega$ , and so on.

### 1.4 Logarithmic expression for gain: the decibel (dB)

The logarithmic expressions for gain have several uses. To work out the gain of a multistage amplifier from an expression such as (1.2), one just *adds* the logarithmic gain for each coupling and for each amplifier to get the overall gain of many stages in cascade.

In fig. 1.8, we considered how the output voltage,  $v_2$ , was related to the

### Logarithmic gain : the decibel

input voltage  $v_1$  and an expression of the form,  $v_2 = (\text{voltage gain})v_1$  was obtained for an amplifier. If we know what resistances the input and output voltages appear across, say  $R_1$  and  $R_2$  respectively, then we can write that the input power,  $p_1 = v_1^2/R_1$ . Similarly the output power,  $p_2 = v_2^2/R_2$ , where  $v_1$  and  $v_2$  are the RMS voltages. Then a figure for power gain could be obtained from

$$p_2 = (\text{power gain})p_1.$$

An alternative to the dimensionless figure for power gain is that expressed in decibels (dB) and it is defined by:

$$\text{Power gain (dB)} = 10 \log_{10} \frac{p_2}{p_1}. \quad (1.3)$$

Thus an amplifier giving 4 watts output for 4mW input will have a power gain of 30 dB. If we write the powers in terms of voltages we get

$$\begin{aligned} \text{Power gain (dB)} &= 10 \log_{10} \frac{v_2^2/R_2}{v_1^2/R_1} \\ &= 20 \log_{10} \frac{v_2}{v_1} + 10 \log_{10} \frac{R_1}{R_2}. \end{aligned} \quad (1.4)$$

In any circuits where  $R_2 = R_1$ , then and *only* then:

$$\begin{aligned} \text{Power gain (dB)} &= 20 \log_{10} \frac{v_2}{v_1} \\ &= 20 \log_{10} (\text{voltage gain}). \end{aligned} \quad (1.5)$$

Many communication circuits are designed with standard source and load resistors of 600  $\Omega$  and transmission lines of 50 and 75  $\Omega$ . In these systems, (1.5) expressing the *voltage gain* in dB is often used.

The decibel unit of power gain is very useful for two reasons:

(a) The response curves of many circuits have simple forms when the gain in decibels is plotted against the frequency on a logarithmic scale.

(b) When power (or voltage or current) amplifiers are followed by further circuits with gain (+dB) or attenuation (-dB), then the overall gain is obtained algebraically by *summing* the gains and attenuations of all parts in a path between the input and output.

Thus if our amplifier of input 4 mW and output 4 W is followed by a passive circuit of power gain 0.5 (or attenuation of 2) and this is followed by a further amplifier of power gain 400, then in terms of decibels:

$$\text{Power gain of } 0.5 = 10 \log_{10} 0.5 = -10 \log_{10} 2 = -3 \text{ dB.}$$

$$\text{Power gain of } 400 = 10 \log_{10} 400 = 10 \times 2.6 = +26 \text{ dB,}$$

and therefore the overall gain =  $30 - 3 + 26 = +53$  dB (or 200000 times).

### Principles of amplifiers

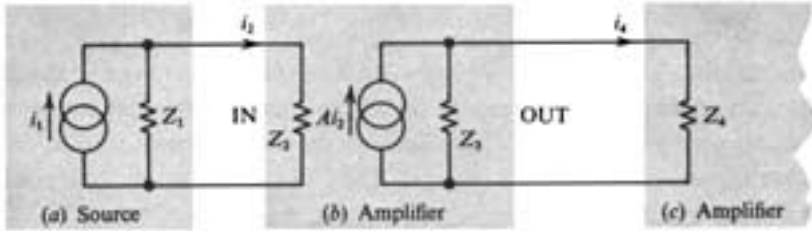


Fig. 1.10. Current coupling.

Readers will see some amplifier data sheets with the gain quoted in decibels *without* the output load being specified. These data should be treated with caution.

### 1.5 Coupling between current amplifiers

The circuit of fig. 1.10 contains the following parts.

(a) is a source of current  $i_1$  and internal impedance  $Z_1$ . Norton's theorem allows the source, whatever its internal complexity, to be reduced to a single current generator and parallel impedance  $Z_1$ . The conduction path  $Z_1$  means that the source can waste some of its current internally which is the dual of a voltage source dropping some of its voltage internally.

(b) is an amplifier whose input impedance is  $Z_2$ : thus to drive a current  $i_2$  into the input terminals, some voltage must exist there. The amplifier is reduced to an equivalent circuit of a single generator  $Ai_2$  and a parallel impedance  $Z_3$  at the output terminals. Here  $A$  is the current gain of the amplifier when it is loaded by a short circuit and  $Z_3$  is its output impedance.

In the ideal current amplifier,  $Z_2 = 0$ . It may appear unreal to terminate any source by a short circuit, but certain devices are good current amplifiers and we shall show that, for best current coupling, they should be followed by low impedance stages.

(c) is a further amplifier which has an input impedance  $Z_4$  or it is a load.

Considering the input circuit of the first amplifier, we wish to know what current,  $i_2$ , flows into the first amplifier compared with  $i_1$ , which is apparently available from the source. Kirchhoff's current law allows us to write that the current going down  $Z_1$  is  $i_1 - i_2$ , whence we can write expressions for the voltage at the amplifier input as

$$Z_1(i_1 - i_2) \quad \text{or} \quad i_2 Z_2.$$

### Coupling between current amplifiers

Since these are identical,

$$Z_1(i_1 - i_2) = i_2 Z_2,$$

so 
$$i_2 = i_1 \left( \frac{Z_1}{Z_1 + Z_2} \right). \quad (1.6)$$

Note that this is the dual of the voltage coupling expression. Now it is the load impedance  $Z_2$  which should be much smaller than the source impedance to give good current coupling, i.e. when,

$$Z_2 \ll Z_1, \quad (Z_1 + Z_2) \approx Z_1,$$

so 
$$i_2 \approx i_1.$$

Consider next the current  $i_4$  coupled from the amplifier output to the next stage input in fig. 1.10; here

$$i_4 = A i_2 \left( \frac{Z_3}{Z_3 + Z_4} \right) = A \left( \frac{Z_1}{Z_1 + Z_2} \right) \left( \frac{Z_3}{Z_3 + Z_4} \right) i_1.$$

So the overall gain,  $i_4/i_1$ , is the product of the gain of an amplifier and the efficiency of its input and output coupling; namely  $Z_1/(Z_1 + Z_2)$  and  $Z_3/(Z_3 + Z_4)$  respectively. If these figures are known or calculated in decibels, the terms are added rather than multiplied.

It is interesting that bipolar transistors whose input resistances are usually much smaller than their output resistances give good current coupling between each stage when they are connected in cascade. (Typical figures for a small transistor are an input resistance of 1 k $\Omega$  and an output resistance of 30 k $\Omega$  or, for a power transistor, 10  $\Omega$  and 200  $\Omega$  respectively.)

## 1.6 Loading of a source for maximum power output

The circuit of fig. 1.11 shows:

(a) a source whose voltage on no load is  $v_1$  and whose internal impedance  $Z_1$ , has resistive and reactive components,  $R_1$  and  $X_1$ .

(b) a load whose impedance,  $Z_2$ , we wish to determine to get maximum power output from the source. The load is considered generally to be made up of a resistive part  $R_2$  in series with a reactive part of impedance  $X_2$ .

We can write the value of the current into the load,  $i_2$ , as:

$$i_2 = \frac{\text{e.m.f.}}{\text{impedance}} = \frac{v_1}{Z_1 + Z_2} = \frac{v_1}{R_1 + R_2 + j(X_1 + X_2)}. \quad (1.7)$$

The expressions for power in any load are  $|v_2| |i_2| \cos \phi$  or  $|i_2|^2 R_2$ . Both



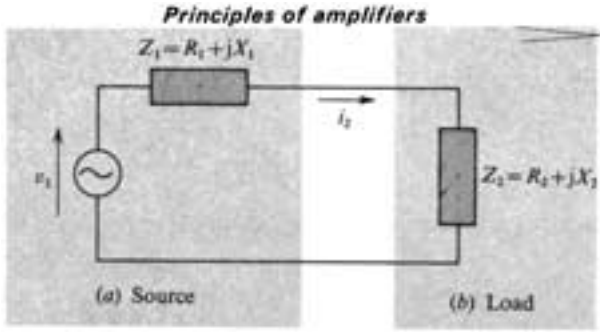


Fig. 1.11. Power coupling.

will give the same result. Here we do not know the load voltage,  $v_2$ , but we do know the load current  $i_2$  and the resistive part of the load  $R_2$  through which the current flows. Hence the power into the load,  $p_2$  is given by:

$$p_2 = |i_2|^2 R_2 = \left| \frac{v_1}{R_1 + R_2 + j(X_1 + X_2)} \right|^2 R_2$$

which cannot exceed 
$$\frac{v_1^2 R_2}{(R_1 + R_2)^2} \quad (1.8)$$

This is because the complex denominator can be made a minimum if  $X_1 = -X_2$  and this will make the power a maximum. Thus the first condition for getting maximum power output is that the load reactance,  $X_2$ , should be the conjugate of the source internal reactance,  $X_1$ ; i.e. if one is inductive the other should be capacitive and vice versa.

Differentiating the expression for power,  $p_2$ , with respect to  $R_2$  gives:

$$\frac{dp_2}{dR_2} = \frac{(R_1 + R_2)^2 v_1^2 - 2v_1^2 R_2 (R_1 + R_2)}{(R_1 + R_2)^4}$$

= 0 for a maximum or minimum. This is given by setting the numerator to zero,

$$0 = (R_1 + R_2) - 2R_2,$$

hence 
$$R_1 = R_2. \quad (1.9)$$

This is a well known result that the resistive part of the load impedance must be equal to the resistive part of the source impedance for maximum power output. Substituting the value  $R_2 = R_1$  into the expression for power  $p_2$ , (1.8), gives:

$$p_2 \text{ (maximum)} = \frac{1}{4} \frac{v_1^2}{R_1}.$$

Note that  $v_1^2/R_1$  is the power that could be dissipated internally in the source if the output terminals were loaded only by a reactance  $X_2$  equal to  $-X_1$ . Thus the maximum power output is a quarter of that that could be dissipated internally in the source.

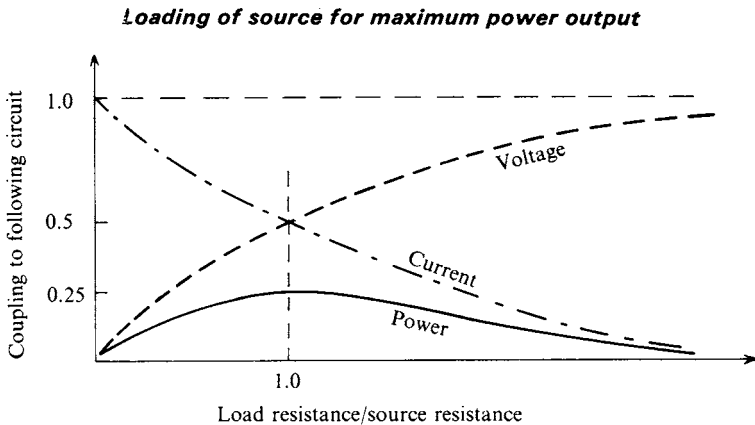


Fig. 1.12. Variation of coupling with the ratio of load to source resistance.

Power matching is used mainly in three situations:

(a) Where the signal levels are very small so any power lost gives a much worse signal to noise ratio: for example, it is used in all aerial to receiver connections in television, radio and radar equipment.

(b) Where the signal at high frequency is connected through lines of appreciable self capacity and self inductance to a load. Then it is possible to get large standing waves due to reflections from the load which can make the source to load power transfer low.

(c) Where signals are very large, say at the output stage of a transmitter, and where the maximum efficiency is desirable on economic grounds.

Fig. 1.12, summarises how the ratio of load to source resistance influences the efficiency of voltage, current and power coupling between circuits.

## 1.7 Frequency characteristics of coupling circuits and amplifiers

So far, the gain and other properties of the amplifier blocks and the coupling between the blocks have not been related in any way to frequency. There will always be some high frequency at which the gain of any amplifier is less than its gain at low frequency. The effects are akin to mechanical inertia; on requiring an output, it takes a finite time for current flowing at an input terminal of a device to pass through it and reach its output – this is called transit time and it is naturally very short if the device is small. Also, it takes time for the voltage to build up in an output circuit after current has started to flow into it, due to its capacitance. Thus we can show some features of an amplifier's response by showing the output of an amplifier for a step input, fig. 1.13.

## Principles of amplifiers

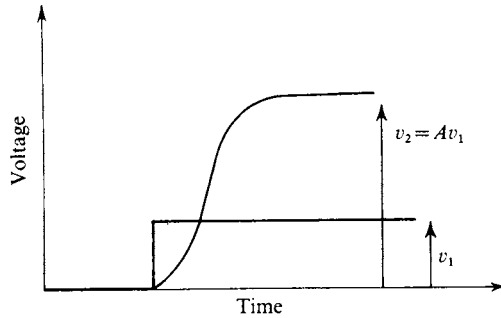


Fig. 1.13. Amplifier output for step input.

To a rough approximation, the output may rise exponentially; the time constant of the amplifier can be obtained from the time taken for the output to get to 63 per cent or  $1 - 1/e$  of the state to which it eventually settles. If this time is  $\tau_2$ , then we have approximated the output as a function of time to  $v_2(t) = Av_1(1 - e^{-t/\tau_2})$ .

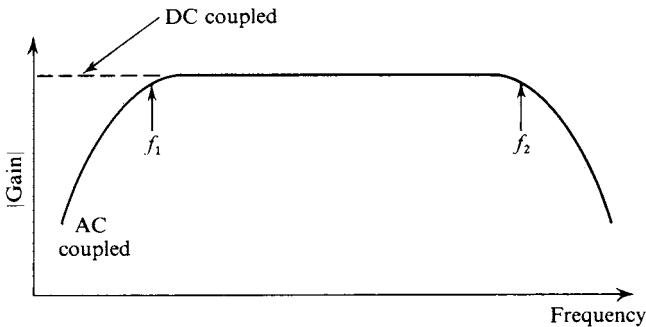


Fig. 1.14. Frequency response of a typical circuit.

An alternative representation to show the gain of an amplifier or of a coupling circuit is to plot the magnitude of its gain against frequency, as in fig. 1.14. The approximate relationship between  $f_2$  when the gain starts dropping and  $\tau_2$  is simple and it will be developed later.

The important features of an amplifier can be seen from a plot of its  $|\text{gain}|$  against frequency. It will amplify signals at frequencies between  $f_1$  and  $f_2$  by very nearly the same amount. Thus a musical note with certain harmonics at the source should be almost faithfully amplified if the fundamental and the main harmonics present are in the range of frequencies between  $f_1$  and  $f_2$ . The waveform of the electrical signal to make a television picture is very complex. It contains components between 25 Hz and 5 MHz and thus 'video' amplifiers need to have a flat response over this band.

### Frequency characteristics of amplifiers

The methods of Fourier series and Fourier transforms allow pulses, ramp waveforms and square waves to be broken up into a spectrum of frequencies. The circuit should have approximately the same gain and approximately the same phase shift over this spectrum for the waveform at the output to closely resemble that at the input.

We wish therefore to know which components in the coupling and amplifier circuits will give rise to the frequencies  $f_1$  and  $f_2$  at which the gain drops from a largely constant figure called the *midband gain*. It is possible to have coupling circuits whose gain stays constant down to zero frequency – such circuits are called direct current coupled or ‘DC coupled’. With many circuits this is not necessary and they can be simplified by being coupled for alternating signals only and so are called ‘AC coupled’. The difference between these two is shown at the left-hand end of the response plot, fig. 1.14.

We want to construct such a plot with the minimum of computational effort. We wish to know which components in our amplifiers and coupling circuits give rise to the drop in gain at the extremes of frequency. Then we can design circuits to handle just the frequency band required for the signals in which we may be interested.

#### 1.8 Coupling circuits at low frequency

The following analysis explores the effect of a simple coupling circuit between a source and load. Exactly the same effect is produced by coupling circuits between stages of amplifiers and by the decoupling circuits needed by amplifiers (decoupling circuits are mentioned in the chapters on amplifier realisation with field-effect and bipolar transistors). In those cases one must first identify the resistors in series with the reactive element and the analysis then reduces to the same as that now given.

The circuit, fig. 1.15, shows:

(a) is a sinusoidal source of voltage of amplitude  $v_1$  and frequency  $\omega$  rad/s =  $2\pi f$  where  $f$  is in hertz (Hz). The source internal impedance  $Z_1$  is shown to be partly resistive and partly reactive. The reactive part is due to a capacitor  $C_1$  which may be blocking the internal supply voltages of the source from appearing at its output terminal. Alternatively it may be stopping the source circuit from upsetting the DC supply voltages of an amplifier which is forming the first stage of the load. Then  $C_1$  may actually be within the load but it can be considered as having an effect similar to that of  $R_1$ ; i.e. a voltage drop will occur across it so that part of  $v_1$  is dropped and not usefully developed across the resistive part of the load.

**Principles of amplifiers**

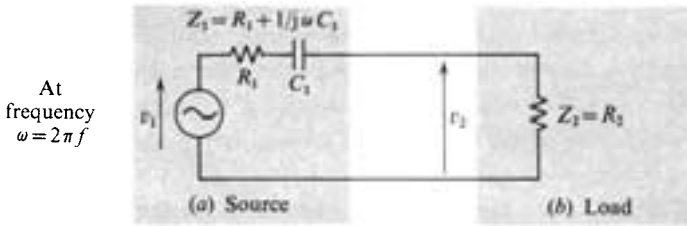


Fig. 1.15. Coupling circuit with series capacitor.

(b) is the load which is considered to be resistive only, so  $Z_2 = R_2$ . This is an approximation because there will be stray capacities in all circuits, but the fact is separately investigated in § 1.9.

We need to obtain an expression for the voltage  $v_2$  appearing at the load in terms of the source voltage  $v_1$ . The expression for voltage coupling gives

$$v_2 = v_1 \left( \frac{Z_2}{Z_1 + Z_2} \right) = v_1 \left( \frac{R_2}{R_1 + 1/j\omega C_1 + R_2} \right) = \frac{v_1 R_2 / (R_1 + R_2)}{1 + 1/j\omega C_1 (R_1 + R_2)}. \quad (1.10)$$

By studying the dimensions of each term of the final expression, it can be seen that the denominator must be dimensionless. Since  $\omega$  has the units of  $s^{-1}$ , the product  $C_1(R_1 + R_2)$  must have the units of seconds and is called the time constant,  $\tau_1$ . (This seems odd until the units of farads  $\times$  ohms are looked at more closely and are found to be seconds!)

Now we wish to find out how the expression for  $v_2$  changes with the frequency,  $\omega$ . We consider three cases.

(a) Frequency is high so  $\omega$  in the denominator of the expression makes the complex part  $\ll 1$ .

$$\text{So gain} = \frac{v_2}{v_1} \approx \frac{R_2}{R_1 + R_2} = B, \quad \text{say.} \quad (1.11)$$

Note that this is real and not imaginary. Therefore there is no phase shift associated with the circuit gain at high frequency. This is plotted in fig. 1.17 as the region (a).

(b) At a frequency  $\omega = \omega_1$ , such that

$$\omega_1 C_1 (R_1 + R_2) = 1 \quad \left( \text{i.e. } \omega_1 = \frac{1}{C_1 (R_1 + R_2)} = \frac{1}{\tau_1} \right). \quad (1.12)$$

$$\begin{aligned} \text{Gain} &= \frac{v_2}{v_1} = \frac{R_2 / (R_1 + R_2)}{1 + 1/j \cdot 1} = \frac{B}{1 - j} \\ &= \frac{B(1 + j)}{2} = 0.707B \angle +45^\circ. \end{aligned}$$

Fig. 1.16 shows the conversion from cartesian to polar co-ordinates.

### Coupling circuits at low frequency

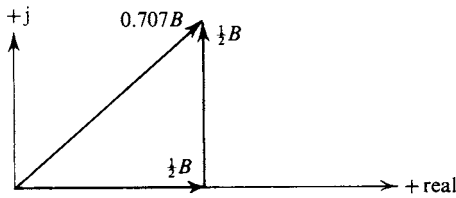


Fig. 1.16. Phasor diagram for gain at low frequency turnover.

At this particular frequency,  $\omega_1$ , the gain is 70.7 per cent of its value at the higher frequency and the phase shift is such that the output *leads* the input by  $45^\circ$ . This is plotted on fig. 1.17 in the region (b).  $\omega_1$  is called the *turnover frequency*.

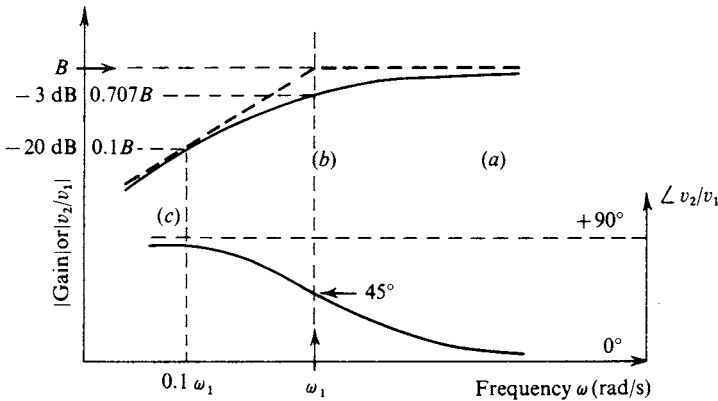


Fig. 1.17. Gain magnitude and phase angle plotted against frequency.

(c) The third region of interest is at very low frequency, well below the turnover frequency  $\omega_1$ . Remember that at  $\omega_1$ , the complex part of the denominator of the expression had equalled unity, so, at a much lower frequency,

$$\frac{1}{\omega C_1(R_1 + R_2)} \gg 1.$$

Using

$$C_1(R_1 + R_2) = \frac{1}{\omega_1},$$

then from (1.10)

$$\text{Gain} = \frac{v_2}{v_1} \approx \frac{R_2/(R_1 + R_2)}{\omega_1/j\omega} = 0 + jB \frac{\omega}{\omega_1} = B \frac{\omega}{\omega_1} \angle +90^\circ. \quad (1.13)$$

The final expression has been converted from complex terms to polar co-ordinates to give a magnitude and phase angle for the gain and these are shown in region (c) of figure 1.17.

## Principles of amplifiers

Thus at a frequency one tenth of the turnover frequency,  $\omega = 0.1\omega_1$ , the magnitude of the gain is  $0.1B$ , and at one hundredth of the turnover frequency, the gain is  $0.01B$ . Thus on a logarithmic plot of gain against frequency, the relation will be linear (note  $0.1B = 20 \log_{10} B - 20$  decibels and  $0.01B = 20 \log_{10} B - 40$  decibels because these are voltage ratios).

The broken lines on fig. 1.17 where the gain tends to a constant value  $B$  at frequencies above the frequency  $\omega_1$  and where the gain tends to fall linearly at frequencies below  $\omega_1$  show an approximate response curve which is called the asymptotic approximation to the frequency response. More accurately, the gain has dropped to  $0.707B$  at  $\omega_1$  and the response curve really passes through this point and is an asymptote to the two broken lines which are accurate for low or high frequencies. The reason for calling  $\omega_1$  the turnover frequency or break frequency can now be seen; clearly the gain has stopped being a constant figure  $B$  and drops steeply once the frequency drops below  $\omega_1$ .

The expression for gain gave an angle as well as a magnitude for the ratio  $v_2/v_1$ . Rewriting the expression as  $v_2 = \text{gain} \times v_1$ , we see that if the gain had a positive angle between  $0$  and  $90^\circ$  associated with it then  $v_2$  will lead  $v_1$  in phase by between  $0$  and  $90^\circ$ , the actual value depending on the frequency. The cartesian plot of  $\log |\text{gain}|$  and  $\angle \text{gain}$  against  $\log$  frequency is called the Bode plot for the circuit and fully specifies the gain of the circuit.

The alternative scaling on the  $|\text{gain}|$  axis shows how simple the relation becomes in decibels. If the output of  $Bv_1$  at higher frequencies is taken as the normal level, then when the frequency has dropped to  $\omega_1$ , the output is  $0.707$  of  $Bv_1$ .

$$\begin{aligned}\text{Voltage ratio } 0.707 &= 20 \log_{10} 0.707 \\ &= -20 \log_{10} 1.414 \\ &\approx -3 \text{ decibels.}\end{aligned}$$

When the frequency is well below  $\omega_1$ , if the frequency is halved, or dropped by an octave, the gain will also be halved.

$$\begin{aligned}\text{Voltage ratio } 0.5 &= 20 \log_{10} 0.5 \\ &= -20 \log_{10} 2.0 \approx -6 \text{ decibels.}\end{aligned}$$

So the slope of the asymptote is  $-6$  decibels/octave. It can alternatively be expressed as  $-20$  decibels/decade.

The analysis from fig. 1.15 showed the source as a voltage generator. A similar analysis could be done if the source was a current generator,  $i_1$ , and had a parallel conductance  $G_1$ . However it is easier to use the conversion from current to voltage source shown in fig. 1.18.