

Index

- ABCD parameters, 511, 515
- a.c. bridge, 132–6
- active element, 3
- active power, 187
- admittance, 123–6
 - complex, 116, 123
 - driving point, 504
 - generalized, 348, 361–3
 - transfer, 504
- admittance matrix, 513
- admittance parameters, 508
- alternating quantity, 2, 99
- ammeter, 251
- ampere, 6
- amplifier, 78, 510
- amplitude of a.c. waveform, 99
- amplitude
 - response, 367
 - spectrum, 474
- angular frequency, 99
- Argand diagram, 106
- argument of complex number, 105
- asymmetrical network, 87
- attenuator, 45, 534
- autotransformer, 214–17
- auxiliary equation, 288
- average power, 187

- balanced network, 87, 502
- band-pass characteristic, 157, 177
- bandwidth, 155
- battery model, 43
- bias point, 426
- bilateral element, 418
- Bode diagram, 130
- branch, 43

- break frequency, 131
- break point, 429
- bridge circuits, 61, 72, 132–40, 221
- Butterworth filter, 372

- capacitance, 2, 13, 103
 - stored energy in, 24
- capacitances
 - in parallel, 26
 - in series, 24
- capacitive circuit
 - reactance, 103
 - susceptance, 125
- capacitors
 - loss-angle in, 150
 - losses in, 149
 - model for, 36
- Cartesian coordinates, 106
- cascaded networks, 518, 530
- chain matrix, 518–25
- characteristic impedance, 532
- characteristics (of device), 419–25
- charge, 5
- circle diagram, 129
- circuit
 - active, 3
 - distributed, 3
 - dual, 37, 164
 - lumped model, 3
 - passive, 3, 44
- circuit reduction, 84
- coefficient of coupling, 33, 175
- coil, 26
- compensation theorem, 82
- complementary function, 285

574 *Index*

- complex
 - algebra, 106
 - conjugate, 198
 - exponential, 107
 - frequency, 348, 369
 - impedance, 110
 - plane, 106, 108, 361
 - power, 198
 - quantity, 105
- conductance, 19, 69, 124
- conduction angle, 20, 452
- conductivity, 20
- conjugate bridge, 133
- conservation
 - of charge, 13
 - of energy, 9, 13
 - of watts and vars, 194
- controlled source, 33, 75, 507
- convolution, 392–405
 - integral, 396
 - theorem, 401
- copper loss, 21, 213
- corner frequency, 131
- corresponding ends (of coil), 32, 142
- coulomb, 6
- coupled coils, 141, 301
- coupling coefficient, 33, 175
- coupling network, 127
- Cramer's rule, 54
- critical damping, 294
- critical coupling, 174–6
- current
 - alternating, 2, 98–101
 - direct, 2
- current convention, 7
- current divider, 45, 165
- current source, 11, 117

- D-impedance, 309
- D-operator, 304
- damped natural frequency, 294
- damped sinusoid, 293
- damping, 294, 362–4
- damping constant, 294
- decibel, 130
- delay time, 312
- delayed function, 326
- delta circuit, 66
- delta function, 319
- dependent source, 75
- determinant, 54
- differential operator, 309
- differentiating circuit, 316

- diode
 - ideal, 429
 - real, 437
 - zener, 437
- Dirac function, 319
- discontinuous function, 317
- discriminant, 293
- divider, 45, 350
- dot convention, 32, 142
- double-energy circuit, 291
- doublet (unit), 325
- driving point impedance, 143, 505
- duality, 37
- dual networks, 45, 67, 164
- dynamic resistance, 426
 - of resonant circuit, 166
- dynamometer, 251

- effective resistance, 146
- effective value of sinusoid, 100
- electrical angle, 100
- electrodynamometer, 251
- electrokinetic momentum, 347
- electromotive force (e.m.f.), 1, 27
- element
 - active, 3
 - bilateral, 418
 - ideal, 36
 - lumped, 3
 - non-linear, 418
 - passive, 3, 36
- energy
 - initial, 281, 291
 - sink, 1, 9
 - source, 1, 9
 - storage in elements, 2, 24, 28
- equivalent circuits
 - for capacitor, 149
 - for inductor, 147
 - series–parallel, 21
 - star–delta, 66
- Euler's identity, 105
- even function, 466
- excitation function, 349
- exciting current, 202, 205
- exponential Fourier series, 471

- farad, 23
- Faraday's law, 31
- field, 1
- filters
 - for rectifiers, 482–6
 - high-pass, 127

- low-pass, 372
- notch, 140
- twin-T, 136, 528
- final value theorem, 358
- first-order circuit, 291
- flux
 - density (B), 203
 - leakage, 202
 - magnetic, 26, 202
 - mutual, 31
- forced response, 285
- form factor, 101
- Foster's reactance theorem, 173
- Fourier series
 - coefficients, 460
 - cosine, 466
 - exponential, 471
 - for rectifier, 469
 - sine, 466
- frequency
 - angular, 99
 - complex, 348
 - half-power, 155
 - natural, 294
 - negative, 472
 - response, 126
 - spectrum, 466
 - undamped, 294
- frequency changer, 445
- function
 - network, 349
 - rational, 334
 - transfer, 126
- generalized network function, 349
- generator (three-phase), 231
- Gibbs phenomena, 465
- g -parameters, 507
- gyrator, 524
- half-power bandwidth, 155
- harmonic components, 461
- henry, 27
- hertz, 99
- hybrid parameters, 506
- hysteresis loss, 203
- ideal source, 11
- ideal transformer, 199, 522
- image impedance, 531
- immittance, 348
- impedance
 - complex, 110
 - D-operator, 309
 - driving point, 143, 504
 - dynamic, 166
 - generalized, 348
 - input, 143
 - modulus of, 110
 - transfer, 505
- impedance diagram, 115
- impedance matrix, 513
- impedance transformation, 200
- impulse
 - function, 317, 319
 - response, 320, 351
 - train, 392
- incremental (slope) resistance, 426
- independent parameters, 502
- induced e.m.f. 27
- inductance, 2, 26, 102
 - leakage, 207
 - mutual, 31, 35, 141
 - self, 26, 27
 - stored energy in, 28
- inductances
 - in parallel, 29
 - in series, 30
- inductive reactance, 103
- inductor
 - losses in, 146
 - model for, 36
- initial conditions, 281, 289
- initial value theorem, 358
- in-phase component, 192
- insertion loss, 536
- integrating circuit, 316
- inverse matrix, 515
- inverse transform, 328
- iron loss, 203
- iterative impedance, 530
- joule, 8
- j -operator, 106
- Kirchhoff's laws, 13–18, 419
 - current, 13
 - voltage, 16
- ladder method, 87, 372
- ladder network, 87
- Laplace transform, 328
 - of delayed functions, 358
 - of derivative, 330
 - of integral, 331
- lattice network, 72, 521

576 *Index*

- leakage inductance, 207
- linear element, 3, 418
- linearity, 57
- line spectra, 475
- load line, 423
- locus diagram, 129
- logarithmic decrement, 295
- loop, 44
- loop equations, 48, 52
- loss-angle (of capacitor), 150
- low-pass filter, 372
- lumped element, 3

- magnetizing current, 203
- magnetizing force (H), 203
- magnitude (of a.c. waveform), 100
- mark-space ratio, 376
- matching, 201, 218–21
- maximum power transfer, 217
- Maxwell's cyclic currents, 49
- mesh, 44
- mesh analysis, 47–50, 52, 71, 545
- Millman's theorem, 86
- mistuning, 160
- modulator, 445
- multiple resonance, 169–73
- mutual conductance, 69, 70
- mutual inductance, 31, 35, 141, 175, 344
- mutual resistance, 48, 53

- natural response, 285
- negative impedance converter, 524
- network, 44
- network function, 349
- nodal analysis, 67–70, 71, 125
- nodal equations, 69
- node, 13, 43
- non-linear elements, 3, 418
- Norton's theorem 64
- Nyquist diagram, 129

- Odd function, 466
- ohm, 19
- Ohm's law, 18, 112
- open-circuit impedance, 505
- open-circuit test, 209
- operating point, 425
- operational amplifier, 78, 510
- oscillatory response, 293, 363
- output resistance, 43, 80
- overdamped circuit, 294, 362

- parabola (unit), 325
- parallel resonant circuit, 164
- Parseval's theorem, 478
- partial fractions, 334–9
- particular integral, 285
- passive circuit, 3
- peak inverse voltage, 450
- period, 99
- periodicity theorem, 382
- phase angle, 99
- phase response, 239, 367
- phase sequence, 246
- phase sensitive detector, 447
- phase transformation, 270
- phasor
 - cartesian form, 105
 - diagram, 113, 118
 - polar form, 106
 - rotting, 107
 - stationary, 108
- pi-network, 516
- piecewise-linear circuits, 428–43
- poles
 - of admittance, 362
 - of impedance, 172
 - of network function, 360
 - repeated, 362
- pole-zero methods, 359–72
- pole-zero diagram, 361
- port, 44
- potential difference (p.d.), 7
- potentiometer, 46
- power
 - active and reactive, 187, 190
 - apparent, 191
 - average, 187–8
 - complex, 198
 - diagram, 249
 - in harmonic components, 478
 - instantaneous, 8, 188, 273
 - real, 187, 188
 - sign convention, 9, 188
 - triangle, 191
- power factor, 150, 194
- power factor correction, 194, 249
- practical voltage source, 42
- pulse
 - repeated, 376
 - transform of, 381

- quadrature component, 192
- quasi-steady state, 377

- Q*-factor,
 of capacitor, 150
 of inductor, 147
 of resonant circuit, 165, 169, 253,
 294
- radian, 99
 ramp function, 325
 rational function, 334
 rationalization, 124
 reactance, 103, 110
 reactive power, 190
 reciprocal network, 505
 reciprocity theorem, 58, 546
 rectifier circuits, 448
 bridge, 453
 full-wave, 453
 half-wave, 448
 ripple in, 482
 regulation (of transformer), 211
 resistance, 2, 18, 101
 resistances
 in parallel, 22
 in series, 21
 resistivity, 20
 resistor
 model for, 36
 non-linear, 445
 resonance, 146, 158
 resonance curve, 162
 resonant circuits
 inductively coupled, 173
 losses in, 151
 magnification factor in, 157, 165
 parallel, 164
 series, 151
 resonant frequency, 153, 158
 response function, 349
 root mean square (r.m.s.) value, 101,
 189, 478
 roots (of polynomial), 354
 Rosen's theorem, 67
- s* (complex frequency), 348
 domain, 340
 plane, 361
 sampling, 394
 Schering bridge, 133
 Scott connection, 271
 second-order circuit, 291
 self inductance, 26
 shift theorem, 357
- short-circuit test, 210
 siemens, 19, 124
 sifting property, 394
 single-energy circuit, 291
 singularity function, 317–27
 sink, 9
 skin effect, 146
 small-signal model, 426
 source,
 controlled, 33, 75, 507
 current, 12, 64
 dependent, 33, 75, 507
 ideal, 11
 practical, 42, 64
 transformation, 64
 voltage, 11, 64
 spectrum, 474
 stagger tuning, 177
 star connection, 66, 239
 star–delta transformation, 66, 86
 steady state, 280
 steady-state response, 285, 377
 step function, 318
 step response, 319
 substitution theorem, 81
 superposition theorem, 55, 546
 susceptance, 124
 symmetrical circuits, 87, 502
- tee network, 516
 Tee-pi transformation, 67, 138, 516
 Tellegen's theorem, 194
 Thévenin's theorem, 58, 313, 547
 Thévenin–Norton transformation,
 64, 117
 third-harmonic current, 269
 three-phase circuit, 233
 balanced load in, 236
 delta connection in, 239
 line voltage in, 235
 neutral point in, 235
 phase sequence in, 239, 246
 phase voltage in, 235
 star connection in, 239
 unbalanced load in, 245
 Y-connection in, 239
 thyristor, 455
 time constant, 286
 time domain, 340
 total response, 295
 transfer characteristic, 423
 transfer function, 126, 349

578 *Index*

- transfer impedance, 505
- transformer
 - auto, 214
 - copper loss in, 213
 - core loss in, 203, 213
 - efficiency in, 213
 - equivalent circuit, 261
 - ideal, 199
 - regulation in, 211
 - single phase, 201
 - tests, 209, 261
 - third harmonic currents in, 269
 - three-phase, 258
- transformer bridge, 221
- transient response, 282, 285
- transistor, 423
 - model, 426, 427, 509
 - parameters, 503
- transmission parameters, 511
- triac, 459
- triangular pulse, 383
- tuning, 157
- turnover frequency, 131
- twin-T network, 136, 528
- two-phase voltages, 271
- two-port network, 126, 501
- two-wattmeter method, 253

- unbalanced network, 87

- underdamped circuit, 294, 362
- universal resonance curve, 161
- unsymmetrical network, 503

- var, 191
- volt, 7
- volt-ampere, 191
- voltage divider, 44, 350
- voltage source
 - ideal, 11
 - practical, 42, 64

- watt, 8
- wattmeter, 251
- waveform
 - rectified sine, 304, 469–71
 - sawtooth, 384
 - square, 381, 463–6
 - trapezoidal, 499
 - triangular, 383, 466–8
 - TV video, 390
- Wheatstone bridge, 61, 72
- Wien bridge, 135

- Y– Δ transformation, 66, 244
- y-parameters, 503

- zeros of network function, 172, 360
- z-parameters, 505