

# Index

- anomalous eddy current losses 351–6
- antenna, three-winding parallel resonant transformer 344–9
- approximate factors of a polynomial 142, 260, 311
- band-pass response 49
- band-reject response 49
- block diagram 17
  - common-emitter amplifier 55–6
  - feedback system 56
- Bode plot 43
  - first-order transfer functions 43–8
  - second-order transfer function 49–52
- boost converter
  - basic operation 386–92
  - conversion ratio 386–8
  - inductor current ripple 386–7
  - OrCAD/Pspice simulation 389–91
  - output voltage ripple (heavy load) 388–9
  - output voltage ripple (light or no load) 466
  - peak current-mode control 446–50
- bridge circuit
  - input impedance 2–12, 87
  - null-impedance calculations 64–8
  - phase shifter 101
  - RHP zero 83–4
  - voltage transfer functions 78–83
- bridge circuit with dependent source
  - input impedance 4–11
- buck converter
  - basic operation 370–9
  - conversion ratio 371
  - discontinuous conduction mode (DCM) 378–9
  - inductor current ripple 374–6
  - input filter 379–85
  - output voltage ripple 372–3, 464
  - OrCAD/Pspice simulation 384–5
  - single-loop voltage feedback control 433–9
  - voltage and current feedback control 453–9
- buck-boost converter
  - basic operation 392–7
  - control-to-output transfer function 404, 408–11
  - conversion ratio 393
  - inductor current ripple 394–6
  - input admittance 404, 408
  - line-to-output transfer function 404, 407
- OrCAD/Pspice simulation 395–7
  - output impedance 404, 408
  - output voltage ripple (heavy load) 394
  - output voltage ripple (light or no load) 466–7
  - RHP zero 410–1
- Cantor set 354
- capacitively tapped parallel resonant circuit 339–44
- cascaded resonant circuits 60
- cascode amplifier 191–5
- cascode MOS amplifier 252–61
  - bandwidth 261
- CC-PWM (current controlled PWM switch 440, 443–7
  - large-signal average model 443
  - small-signal average model 444–5
- CE–CE amplifier 181–5, 188–91, 240–2, 244
- characteristic equation 19
- Chebyshev fifth-order low-pass filter 261–4
- closed-loop gain, ideal 196, 274
- CMLSCCM (current-mode large-signal continuous conduction mode) subcircuit 456–9
- Colpitts oscillator 220–5, 248–51
- common-emitter amplifier
  - collector-to-base feedback resistor 29–30, 57–8
  - gain analysis 28–30, 124–30
  - Miller effect 53–55
  - pole due to emitter bypass capacitor, 28–30, 57–8
- complete response of a linear system 34–41
- conditional stability 227
- conducted emissions 379–80
- constant phase angle behavior, and infinite scaling networks 351
- conversion ratio
  - current 366
  - voltage 366
- converters *see* boost converter; buck converter; buck-boost converter; Cuk converter; inverse Watkins–Johnson converter; tapped buck converter; Watkins–Johnson converter; quadratic converters, fourth-order converters
- coupling coefficient 345
- Cuk converter 464–7

- low current ripple benefits 398–400
- storage time modulation 468–70
- with isolation transformer 467
- with switches rearranged 415–17
- current feedback pair 133–7
- current gain transfer function, definition 17
- current mixing and input impedance analysis 196–200
- current-mode control 440–6
- current-sampling current-mixing feedback amplifier 188–91, 240–2
- current-sampling voltage-mixing feedback amplifier 181–5, 236–9
- current sensing and output admittance analysis 209–13
- current source, output impedance 13
- dc-to-dc converters 365–470
  - basic characteristics 366–9
  - battery charger 369–70
  - boost converter 386–92, 466
  - buck-boost converter 392–7, 466–7
  - buck converter 370–85, 464–5, 467
  - Cuk converter 397–400, 467–70
  - fourth-order converter 415–17
  - input resistance 368
  - inverse Watkins–Johnson converter 468
  - output resistance 462–3
  - quadratic converters 417–26
  - tapped buck converter 412–15
  - Watkins–Johnson converter 414–15
- delay networks/equalizers, lattice filters as 327–35
- differential amplifier with adjustable gain 99–101
- discontinuous conduction mode (DCM), buck converter 378
- driving-point admittance function, definition 17–19
- driving-point analysis, feedback amplifiers 170–5
  - basic principle 170–1
  - FET amplifier 171–5, 236
  - input admittance for voltage mixing 204–9, 245
  - input impedance for current mixing 196–200, 244
  - inside input conductance in shunt-series feedback 206–9
  - inside output impedance in shunt-series feedback 202–4
  - output admittance for current-sensing 209–13, 246
  - output impedance for voltage sensing 200–4, 244
- driving-point impedance function, definition 17–19
- duty ratio function 371
- dynamic load response 439, 459
- effective turns ratio 345
- efficiency of dc-to-dc converters 366
- emitter-follower, output impedance 105
- entropy
  - high-entropy versus low-entropy expressions 11–12
  - low-entropy expressions 1, 4, 7
- equalizer 123–4, 327–35
- extra-element theorem (EET) 61–106
  - advantages 4
  - Bode's contribution to its origins 61
  - for dependent sources 88–91
  - for impedance elements 74–7
  - null double injection 62–4
  - see also* *N*-extra element theorem (NEET)
- excitation of a transfer function 15
- excitation of an impedance function 18–19
- fast analytical techniques 1–2
- feedback amplifiers *see* driving point analysis, feedback amplifiers; gain analysis, feedback amplifiers; loop gain; phase and gain margins; stability
- feedback control of dc-to-dc converters 432–59
  - current feedback control 440–46
  - single-loop voltage feedback control 433–9
  - two-loop with voltage feedback and peak current control 453–9
- feedback theorem due to Middlebrook 176
- FET amplifier with feedback
  - gain analysis 166–70
  - input impedance 236
  - loop gain 176–9, 236
  - output impedance 171–5
- filters, passive
  - capacitively tapped parallel resonant filter 339–44
  - Chebyshev fifth-order low-pass filter 261–5
  - lattice filters 327–35
  - parallel resonant 336–9
  - RC filters with gain 317–26, 359–61
  - three-winding parallel resonant transformer 344–9, 362
- fourth-order converters 415–17
- fractal dimension 354
- fractal networks 351–7
- fractional derivative 357
- functional equation, fractal network 353
- gain analysis, feedback amplifiers 164–6, 180–95
  - CE–CE amplifier with series-shunt feedback 181–5, 236–9
  - closed-loop gain using the EET 164–5
  - current-loaded cascode amplifier with shunt-shunt feedback 191–5, 242–3

- gain analysis, feedback amplifiers (*cont.*)  
 differential input followed by a CE amplifier  
 stage with shunt-series feedback 157, 185–8,  
 239–40  
 FET shunt-shunt feedback amplifier 166–70,  
 236  
 two-stage CE series-series feedback with  
 current-sense transformer 188–91, 240–2
- gain margin *see* phase and gain margins
- general linear element 137
- high-frequency and microwave circuits *see* cascode  
 MOS amplifier; Chebyshev fifth-order  
 low-pass filter; MESFET amplifier; video  
 amplifier
- ideal closed-loop gain 196, 273  
 indeterminacy 157–9, 423
- index permutation symbol 138
- infinite grid 349–51, 362
- infinite ladder 350–1, 363
- infinite scaling networks 349–56  
 constant phase angle behavior 351  
 fractal dimension 354  
 fractional derivative 357  
 functional equation 353  
 power law 356  
 Riemann–Liouville fractional integral 357  
 unified model for  $R$ ,  $L$  and  $C$  356–7
- input filter  
 buck-boost 395  
 buck converter 379–85, 464  
 series damping 380, 466  
 shunt or parallel damping 380, 465
- input impedance/admittance *see* driving-point  
 analysis, feedback amplifiers
- inverse gain 89–91, 132, 138
- inverse Watkin–Johnson converter 468
- lattice fitters 327–35
- linear regulator  
 series 461–2  
 shunt 462
- loading of feedback network  
 current mixing 197  
 current sensing 211  
 voltage mixing 206  
 voltage sensing 202
- loop gain 175–6  
 current/voltage loop gain 247–8  
 injection at an arbitrary point 213–18, 246  
 injection immediately after the amplifying  
 element 213  
 in buck converter 437, 456  
 measurement by injection 236, 250, 437, 456  
 low-entropy expressions 1, 4, 7, 11–12
- magnitude and phase response 41–3
- MESFET amplifier 265–310  
 bandwidth 310  
 microwave and high-frequency circuits *see* cascode  
 MOS amplifier; Chebyshev fifth-order  
 low-pass filter; MESFET amplifier; video  
 amplifier
- minimum phase systems 218
- MOS amplifier, cascode *see* cascode MOS  
 amplifier
- mutual inductance 345
- $N$ -extra-element-theorem (NEET) 137–9  
 2-EET for dependent sources, 130–2  
 2-EET for impedance elements 108–10  
 determinant form 148  
 proof of NEET 147–153  
 redundancy relations 139  
 reference element function 138  
 reference inverse gain function 138  
 reference network 108  
 reference null inverse gain function 138  
 reference state of a port 108–9  
 reference transfer function 109–10
- negative null impedance 68, 83–4
- $N$ -port network 107, 147
- notch filter 32–4, 139–47
- null double injection 62–4
- null-driving point impedance 64
- null-inverse gain 90, 131, 138
- null response in transform circuit 24–5
- nulls of a transfer function 24–5
- Nyquist plot and stability condition 218–19,  
 225–6
- open-short theorem 115, 154
- operational amplifier, nonideal  
 gain in inverting configuration 95–7  
 gain in noninverting configuration 97–8  
 input impedance in noninverting configuration  
 92–5  
 output impedance in inverting configuration 91  
 pole-zero compensation 58–60  
 transimpedance amplifier 228–32
- operational amplifier with T-feedback 68–9, 84
- opposite state of a port 109
- OrCAD/Pspice simulations  
 boost converter 389–92  
 buck-boost converter 395–7  
 buck converter with peak current-mode control  
 456–9  
 buck converter with voltage feedback 437–9  
 cascode amplifier 242–3  
 Colpitts oscillator 248–50  
 differential input amplifier with voltage sampling  
 and voltage mixing 239–40, 244–5  
 input filter for buck converter 382–5  
 loop gain measurement in a FET amplifier  
 237

- loop gain measurement in the buck converter 437–8
- loop gain measurement in the buck converter with current mode control 459
- quadratic converter 468
- three-winding-parallel resonant transformer 362–3
- two-stage CE–CE amplifier with current sampling and current mixing 236–9, 244
- two-stage CE–CE amplifier with current sampling and voltage mixing 240–2, 246
- unstable loop-gain measurement 250
- video amplifier 311–16
- oscillation *see* stability
- output impedance/admittance *see* driving-point analysis, feedback amplifiers
- parameter-extraction method 5
- passive filters *see* filters, passive
- peak current control
  - model of PWM switch 440–5,
  - model of the current loop 450–3
  - subharmonic oscillation 441
- permutation symbol, index 138
- phase and gain margins 226–32
- phase and magnitude response 41–3
- phase shifter 83, 101–2
- phasor notation 42
- poles of a network 17, 19–24
- port
  - opposite state 109
  - reference state 108
- PWM switch
  - average large-signal and small-signal models 402–3
  - current-controlled PWM switch 440–4
  - effect of parasitic elements 426–32
  - high-frequency resistance across port  $a$ – $p$  426–9
  - invariant terminal characteristics 400–2
  - on-resistance of the switches 429–30
  - saturation models of the switches 431–2
  - storage time modulation 430–1
- $Q$ -factor 2–7
  - high- $Q$  approximation of parallel resonant filter 337–9
  - tapped parallel resonant filter 343
  - three-winding parallel resonant filter 347
  - triple-damped parallel resonant filter 337
- quadratic converter 418, 468
  - control-to-output transfer function 420–6
  - conversion ratio 420
- $RC$  filter with gain *see* filters, passive
- redundancy relations 139
- reference element function 136
- reference inverse gain function 138
- reference network 108
- reference null inverse gain function 138
- reference state of a port 108–9
- reference transfer function 109–10
- resonant filter *see* filters, passive
- Riemman–Liouville fractional integral 357
- right-half plane (RHP) zero
  - in bridge circuits 57, 83–4
  - in buck-boost converter 410–11
  - in cascode MOS amplifier 253
  - in CE amplifier 30, 53–4
- scaling equation 354
- scaling/fractal networks 351
- series-series feedback *see* current-sampling voltage-mixing feedback
- series-shunt feedback *see* current-sampling current-mixing feedback
- shunt-series feedback *see* voltage-sampling voltage-mixing feedback
- shunt-shunt feedback *see* voltage-sampling current-mixing feedback
- stability
  - conditional 227
  - feedback systems 218–26
  - frequency-domain and time-domain equivalence 35–41
  - impedance criteria 222–5
  - Nyquist encirclement stability condition 225–6
- stability margin *see* phase and gain, margins
- storage time modulation 430, 468–70
- subharmonic oscillation 440–6
- subtractor with adjustable gain 99
- tapped buck converter *see* dc-to-dc converters
- three-winding transformer 345–9, 362–3
- transadmittance transfer function, definition 17–19
- transfer function
  - contribution of a  $1:m$  transformer to a transfer function 154–7
  - determination of poles 19–21
  - determination of zeros 24–5
  - first-order 43–8
  - second-order 48–52
  - six different types in an electrical circuit, definition 15–17
- transimpedance transfer function, definition 15–17
- transimpedance operational amplifier 228–32
- unstable systems *see* stability
- video amplifier frequency response 311–16
- VMLSCCM (voltage mode large-signal continuous conduction mode) subcircuit for the PWM switch 437

Cambridge University Press

0521624428 - Fast Analytical Techniques for Electrical and Electronic Circuits

Vatche Vorperian

Index

[More information](#)**476** **Index**

---

- voltage gain transfer function, definition 17–19
- voltage mixing and input admittance *see*  
driving-point analysis, feedback amplifiers
- voltage sampling and output impedance *see*  
driving-point analysis, feedback amplifiers
- voltage-sampling current-mixing feedback  
amplifier 166–70, 191–5, 236, 242–3
- voltage-sampling voltage-mixing feedback  
amplifier 157, 185–8, 239–40
- wave translation system patent 163
- Watkins–Johnson converter 414–15, 467  
inverse converter 468
- zeros of a transfer function 17, 24–5  
determination principle 24–5