

Contents

<i>Preface</i>	xi
1 Introduction	1
1.1 Fast analytical methods	1
1.2 Input impedance of a bridge circuit	2
1.3 Input impedance of a bridge circuit with a dependent source	4
1.4 Input impedance of a reactive bridge circuit with a dependent source	8
1.5 Review	11
Problems	11
References	14
2 Transfer functions	15
2.1 Definition of a transfer function	15
2.2 The six types of transfer functions of an electrical circuit	17
2.3 Determination of the poles of a network	19
2.4 Determination of the zeros of a transfer function	24
2.5 The complete response, stability and transfer functions	34
2.6 Magnitude and phase response	41
2.7 First-order transfer functions	43
2.8 Second-order transfer functions	48
2.9 Review	52
Problems	53
3 The extra element theorem	61
3.1 Introduction	61
3.2 Null double injection	62

viii Contents

3.3	The EET for impedance elements	74
3.4	The EET for dependent sources	88
3.5	Review	98
	Problems	99
	References	106

4 The N -extra element theorem 107

4.1	Introduction	107
4.2	The 2-EET for impedance elements	108
4.3	The 2-EET for dependent sources	130
4.4	The NEET	137
4.5	A proof of the NEET	147
4.6	Review	153
	Problems	154
	References	162

5 Electronic negative feedback 163

5.1	Introduction	163
5.2	The EET for dependent sources and formulation of electronic feedback	164
	5.2.1 Gain analysis	164
	5.2.2 Driving-point analysis	170
	5.2.3 Loop gain	175
5.3	Does this <i>circuit</i> have feedback or not? This is <i>not</i> the question	179
5.4	Gain analysis of feedback amplifiers	180
5.5	Driving-point analysis of feedback amplifiers	195
	5.5.1 Input <i>impedance</i> for current mixing	196
	5.5.2 Output <i>impedance</i> for voltage sensing	200
	5.5.3 Input <i>admittance</i> for voltage mixing	204
	5.5.4 Output <i>admittance</i> for current sensing	209
5.6	Loop gain: a more detailed look	213
5.7	Stability	218
5.8	Phase and gain margins	226
5.9	Review	233
	Problems	234
	References	251

ix Contents

6	High-frequency and microwave circuits	252
6.1	Introduction	252
6.2	Cascode MOS amplifier	252
6.3	Fifth-order Chebyshev low-pass filter	261
6.4	MESFET amplifier	265
6.5	Review	310
	Problems	311
	References	316
7	Passive filters	317
7.1	Introduction	317
7.2	RC filters with gain	317
7.3	Lattice filters	327
7.4	Resonant filters	335
	7.4.1 Parallel resonant filters	336
	7.4.2 Tapped parallel resonant filter	339
	7.4.3 The three-winding transformer	344
7.5	Infinite scaling networks	349
	7.5.1 Infinite grid	349
	7.5.2 Infinite scaling networks	351
	7.5.3 A generalized linear element and a unified R , L and C model	356
7.6	Review	358
	Problems	358
	References	364
8	PWM switching dc-to-dc converters	365
8.1	Introduction	365
8.2	Basic characteristics of dc-to-dc converters	366
8.3	The buck converter	370
8.4	The boost converter	386
8.5	The buck-boost converter	392
8.6	The Cuk converter	397
8.7	The PWM switch and its invariant terminal characteristics	400

Cambridge University Press

0521624428 - Fast Analytical Techniques for Electrical and Electronic Circuits

Vatche Vorperian

Table of Contents

[More information](#)**x** **Contents**

8.8	Average large-signal and small-signal equivalent circuit models of the PWM switch	402
8.9	The PWM switch in other converter topologies	411
8.10	The effect of parasitic elements on the model of the PWM switch	426
8.11	Feedback control of dc-to-dc converters	432
	8.11.1 Single-loop voltage feedback control	433
	8.11.2 Current feedback control	440
	8.11.3 Voltage feedback control with peak current control	453
8.12	Review	460
	Problems	461
	References	470
	<i>Index</i>	472