

CONTENTS

<i>Preface</i>	<i>page xi</i>
1 ELECTRONIC SYSTEMS: A CENTURY OF PROGRESS	1
1.1 Electronic Devices: An Overview	3
The Diode: 3 • The Vacuum Triode: 5 • The Transistor and Integrated Circuits: 6	
1.2 Wireless Communication: A New Era	8
Electrical Tuning: 9 • Vacuum Tube Circuits: 10 • The Superheterodyne Receiver: 11	
1.3 The Telegraph and Telephone: Wide-Scale Interconnections	13
The Telegraph: 13 • Basic Telephone System: 14 • Analog Telephone Signals: 15 • Digital Telephone Systems: 17	
1.4 Television: Time-Dependent Visual Images	19
Analog Television: 20 • Cathode-Ray Tube Display: 21 • Video Camera Devices: 23 • Digital Television: 26	
1.5 The Electromagnetic Spectrum: A Multitude of Uses	28
Frequency Spectrum: 29 • Radar: 30 • Communications Satellites: 32	
1.6 Computers: Transistors By the Millions	35
Logic Circuits: 35 • A Basic Computer: 38 • Memories: 42	
1.7 Integrated Circuits: Shrinking Device Sizes and Increased Complexity	45
REFERENCES	47
PROBLEMS	49
COMPUTER SIMULATIONS	56
2 THE SEMICONDUCTOR JUNCTION DIODE: THE BASIS OF MODERN ELECTRONICS	59
2.1 Electrons and Conduction: A Look at Elementary Processes	60

2.2	Semiconductors: The Role of Electrons and Holes	65
	An Intrinsic Semiconductor: 67 • An <i>n</i> -type Semiconductor: 68 • A <i>p</i> -type Semiconductor: 69	
2.3	The Junction Diode: A Quintessential Semiconductor Device	72
	The Built-in Potential: 75 • An External Potential: 76	
2.4	The Junction Diode: Its Terminal Characteristics	77
	Current of a Diode: 78 • SPICE Model: 81	
2.5	A Circuit with a Diode: Dealing with a Nonlinear Element	83
	Load Line: 84 • An Iterative Approach: 85 • SPICE Solution: 87	
2.6	Modeling the Junction Diode: The Role of Approximations	92
	The Ideal Diode Switch Model: 92 • Constant Forward-Biased Voltage Diode Model: 94 • Diode Model with a Series Resistor: 95	
2.7	The Photovoltaic Cell: Photon–Semiconductor Interactions	100
	Photons: 100	
2.8	Light-Emitting and Laser Diodes: Optical Communication	107
	Light-Emitting Diodes: 107 • Light-Emitting Diode Applications: 108	
	REFERENCES	116
	PROBLEMS	118
	COMPUTER SIMULATIONS	129
3	THE BIPOLAR JUNCTION TRANSISTOR: AN ACTIVE ELECTRONIC DEVICE	133
3.1	The Common–Base Configuration: A Physical Description	137
3.2	The Common–Emitter Configuration: Same Device, Different Perspective	143
	Equivalent Circuit: 143 • Transfer Characteristic: 144 • SPICE Simulation Model: 146	
3.3	The Common–Emitter Equivalent Circuit: Solving Transistor Circuits	153
	An External Base Bias: 154 • An Emitter Resistor: 155 • An Emitter–Follower Circuit: 158	
3.4	Digital Logic Circuits: Static and Dynamic Characteristics	164
	Transistor Operating Regions: 165 • Capacitive Load: 166 • Logic Families: 170 • Transistor–Transistor Logic: 173	
3.5	Amplifier Circuits: Small-Signal Behavior	177
	Analog Signals: 178 • Capacitive Coupling: 179 • Small-Signal Equivalent Circuit: 181 • Hybrid- π Transistor Model: 183	
3.6	The PNP Transistor: A Complementary Device	190
	Complementary Symmetry: 193	

REFERENCES	198
PROBLEMS	199
COMPUTER SIMULATIONS	210
DESIGN EXERCISES	214
4 THE METAL-OXIDE FIELD-EFFECT TRANSISTOR: ANOTHER ACTIVE DEVICE	217
4.1 Field-Induced Carriers: The Physics of a MOSFET Device SPICE Model: 226	221
4.2 The Common-Source Equivalent Circuit: Applications A Common-Source Amplifier: 233 • A Source-Follower Amplifier: 235	231
4.3 MOSFET Logic Gates: Basic Considerations An Elementary Logic Inverter: 246 • A MOSFET Inverter Gate: 247	244
4.4 Integrated-Circuit Logic Gates: No Resistors An Enhancement-Type Load: 253 • Substrate Bias: 255 • A Depletion-Type Load: 257	253
4.5 Complementary Metal-Oxide Semiconductor Logic Gates: An Energy-Efficient Logic Family The <i>p</i> -Channel MOSFET Device: 262 • A CMOS Inverter Gate: 264 • CMOS Logic Gates: 268	262
4.6 Logic Memories: The Basis of Megabytes of Storage A MOSFET Bistable Circuit: 272 • A Flip-Flop Memory Element: 274 • A Memory Array: 275 • The Dynamic Memory Array: 278	272
REFERENCES	283
PROBLEMS	284
COMPUTER SIMULATIONS	295
DESIGN EXERCISES	296
5 NEGATIVE FEEDBACK AND OPERATIONAL AMPLIFIERS	299
5.1 Negative Feedback: A Key Concept Decibel Notation: 304 • Reducing Distortion: 305 • Additional Benefits of Negative Feedback: 309	303
5.2 Stability: Not All Amplifiers Are Equal Amplifier Phase Shift: 317 • Stability: 321	316
5.3 Analysis of Operational Amplifier Circuits: Basic Considerations Ideal Op Amp – Input Virtual Short: 327 • Op Amp Limitations: 331	327
5.4 Preemphasis and Deemphasis Circuits: Design Examples	339

	Preemphasis Circuit: 340 • Deemphasis Circuit: 341 • Design: 342 • SPICE Verification: 344	
5.5	A Wide-bandwidth Amplifier: A Design Example	346
	Single-Stage Amplifier: 347 • Two-Stage Amplifier: 348 • Three-Stage Amplifier: 349 • Final Design: 350 • SPICE Verification: 352	
	REFERENCES	355
	PROBLEMS	356
	COMPUTER SIMULATIONS	363
	DESIGN EXERCISES	366
6	ELECTRONIC POWER SUPPLIES	369
6.1	Rectifiers: From Alternating to Direct Current	371
	The Half-Wave Rectifier: 371 • Full-Wave Rectifier – A Center-Tapped Transformer: 373 • Full-Wave Rectification – A Bridge Rectifier: 374	
6.2	Filters: Reducing Load-Voltage Fluctuations	380
	Capacitor Filters – Half-Wave Rectifiers: 380 • Capacitor Filters – Full-Wave Rectifiers: 383 • A Nonideal Transformer: 384	
6.3	Zener Diode Regulator: An Improved Output Voltage	390
6.4	An Electronic Regulator: Nearly Ideal Power Supply	396
	A Basic Operational Amplifier Regulator: 396 • An Electronic Regulator with a Zener Diode Voltage Reference: 398 • An Electronic Regulator with a Band-Gap Voltage Reference: 399 • The Electronic Switching Regulator: 404	
6.5	Batteries: An Increasingly Important Electrical Energy Source	406
	REFERENCES	411
	PROBLEMS	412
	COMPUTER SIMULATIONS	419
	DESIGN EXERCISES	421
	APPENDIX A FABRICATION OF INTEGRATED CIRCUITS	423
A.1	Integrated Circuit Transistors	424
A.2	Fabrication Processes	427
	Crystal Growth and Wafer Fabrication: 427 • Epitaxial Deposition: 428 • Doping: Thermal Diffusion: 428 • Doping: Ion Implantation: 429 • Thermal Oxidation: 429 • Optical Lithography: 429 • Etching: 431 • Thin Films: 431	
A.3	Summary	432
	REFERENCES	432

APPENDIX B THE DESIGN PROCESS	434
B.1 Bipolar Junction Transistor Circuits (Chapter 3)	435
A Single-Transistor Logic Inverter: 435 • Design: 435 •	
A Single-Transistor Small-Signal Amplifier: 436 • Design: 437	
B.2 Metal-Oxide Field-Effect Transistor (Chapter 4)	439
Biasing a MOSFET Circuit: 439 • Design: 439	
B.3 Negative Feedback and Operational Amplifiers (Chapter 5)	442
A Small-Signal Amplifier: 442 • Design: 443	
B.4 Electronic Power Supplies (Chapter 6)	445
Power Supply With a Selectable Output Voltage: 445 •	
Design: 445	
REFERENCES	449
<i>Index</i>	451