

## Index

- $\beta$ , 48–50
- $h_{FE}$ , 48–50
- $Q$ , 124
- $r_{BE}$ , 53, 57
- $r_e$ , 52, 57
- $V_{BE}$ , 50, 52
- $V_{CB}$ , 50
- $V_{CE}$ , 51
  
- 3 dB point, 26
- 2N3904 pinout, 54
- 2N3906 pinout, 54
- 2N5485 pinout, 69
- 311 comparator, 114
- 311 pinout, 114
- 555 timer, 118, 156
- 7400 IC series, 125
- 741 op amp, 85
- 741 pinout, 86
- 74121 monostable, 156, 159
- 74121 pinout, 159
- 74138 decoder, 178
- 74150 mux, 162
- 74150 pinout, 162
- 74191 counter, 168
- 7489 RAM, 163
- 7489 pinout, 163
  
- AC coupling, 43
- acceptor, 32
- active bandpass filter, 123
- active differentiator, 102, 106
- active filter, 123
- active integrator, 103, 107
- active rectifier, 108
- ADC, 167
  - successive-approximation, 171
  - tracking, 170
- addition, binary, 141
- algebra, Boolean, 126, 140, 141
- alternating current, 15
- ammeter, ideal, 39
- amplifier, 50
  - common-emitter, 57
  - difference, 95
  - differential, 86
  - exponential, 105
  - grounded-emitter, 59
  - inverting, 168
    - op amp, 88
  - logarithmic, 105
  - noninverting, 89
    - op amp, 89
  - operational, 79, 85
- amplitude, 13, 17, 18
- analog, 167
- analog information, 167
- analog-to-digital conversion, 167
- analog-to-digital converter, 167
- anode, 35, 54
- arithmetic, binary, 125, 126, 141
- assertion-level logic, 127, 146
- assertion-level logic notation, 146
- astable multivibrator, 120, 156
- asynchronous counter, 151, 157
- attenuating probe, 10
- attenuation, 10, 26, 77
- attenuator, 76, 77, 91
  
- bandpass filter, 123
- bandwidth, 87
- base, 48
- BCD counter, 157
- bi-quinary counter, 157
- bias current, 94
- binary addition, 141
- binary arithmetic, 125, 126, 141
- binary counter, 156, 157
- binary search algorithm, 171
- binary-coded decimal, 157
- bipolar junction transistor, 47
- bistable multivibrator, 143, 156
- blocking capacitor, 56
- Boolean algebra, 126, 140, 141
- bounce, contact, 152
- breadboard, 2
- breadboard LED indicators, 137
- breadboard level switches, 137, 138
- breakpoint, 26
- buffer, 55
  - push–pull, 62

- buffering, 55
- capacitance code, 20
- capacitance
  - parasitic, 56
  - stray, 115
- capacitive reactance, 19
- capacitor, 15, 16, 19, 20
  - blocking, 56
  - ceramic, 16
  - electrolytic, 16
  - mica, 16
  - paper, 16
  - polarized, 16
  - types of, 16
- carry-in, 156
- carry-out, 156, 157
- cascaded counters, 156
- cathode, 35, 54
- clipping, 77
- closed-loop, 89
- CMOS, 125
- CMOS ICs, powering, 136
- CMOS logic, 133
- CMOS TTL, 133
- CMRR, 78, 96, 97
- collector, 48
- common-emitter amplifier, 57
- common-mode, 78
- common-mode gain, 78
- common-mode rejection, 78
- common-mode rejection ratio, 78, 96
- comparator, 113
  - 311, 114
  - voltage, 113
  - magnitude, 142
- compliance, 59, 71
- contact bounce, 152
- conversion
  - analog-to-digital, 167
  - digital-to-analog, 167
- converter
  - analog-to-digital, 167
  - digital-to-analog, 167
- counter, 151, 152, 156
  - 74191, 168
  - asynchronous, 151, 157
  - BCD, 157
  - bi-quinary, 157
  - binary, 156, 157
  - decade, 157
  - cascaded, 156
  - decimal, 157, 158
  - four-bit, 157
  - negative-edge-triggered, 157
  - ripple, 151, 157
  - synchronous, 152, 157
  - two-bit, 151, 156
- crossover distortion, 63, 109
- CRT, 9
- current mirror, 79
- current source
  - FET, 70
  - op amp, 97
  - transistor, 59
- current-source load, FET, 72
- CY62256 memory, 177
- D-type flip-flop, 147
- DAC, 167
- DAC0806, 174
- DAC080x, 178
  - family, 174
- Darlington, 61
- data selector, 162
- DC coupling, 79, 85
- DC offset, 87
- debouncer, switch, 153
- debugging, 144
- debugging digital logic, 144
- decade counter, 157
- decibel, 26, 83
- decimal, binary-coded, 157
- decimal counter, 157, 158
- decoder, 178
  - 74138, 178
- delay, propagation, 148
- DeMorgan's theorem, 141, 146
- diagram
  - state, 143
  - timing, 143
- dielectric, 16
- dielectric constant, 16
- difference amplifier, 95
- differential amplifier, 75, 76, 86
- differential gain, 76, 77
- differential signal, 75
- differentiator, 15, 27, 75, 102
  - active, 102, 106
  - op amp, 102, 106
- digital, 167
- digital information, 167
- digital logic, 125
  - debugging, 144
- digital meter, 1
- digital recording, 177
- digital-to-analog conversion, 167
- digital-to-analog converter, 167
- diode, 31
  - gate-channel, 66
  - light-emitting, 60
  - zener, 123
- diode characteristic, 31, 33, 34
- diode constant,  $n$ , 106
- diode drop, 37
- diode logic, 131
- diode test, multimeter, 54
- diode-bridge rectifier, 43
- DIP IC package, pin numbers, 129

- display
  - logic-level, 137
  - TIL311, 158
- distortion, 58
  - crossover, 63, 109
- divide-by-four circuit, 151
- divide-by-ten circuit, 158
- divide-by-two circuit, 148
- DMM, 1
- donor, 32
- driver, push-pull, 109
- DVM, 1
- dynamic resistance, 37, 52, 57
  - of diode, 37
  - of emitter, 52
  - FET source, 72
- Ebers-Moll transistor model, 52
- ECL, 125
- electrolytic, 16
- electrolytic capacitor, 16
- emitter, 48
- emitter follower, 55
- emitter resistance, 52
- equality tester, 141
- exclusive-OR gate, 141
- exponential amplifier, 105
  
- factor, quality ( $Q$ ), 124
- false, 126
- feedback, 79
  - negative, 71, 75, 79, 88, 117
  - positive, 62, 113, 117
- FET, 65
- FET current source, 70
- FET saturation, 67
- filter, 123
  - active, 123
  - bandpass, 123
  - high-pass, 15, 28
  - low-pass, 15, 25, 28
- finite-state machine, 143, 162
- flip-flop, 143, 156
  - D-type, 147
  - JK, 148
  - toggling, 148
- follower, voltage, 94
- forward-bias, 34
- four-bit counter, 157
- frequency domain, 15, 101
- function generator, 2, 13
  
- gain, common-mode, 78
- gain, differential, 77
- gate current, 66
- gate
  - exclusive-OR, 141
  - NAND, 140
  - OR, 142
  - XOR, 141
- gate-channel diode, 66
- golden rules, op amp, 90
- ground, virtual, 93, 168
- ground clip, 10
- grounded-emitter amplifier, 59
  
- half-power frequency, 26
- hexadecimal, 158, 164
- hexadecimal display, TIL311, 158
- high (logic level), 126
- hysteresis, 116, 170
  
- IC
  - digital, 85
  - linear, 85
- ideal ammeter, 39
- ideal op amp, 87
- ideal rectifier, 36
- ideal voltmeter, 39
- impedance
  - input, 45
  - output, 45
    - measuring, 46
- indicators, LED, breadboard, 137
- inductance, 19
- inductive reactance, 19
- inductor, 19
- information
  - analog, 167
  - digital, 167
- input bias current, 94
- input impedance, 45
- input offset voltage, 78, 91
- integrated circuit
  - digital, 85
  - linear, 85
- integrator, 15, 24, 103
  - active, 103, 107
  - op amp, 103, 107
- internal state, 143, 146, 149, 162
- inverter, 60, 141, 149
- inverting amplifier, 58, 88, 168
  - op amp, 88, 168
  
- JFET, 65
- JK flip-flop, 148
- junction diode, 32
- junction, summing, 93, 169
  
- latch, RS, 145, 153
- LED, 60
- LED indicators, breadboard, 137
- level switches, breadboard, 137, 138
- LF398 SHA, 177
- light-emitting diode, *see* LED
- linear region, FET, 68
- logarithmic amplifier, 105
- logarithmic search algorithm, 171

- logic
  - assertion-level, 127, 146
  - digital, 125
  - diode, 131
  - multiplexer, 162
  - negative, 127
  - positive, 127
  - sequential, 143
  - synchronous, 144
- logic function, universal, 140
- logic levels, 125, 126
  - TTL, 126
- logic-level displays, 137
- low (logic level), 126
- machine, state, 143, 162
- magnitude comparator, 142
- margin, noise, 126
- memory
  - random-access, 162
  - word-addressable, 163
- meter, digital, 1
- mho, 48
- MKS, 16
- momentary-contact switch, 153
- monostable, 156, 159
- monostable, 74121, 156, 159
- monostable multivibrator, 156, 159
- MOSFET, 65
- MOSFET logic, 133
- multimeter, 1
- multimeter diode test, 54
- multiplexer, 162
- multiplexer logic, 162
- multivibrator, 120, 143, 156, 159
  - astable, 120, 156
  - bistable, 143, 156
  - monostable, 156, 159
- mux, 162
- NAND, 140
- NAND gate, 140
- negative feedback, 75, 79, 88
- negative logic, 127
- negative-edge-triggered counter, 157
- negative-edge triggering, 147, 149, 157
- noise margin, 126
- noninverting amplifier, op amp, 89
- NPN transistor, 48
- offset voltage, 78
- Ohm's law, 6
- one (logic level), 126
- one-shot, 156, 159
- op amp, 79, 85
  - differentiator, 102
  - golden rules, 90
  - ideal, 87
  - integrator, 103
  - inverting amplifier, 88
  - noninverting amplifier, 89
  - rectifier, 108
  - signal-processing, 101
- op-amp inverting amplifier, 168
- open-collector output, 164
- open-loop, 88, 91, 113
- operational amplifier, *see* op amp
- OR, 142
- OR gate, 142
- oscillation, 115
  - parasitic, 56
- oscillator, square-wave, 117
  - relaxation, 117
  - sine-cosine, 122
- oscilloscope, 8–10
  - cursors, 14
  - measurement, 13
  - triggering, 12
- output impedance, 45
  - measurement of, 46
- output, 3-state, *see* output, three-state
- output, open-collector, 164
- output, three-state, 164
- output, totem-pole, 133, 164
- output, tri-state, *see* output, three-state
- parasitic capacitance, 56
- parasitic oscillation, 56
- passband, 124
- peak-to-peak voltage, 17
- permittivity, 16
- phase shift, 25
- pickup, 115
- pin numbers, DIP IC package, 129
- pinch-off, 66
- pinch-off voltage, FET, 68
- pinout
  - 74121, 159
  - 74150, 162
  - 7489, 163
- PN junction, 32, 47
- PNP transistor, 48
- positive feedback, 113
- positive logic, 127
- positive-edge triggering, 147
- potentiometer, 6, 22, 23
- power supplies, 40
- powering CMOS ICs, 136
- powering TTL ICs, 136
- probe, 10
  - attenuating, 10
  - oscilloscope, 10
- probe compensation adjustment, 10
- propagation delay, 148
  - measurement of, 148
- pull-up resistor, 114, 164
- push-pull buffer, 62
- push-pull driver, 109

- quality factor ( $Q$ ), 124  
 quiescent voltage, 57
- RAM, 162  
   7489, 163  
 random-access memory, *see* RAM  
 RC circuit, 15  
 RC timing network, 159  
 reactance, 19  
   capacitive, 19  
   inductive, 19  
 recording, digital, 177  
 rectification, 31, 36  
 rectifier, 36, 40  
   active, 108  
   full-wave, 43  
   half-wave, 40  
   ideal, 36  
   op amp, 108  
 reference lead, 10  
 register, shift, 181  
 regulator, 40  
 rejection ratio, common-mode, 96  
 relaxation oscillator, 117  
 resistance  
   dynamic, 37, 52, 57  
   static, 37  
 resistor  
   pull-up, 114, 164  
   shunt, 104  
 reverse saturation current, 33, 52  
 reverse-bias, 34  
 ripple counter, 151, 157  
 ripple voltage, 43  
 RS latch, 145, 153
- sample-and-hold, 177  
 saturated switch, 60  
 saturation  
   bipolar-transistor, 59, 60  
   transistor, 68  
 saturation current, 33, 52  
 saturation drain current, FET, 68  
 saturation region, FET, 67  
 saturation voltage, 91  
 Schmitt trigger, 116  
 search algorithm  
   binary, 171  
   logarithmic, 171  
 sequential logic, 143  
 series, 5, 6, 8  
 SHA, 177  
 shift register, 181  
 short circuit, 7, 11  
 shunt resistor, 104  
 signal processing, op amp, 101  
 simple transistor model, 51  
 sine-cosine oscillator, 122  
 slew rate, 87  
 source follower, 71
- SPDT switch, 152  
 speed, transition, 126  
 state, internal, 143, 146, 149, 162  
 state diagram, 143  
 state machine, 143, 162  
 state table, 146  
 static resistance, 37  
 stored charge, 61  
 stray capacitance, 115  
 successive-approximation ADC, 171  
 summing junction, 93, 169  
 switch, 152  
   momentary-contact, 153  
   SPDT, 152  
   level, breadboard, 137, 138  
 switch debouncer, 153  
 synchronous counter, 152, 157  
 synchronous logic, 144
- table, state, 146  
 table, truth, 140, 141, 143, 146  
 tester, equality, 141  
 theorem, DeMorgan's, 141, 146  
 Thévenin equivalent circuit, 45  
 three-state output, 164  
 three-terminal voltage regulators, 45  
 threshold voltage, 113  
 TIL311 display, 158  
 time constant, 24  
 time domain, 15, 102  
 timer, 118, 156, 555  
 timing diagram, 143  
 timing network, RC, 159  
 TO-92 case, 54  
 toggling flip-flop, 148  
 totem-pole output, 133, 164  
 tracking ADC, 170  
 transconductance amplifier, 48  
 transconductance  
   FET, 68  
   transistor, 68  
    $g_m$ , 48  
 transformer, 40  
 transistor, 48  
 transistor, field-effect, 65  
 transistor, junction, 47  
 transistor, simple model, 51  
 transistor action, 48  
 transistor current source, 59  
 transistor model, Ebers-Moll, 52  
 transistor saturation, 68  
 transition speed, 126  
 tri-state, 149, 150  
 tri-state output, *see* output, three-state  
 trigger, Schmitt, 116  
 triggering  
   negative-edge, 147, 149, 157  
   positive-edge, 147  
 true (logic level), 126  
 truth table, 140, 141, 143, 146

Cambridge University Press

0521815363 - Hands-On Electronics: A One-Semester Course for Class Instruction or Self-Study

Daniel M. Kaplan and Christopher G. White

Index

[More information](#)**204****Index**

---

- TTL, 125
- TTL families, 128, 133
- TTL history, 128, 133
- TTL ICs, powering, 136
- TTL logic levels, 126
- two-bit counter, 151, 156
  
- universal logic function, 140
  
- virtual ground, 93, 168
- voltage
  - peak-to-peak, 17
  - quiescent, 57
  - threshold, 113
  - voltage comparator, 113
  - voltage-divider, 15, 22, 23, 26
  - voltage droop, 43
  - voltage follower, 94
  - voltage regulation, 44
  - voltmeter, ideal, 39
  
- word addressing, 163
  
- XOR, 141
- XOR gate, 141
  
- Zener diode, 35, 123
- zero, 126