

Contents

<i>Preface</i>	<i>xiii</i>
1. BASIC ELECTRICAL PRINCIPLE AND COMPONENTS	1-33
1.1 Introduction	1
1.2 Charge	1
1.3 Electric Potential or Voltage	2
1.4 Electric Current	2
1.5 Alternating Current: Amplitude, Frequency and Phase	3
1.6 Ohm's Law: Resistance	4
1.7 Combination of Resistances: Equivalent Resistance	5
1.8 Colour Code of Resistor	9
1.9 Electric Power and Energy	10
1.10 Basic Idea of Capacitor and Capacitance	10
1.11 Basic Idea of Inductor and Inductance	11
Solved Problems	12
Problems to Practice	28
Multiple Choice Questions	32
2. ELECTRICAL CIRCUITS	34-129
2.1 Introduction	34
2.2 Basic Concepts: Electric Circuit, Loop, Mesh etc.	34
2.3 Circuit Components	35
2.4 Star-Delta Conversion	40
2.5 Kirchhoff's Current Law, Kirchhoff's Voltage Law and Their Applications	42
2.6 Superposition Theorem	45
2.7 Thevenin's Theorem	49
2.8 Norton's Theorem	53
2.9 Maximum Power Transfer Theorem	57
2.10 Millman's Theorem	59
2.11 Reciprocity Theorem	60
Solved Problems	61
Problems to Practice	118
Multiple Choice Questions	128

3. ELECTROSTATIC	130-169
3.1 Introduction	130
3.2 Coulomb's Law and Its Application	130
3.3 Different Physical Parameters Related to an Electric Field	132
3.4 Gauss's Law in Free Space	136
3.5 Inter-relation between Gauss's Law and Coulomb's Law	137
3.6 Gauss's Law in Three Dimensional Free Space	139
3.7 Poisson's Equation in Electrostatic Field	139
3.8 Capacitor and Capacitance	140
3.9 Equivalent Capacitor of Parallel and Series Connection	144
3.10 Energy Stored in Capacitor	145
Solved Problems	145
Problems to Practice	164
Multiple Choice Questions	167
4. FUNDAMENTALS OF AC AND AC CIRCUITS	170-262
4.1 Introduction	170
4.2 Quantification of AC: Average Value, RMS Value and Form Factor	171
4.3 Generation of AC Voltage	177
4.4 Transient Response	179
4.5 Phase and Phase Difference	186
4.6 Phasor Representation and Phasor Diagram	188
4.7 AC Transient Response	191
4.8 Steady State Analysis	197
4.9 Wattless (Idle) Current	208
4.10 L-C-R Resonant Circuit (Acceptor Circuit)	209
4.11 Parallel Resonant Circuit (Rejector Circuit)	211
4.12 Power in AC Circuit	213
Solved Problems	214
Problems to Practice	245
Multiple Choice Questions	260
5. MAGNETOSTATIC	263-299
5.1 Introduction	263
5.2 Different Physical Parameters Related to Magnetic Field	263
5.3 Origin of Magnetism: Weber-Ewing Molecular Theory	264
5.4 Biot-Savart's Law	265
5.5 Application of Biot-Savart's Law	266
5.6 Ampere's Circuital Law	269
5.7 Application of Ampere's Law	270
5.8 Magnetization	270
5.9 Demagnetization: Curie Point	272
5.10 Electromagnetic Induction	272

5.11	Application of Faraday's Law	273
5.12	Transformer EMF and Motional EMF	274
5.13	Self-Inductance	275
5.14	Mutual Inductance	276
5.15	Combination of Inductors	277
	Solved Problems	280
	Problems to Practice	293
	Multiple Choice Questions	297
6.	MAGNETIC CIRCUIT	300-331
6.1	Introduction	300
6.2	Concept of Magnetic Flux Flow	300
6.3	Ampere's Law and Magnetic Circuit: MMF	301
6.4	Hopkinson's Law: Reluctance	302
6.5	Analogous Quantity of Magnetic and Electric Circuit	303
6.6	Magnetic Circuit on AC Excitation	306
6.7	Losses in Magnetic Circuit	309
6.8	Energy Stored in a Magnetic Field	312
6.9	Energy Stored in a Solenoid	312
6.10	Lifting Power of an Electromagnet	312
	Solved Problems	313
	Problems to Practice	324
	Multiple Choice Questions	330
7.	THREE PHASE SYSTEM	332-379
7.1	Introduction	332
7.2	Concept of Three Phase Voltage	332
7.3	Generation of Three Phase Voltage	334
7.4	Three Phase Load: Balanced and Unbalanced Three Phase	335
7.5	Phaser Diagram of Three Phase System	336
7.6	Rotating Magnetic Field	336
7.7	Star and Delta Connected Load	339
7.8	Measurement of Power Consumed by a Three Phase Load	343
	Solved Problems	348
	Problems to Practice	374
	Multiple Choice Questions	379
8.	DC MACHINE	380-431
8.1	Introduction	380
8.2	Construction of DC Machine	381
8.3	Fleming's Rule	385
8.4	Commutation	386
8.5	Armature Reaction	390
8.6	Induced EMF in DC Machine	391

x | FUNDAMENTALS OF ELECTRICAL ENGINEERING

8.7	Torque in DC Machine	394
8.8	Types of DC Machines	396
8.9	DC Generator Characteristics	399
8.10	Characteristics of DC Motor	403
8.11	Speed Control of DC Motor	406
8.12	DC Motor Starter	407
8.13	Losses in DC Machine	408
8.14	Efficiency of DC Machine	409
	Solved Problems	409
	Problems to Practice	425
	Multiple Choice Questions	429
9.	TRANSFORMER	432-475
9.1	Introduction	432
9.2	Construction of a Single Phase Transformer	433
9.3	Induced EMF of an Ideal Transformer	437
9.4	Phasor Diagram of an Ideal Transformer	440
9.5	No-Load Operation of a Transformer	440
9.6	On-Load Operation of a Transformer	441
9.7	Phasor Diagram	442
9.8	Equivalent Circuit of a Transformer	445
9.9	Rating of a Transformer	447
9.10	Load Factor	447
9.11	Losses of a Transformer	448
9.12	Efficiency of a Transformer	449
9.13	Voltage Regulation	450
9.14	Test on Single Phase Transformer	452
9.15	Introduction to Three Phase Transformer	453
9.16	Parallel Operation of Transformer	454
9.17	Polarity of a Transformer	455
9.18	Auto Transformer	455
	Solved Problems	456
	Problems to Practice	468
	Multiple Choice Questions	473
10.	THREE PHASE INDUCTION MOTOR	476-516
10.1	Introduction	476
10.2	Relation between Electrical Angle and Mechanical Angle	477
10.3	Synchronous Speed	478
10.4	Construction of Induction Motor	479
10.5	Working Principle of Induction Motor	480
10.6	Slip	481
10.7	Rotor and Stator EMF Equation	482

10.8	Energy Flow and Losses of Induction Motor	484
10.9	Torque Developed and Maximum Torque in Induction Motor	485
10.10	Torque-Slip Characteristic	486
10.11	Starter of Three Phase Induction Motor	489
10.12	Speed Control of Induction Motor	491
10.13	Equivalent Circuit of Induction Motor	493
10.14	Phasor Diagram of Three Phase Induction Motor	494
10.15	Losses and Efficiency of Induction Motor	494
10.16	Tests on Three Phase Induction Motor	495
	Solved Problems	496
	Problems to Practice	507
	Multiple Choice Questions	514
11.	SYNCHRONOUS MACHINE	517-555
11.1	Introduction	517
11.2	Construction of Synchronous Machine	517
11.3	Induced EMF	519
11.4	Pitch Factor	520
11.5	Distribution Factor	521
11.6	Parallel Operation of Synchronous Generator	522
11.7	Voltage Equation and Phasor Diagram of Synchronous Machine	523
	Solved Problems	524
	Problems to Practice	547
	Multiple Choice Questions	555
12.	AN INTRODUCTION TO POWER SYSTEM	556-569
12.1	Introduction	556
12.2	Basic Structure of Power System	556
12.3	Protection in Power System	566
12.4	Single Line Diagram of Power System	568
	Problems to Practice	568
	Multiple Choice Questions	568
13.	MEASUREMENT AND INSTRUMENTATION	570-627
13.1	Necessity of Measurement	570
13.2	Some Definitions and Classification	571
13.3	Errors in Measurement	574
13.4	Different Electro-Mechanical Indicating Instruments	579
13.5	AC Bridge: Measurement of Inductance Capacitance and Frequency	594
13.6	Digital Instrument	597
13.7	Current Transformer and Potential Transformer	598
	Solved Problems	599
	Problems to Practice	619
	Multiple Choice Questions	623

14. BASIC ELECTRICAL TECHNOLOGY	628–639
14.1 Introduction	628
14.2 Cables and Wires	628
14.3 Types of Cables	628
14.4 Battery	630
14.5 Domestic Wiring	631
14.6 Electric Lamps	632
14.7 Domestic Motors	636
14.8 Electric Shock	637
14.9 Earthing	638