

Index

- 2-pi-models, 104
- active cascode, 34
- ADC *see* analog digital converters
- ADC model
 - basic, 196
 - sampling, 199
- Ampere's law, 54, 61, 75, 77
- amplifier stages
 - basic level, 4
 - cascaded, 44
 - higher level, 31
- analog digital converters, x, 195
- architectures
 - ADC, 201
 - PLL, 171
- back of the envelope calculations *see* estimation
 - analysis
- bandwidth
 - estimate, 42
- basic PLL equations, 175
- basis functions, 162
- bipolar, 4
- bit error rate, 39, 41
 - calculation, 38
 - definition, 203
- body effect, 4, 235
- boundary conditions
 - derivation of, 61
- capacitance
 - calculating, 66
 - definition of, 65
 - fringe, 28
 - one dielectric media, first principle calculation, 68
 - simple calculation, 68
 - two dielectric media, first principle calculation, 70
- capacitor
 - circuit element, 67
 - serial formula, 72
- cascode, 21–22, 28, 31, 33
 - active feedback, 33
- CD stage, 7, 10
 - with resistor capacitor ladder load, 16
- CG stage, 5
- characteristic impedance, 107–108, 116
- charge sampling
 - theory, 222
- circuit analysis *see* circuit theory
- circuit design, 30, 49–50, 85, 90, 101
- circuit theory, ix, 51, 109
- CMOS inverter
 - cross-coupled, 25
 - single, 23
- CMOS transistor
 - inherent gain, 14
 - small geometry bandwidth, 10
 - small geometry current, 182
- common drain *see* CD stage
- common gate *see* CG stage
- common source *see* CS stage
- comparator, 34, 41
 - no output load, 40
- comparator design, 45
- conduction current, 54
- conformal coordinate transformation, 95
- conformal transformations, 93, 96
- continuity equation, 54
- convolution theorem, 216, 221
- co-planar wave guides, 103
- Coulomb gauge, 53
- CS stage, 8, 15
- current distribution
 - perfectly conducting ground plane, 87
 - related to inductance, 66
 - resistive ground plane, 89
 - thin conductors, 93
- current mirror, 20
- current sheet over ground plane
 - first principle calculation, 82
- cylindrical symmetry, 2, 58, 74, 76, 85
- Delta gap source, 161
- design examples, 4, 31, 122, 166, 234
- design phase, 3

- differential nonlinearity (DNL), 202
- differential pair, 18
- Dirac delta function
 - definition of, 213
- distortion, 15, 17, 199, 202, 209
- distributed effects, 102

- effective number of bits (ENOB), 203
- effective radius
 - using adjacent circular segments, 126
 - using area equivalence, 127
 - using maximum length scale, 128
- EFIE, 160
- electric field integral equation *see* EFIE
- electrical length, 108–109, 116, 134
- electromagnetism, ix, 50, 101
- estimation analysis, 1
- estimation calculations, ix
- evaluation, 3

- field energy, 63
 - electrical, 63
 - magnetic, 64
- fine tune, ix, 3, 191, 194, 207
- first principles, ix, 68, 85
- five transistor amplifier, 31
- Flash ADC, 201, 206
- foundry supplied inductor libraries, 104
- Fourier transform
 - sample and hold signal, 218
 - track and hold signal, 218
 - track phase*, 217
- Fourier transform, 212
- full scale voltage, 38, 41
- full wave approximation
 - single frequency, 54

- Galerkin's method, 160
- gate impedance, 6–7
- gauge choice, 53
- gauge invariance, 52
- gauge potentials, 52–53, 94
- gauge symmetry, 53
- Gauge theory, 52
- gauge transformation, 53
- Gauss' law, 62–63
 - definition of, 239
- Green's function
 - 1D, 58
- ground planes, 102

- hand calculation *see* estimation analysis
- Helmholz equation, 56–60, 84
- high frequency phenomena, 85
- high speed integrated circuit
 - size of modern, 102
- homogeneous equation, 56

- ideal impulse sampling, 221
- ideal sampling switch, 214
- impressed current, 54
- impulse sampling, 215
- impulse sensitivity function, 187, 189
- inductance
 - calculating, 73
 - definition of*, 65
 - single straight wire, 74
 - single wire over ground plane, first principle calculation, 79
 - two straight wires, first principle calculation, 74
- inductors as circuit elements, 73
- initialization phase
 - comparator, 35, 42
- input impedance, 5–9, 23–25
- input pair, 35, 39, 42, 45, 49
- input stage
 - comparator, 8, 38, 40, 42, 45, 201
 - Flash ADC, 207, 209
- input transistors *see* input pair
- integral nonlinearity (INL), 202
- integrated circuits, 4, 53, 56, 70, 101, 119, 122
- inter symbol interference (ISI) *see* Jitter:inter symbol interference
- interleaving adc, 203
- inductor model including
 - parasitic capacitance and resistance, 135

- jitter, ix, 3, 165–168, 170, 184, 203, 211, 224, 226–231
- jitter, 166, 230
 - anti-correlated, 227
 - correlated, 227
 - data-dependent, 166
 - deterministic jitter, 166
 - duty cycle distortion, 166
 - Gaussian, rms, 166
 - inter symbol interference, 166
 - periodic, 166
 - random, 166
 - uncorrelated, 229
 - uncorrelated bounded, 166
 - vs phasenoise, 167

- KCL *see* Kirchoff's current law
- Kirchoff's current law, 5

- Laplace equation, 93
- lateral skin effect, 97, 100, 137, 148
- LC-VCO, 149, 191
- linearization techniques, 4
- linearize, 2, 4–5, 21, 175
- linewidth, 171
- lithography, 102
- load resistance, 25, 48

- long wavelength
 - approximation, 55
 - simulators, 152
- loop equations, 26
- Lorenz gauge, 53
- machine learning, 104
- magnetic charges, 52
- magnetic field integral equation *see* MFIE
- Matrix equation, 160
- Maxwell's equations, 51, 66–68, 70, 73–74, 85
 - 1D – solution, 56
 - 2D – solution, 58
 - 3D – solution, 59
 - external sources, 54
 - solutions, 56
- metal-insulator-metal capacitor *see* mim capacitor
- metastability, 38
- method of images, 80
- method of moments, 159
- MFIE, 160
- Miller effect, 9, 27–28
- MIM capacitor, 119
- MOM capacitor, 121
- multi-layer ground planes, 103
- narrow-band applications, 8
- negative resistor, 7–8, 16, 185
- noise analysis, 31, 48
- noise optimization, 45
- noise transfer, 20, 31–32, 41, 171, 219
- nonlinear effects, 4
- nonlinear extension, 9, 29
 - CD stage, 10
 - CS stage, 15
- nonideal sampling switch, 219
- Nyquist criterion, 199
- offset, 202
- Ohm's law, 93
- one turn inductor, 129
- output conductance, 12, 14, 31
- Parseval's theorem, 168, 170
 - definition of, 239
- partial inductance, 122–123
- partial inductance of a wire stub pair, 122
- PCB
 - connection to IC, 102
- performance criteria
 - adc, 202
 - PLL, 172
- permeability, 51
- permittivity, 51, 55, 70, 72, 85, 102, 136, 139, 234
- perturbation analysis, 4
- phase locked loop (PLL), ix, 171
- phase noise, 187
- phenomenological model, 135, 138
- pill box, 61
- pi-models, 104
- pipeline converter, 201
- PLL *see* phase locked loop
- Poisson equation, 57, 58
- positive feedback, 38, 43, 184
- potential field, 52, 152
- power, 202
- printed circuit board (PCB), 102
- propagation constant, 106
- propagation delay, 23
- Q - quality factor
 - definition of, 138
- rectangular cross section, 126
- regeneration phase
 - comparator, 37, 42
- regularization theory, 104
- reset, 35, 40–41, 45, 207
- reset phase
 - comparator, 35
- reset switch, 207
- reset switches, 40, 45
- RF performance, 104
- sampling
 - finite pulse width, 222
- sampling rate, 41, 199–201
- saturation, 5, 16, 23, 27–28, 236
- scaling relationships, 42
- self-resonance, 134
- shielding techniques, 1, 101
- sigma-delta converter, 201
- signal integrity, 103
- signal-to-noise and distortion ratio (SNDR), 202
- signal-to-noise ratio
 - definition, 202
- simple straight wire in free space, 74
- simplification, 2
- simulation, 12, 15, 46, 81, 125, 131–132, 134, 137, 151–152, 161
- simulators, 87, 151
 - principles, 151
- single transistor gain stages, 4
- skin depth, 85
- small geometry CMOS, 23, 28, 87, 102, 121
- SNR, 41, 166, 198, 200–203, 206, 208, 227–229, 231
 - improvement using averaging, 200
- S-parameters, 101, 109, 112–114, 116–117
 - definition of, 109
- spurious-free dynamic range, 203
- stability, 176
 - feedback systems, 176
- Stoke's theorem, 61, 76–77
 - definition of, 240
- strong-arm comparator *see* comparator

- substrate resistance, 136
- substrate resistivity, 137, 234
- Successive Approximation Register (SAR), 202
- surface charge, 63
- surface current, 62

- Taylor expansions *see* Taylor Series
- Taylor series, 10
- third harmonic
 - differential pair, 19
- through-silicon-vias (TSV), 104
- time domain, 25, 31, 42, 184, 189, 223
- time evolution, 37
- time-digital converter, 201
- time-interleaved converters, 202
- timescale/s, 27, 31, 35–36, 38, 40–43, 45, 48, 234
- total harmonic distortion (THD), 202
- track and hold*, 216, 218
- transconductance, 32
- transfer function, 10, 15, 17, 25, 29, 171, 175–176, 178, 181–182
- transition frequency, 6
- transmission lines, 101
 - basic theory, 105

- two transistor stages, 18
- two-turn inductor, 129, 134, 137, 144
- two-dimensional solution, 58
- two-pole system, 9, 177

- VCO
 - active design, 193
 - frequency of oscillation, 184
 - performance criteria, 183
 - steady state amplitude, 185
 - tank design, 191
- vector potential, 52, 56, 60, 66, 76–77, 83, 94, 123, 155, 161
- verification, 3
- vias, 103
- voltage controlled oscillator *see* VCO
- voltage field *see* potential field
- voltage sampling theory, 211
- Volterra series, 9
- volume charge, 63
- volume current, 61

- wavelength, 53, 55, 57, 60, 68–69, 84–85, 88, 93–94, 101–102, 108–110, 117, 151–152, 159