

Contents

Preface	<i>page</i> vii
Acknowledgments	xii
1 Introduction	1
1.1 Notations and Terminology	1
1.2 Countable Graphs	4
1.3 0-Graphs	7
1.4 Electrical Networks	9
1.5 Kirchhoff's Laws	12
1.6 Curiouser and Curiouser	13
1.7 Electrical Analogs for Some Differential Equations	20
1.8 The Transient Behavior of Linear RLC Networks	27
2 Infinite-power Regimes	30
2.1 An Example	31
2.2 The Chainlike Structure	32
2.3 Halin's Result for Locally Finite Graphs	35
2.4 An Extension to Countably Infinite Graphs	38
2.5 Limbs	41
2.6 Current Regimes Satisfying Kirchhoff's Current Law	44
2.7 Joints and Chords	46
2.8 The Equations for a Limb Analysis	47
2.9 Chord Dominance	50
2.10 Limb Analysis, Summarized	52
2.11 Nonlinear Networks	53
2.12 A Contraction Mapping Result	55
2.13 A More General Fixed Point Theorem	58
3 Finite-power Regimes: The Linear Case	61
3.1 Flanders' Theorems	62
3.2 Connections at Infinity: 1-Graphs	66
3.3 Existence and Uniqueness	74
3.4 The Validity of Kirchhoff's Laws	80
3.5 A Dual Analysis	83
3.6 Transferring Pure Sources	87
3.7 Networks with Pure Sources	95
3.8 Thomson's Least Power Principle	99
3.9 The Concavity of Driving-point Resistances	100
3.10 Nondisconnectable 0-Tips	103
3.11 Effectively Shorted 0-Tips	105
4 Finite-power Regimes: The Nonlinear Case	108
4.1 Regular Networks	109
4.2 The Fundamental Operator	116
4.3 The Modular Sequence Space l_M	120
4.4 The Space $l_M^\#$	122
4.5 The Space c_M	125

vi	<i>Content</i>	
4.6	Some Uniform-variation Conditions	127
4.7	Current Regimes in I_M	130
4.8	A Minimization Principle	133
5	Transfinite Electrical Networks	139
5.1	p -Graphs	140
5.2	ω -Graphs	146
5.3	Graphs of Still Higher Ranks	149
5.4	(k, q) -Paths and Terminal Behavior	151
5.5	k -Networks	153
6	Cascades	158
6.1	Linear Uniform Cascades	161
6.2	Nonlinear Uniform Cascades	167
6.3	Backward Mappings of the Axes	171
6.4	Trajectories near the Origin	175
6.5	Characteristic Immittances for Nonlinear Uniform Cascades	179
6.6	Nonlinear Uniform Lattice Cascades	186
6.7	Nonuniform Cascades: Infinity Imperceptible	193
6.8	Nonuniform Cascades: Infinity Perceptible	197
6.9	Input–Output Mappings	201
6.10	ω^p -Cascades	204
6.11	Loaded Cascades	209
7	Grids	215
7.1	Laurent Operators and the Fourier-Series Transformation	217
7.2	n -Dimensional Rectangular Grids	220
7.3	A Nodal Analysis for Uniform Grids	223
7.4	One-dimensional Nonuniformity	229
7.5	Solving Grounded Semi-infinite Grids: Infinity Imperceptible	233
7.6	Solving Ungrounded Semi-infinite Grids: Infinity Imperceptible	240
7.7	Semi-infinite Grids: Infinity Perceptible	245
7.8	Forward and Backward Mappings	250
7.9	Solving Semi-infinite Grids: Infinity Perceptible	255
7.10	Transfinite Grids	260
7.11	Grids with Two-dimensionally Transfinite Nonuniformities	266
8	Applications	267
8.1	Surface Operators	268
8.2	Domain Contractions	274
8.3	Random Walks	285
8.4	Operator Networks	290
	Bibliography	294
	Index of Symbols	303
	Index	305