

## Index

- LC* circuit, 113
  - R:2R* ladder, 697–698
  - RLC* circuit, 113–118
    - resonance, 114
  - $R_{ON}$ 
    - analog switch (lab), 490
    - MOSFET (lab), 489
  - $R_{on}$ 
    - analog switch (lab), 490
  - $f_{crossover}$ , 312
  - $h_{fe}$ , 158
  - $r_e$ 
    - ... deriving, 207
  - '311 (lab), 337
  - '555, 341–343
  - .INC file (assembler/compiler), 817
  - .lst file (RIDE assembler/compiler/simulator), 951
  - #344 lamp (lab), 343
  - #47 lamp (lab), 174
  - “WATCH” window
    - RIDE assembler/compiler/simulator, 953
    - “active low”, 522
    - “loop” (program): origin of term, 815
    - “saturation” (FET usage), 500
    - “sticky” flag, 600, 601
  - 1N5294 current-limiting diode, 342
  - 1N5294 current-limiting diode (lab), 213
  - 1N5717 Schottky diode (lab), 135
  - 2's-complement
    - cheap trick to calculate, 816
  - 2N3904 (lab), 169
  - 2N3906 (lab), 271
  - 4046 PLL, 717
  - 74HC00 (lab), 540
  - 74HC14 (lab), 339
  - 74HC175 (lab), 594
  - 74HC4040 (lab), 730
  - 74HC4046 (lab), 730
  - 74HC574 (lab), 728
  - 74HC74 (lab), 588
  - 74HCT139 (lab), 835
  - 74HCT573 (lab), 786
  - 74LS00 (lab), 540
  - 74LS503 (lab), 725
  - 78L05 regulator (lab), 454
  - 8051 controller, 765
  - 8051 port, 770–771
  - 8051
    - left-justify, 917
- pinout (lab), 786
- addressing modes
  - bit operations, 862–864
  - DPTR, 857–858
  - examples (brief), 867–868
  - indirect addressing, 860–861
  - $R_n$ , 859, 860
  - multiple address spaces, 864–868
  - off-chip operations, 857–860
  - on-chip operations, 857
  - portpins vs external buses (examples), 862
- A in feedback: open-loop gain, 396
- AB in feedback: loop gain, 397, 399
- AC/DC (scope input select), 34
- ACC
  - vs “A” SiLabs (lab), 846
- active filter, 354
  - Bessel, 387
  - Bessel (lab), 374
  - Butterworth, 387
  - Butterworth (lab), 374
  - Chebyshev, 387
  - Chebyshev (lab), 374
  - transient response, 388
  - VCVS, 354
- active filter (lab), 373–374
- active low
  - ... in Verilog, 526, 571
  - why prevalent, 529
- active pullup gate output: CMOS (lab);, 545
- active rectifier, 281
- AD558 (lab), 724
- AD7569 (lab), 926
- ADC
  - see “analog ↔ digital conversion”, 701
- ADC
  - SiLabs (lab) , 942–944
- ADC (lab), 725–729
- ADC & DAC to micro
  - modify waveforms
    - lowpass filter, 923–925
    - rectify: full-wave, 922
    - rectify: half-wave, 923
  - number formats, 922
  - reconstruction filter, 917
  - SiLabs
    - left-justify, 917
- ADDC (lab), 841, 854

- adder
  - worked example, 556–559
- address decoding, 675
- address multiplexing (lab), 786
- addressing modes
  - see “8051: addressing modes”, 857
- ADx address/data lines (lab), 786
- ALE (lab), 787
- aliasing, 696, 735, 738–739
- ALU
  - design with gates, 563
  - design with Verilog, 564
  - worked example, 563
- AM radio (lab), 135
- ammeter (lab), 29
- analog
  - contrasted with digital, 513
  - analog ↔ digital conversion
    - R:2R ladder, 697–698
    - ADC designs, 701–712
      - ... compared, 701
      - “flash” or parallel, 701
    - binary search (SAR), 705–707
    - delta-sigma, 706–712
    - dual-slope, 703
    - how delta-sigma high-passes quantization noise, 710–711
    - how delta-sigma low-passes signal, 711
    - oversampling, 709
    - pipelining, 703
    - tracking, 705
  - aliasing, 714
  - DAC designs, 697–701
    - current summing R:2R, 697
    - PWM, 700
    - switched-capacitor, 699
    - thermometer, 697
  - dither, 714
  - quantization error, 694
  - resolution, 694
  - sample and hold, 705
  - sampling artifacts, 712–714
  - sampling rate, 694–697
    - aliasing, 696
  - analog switch
    - application
      - chopper (lab), 491
      - flying capacitor (lab), 493
      - sample-and-hold (lab), 492
      - switched-capacitor filter (lab), 493–495
  - analog to digital conversion
    - ADC designs
      - single-slope, 616
    - AND as “if”, 574
    - AND as Pass/Block\* function, 573
  - assembler directive (RIDE assembler/compiler/simulator), 947
  - assembly language, 813
    - assembler directive, 817
    - bit versus byte operations, 775, 776, 864
  - CALL subroutine, 826, 830
  - stack, 826
  - directives, 817
    - INCLUDE, 817
  - DPTR initialization, 822, 823
  - EQU, 818
  - extending operations beyond 8 bits, 830
  - format, typical, 823
  - INC, 817
  - INCLUDE, 817
  - indirect addressing, 823
  - jump offsets, 815
  - loop in slow motion, 818
  - moving pointer, 959–961
  - MOVX, 823
  - ORG, 817
  - assertion level logic notation, 522–528
  - assign (in Verilog), 1054
  - audio amplifier (LM386), 920
  - B in feedback: fraction fed back, 396
  - ballast resistor., 469
  - bandpass filter (worked example), 103
  - battery backup (lab), 832
  - Bessel filter, 387
  - beta, 158
  - bias current, 288
  - bias divider, 179
  - biasing, 161
    - details, 163
  - binary, 514
  - binary number codes, 518
  - binary numbers
    - hexadecimal notation, 519
    - signed, 518
    - unsigned, 518
  - binary search (lab), 724
  - binary search ADC, 705–707
  - binary search display (lab), 727
  - bipolar transistor, 154
    - four topologies, 167
    - impedance at collector, 167
  - bipolar transistor (defined), 152
  - bit defined, 514
  - bit move
    - using carry flag, 873
  - bit operations
    - bit move, 873
      - external bus, 869–870
      - in C, 873
      - port pins, 870–871
    - bit versus byte operations, 864
  - Black
    - formalizing feedback, 249
  - Black, Harold
    - memoir, 245
  - bleeder resistor, 143
  - blocking capacitor, 74
  - blocking vs non-blocking assignments, 1077–1079
  - Bluetooth, SiLabs (lab) , 989–991
  - Boole, 520–521
  - bootstrap (op-amp input), 397

- BPV11 (lab), 899
- BR\* (lab), 786
- breadboard (use of), 25
- breadboard printed-circuit, microcomputer (lab), 620
- breakpoint
  - SiLabs (lab), 802
  - SiLabs IDE, 806
- BS250 (lab), 271
- BS250P (lab), 453
- BUK9509–40B (lab), 486
- bullet timer (worked), 642
- bus, 648
- bus activity
  - ISA/EISA , 768–770
- Butterworth filter, 387
- C code
  - bit operations, 873
- C language
  - functions as subroutines, 829
- c2 interface, SiLabs (lab), 793–796
- C8051F410
  - pin use, all labs (lab), 796
- C8051F410 (lab), 792
- CA3096 array (lab), 209
- CA3600 (lab), 544
- cache memory, 653
- CALL
  - see “subroutine”, 826
  - SiLabs (lab), 844
- CALL (lab), 842
- capacitance meter (lab), 749–750
- capacitor
  - blocking, 74
  - decoupling, 75
  - dynamic description, 52
  - exponential *RC* charging), 53
  - hydraulic analogy, 52
  - polarized, 85
  - reading value, 85
  - static description, 52
  - tolerance codes, 89
- carrier frequency
  - group audio project, 505
- carry
  - counter carry-out glitch (lab), 630
  - carry (counter), 611
    - carry-out: synchronous, 612–613
  - carry flag
    - for bit move, 873
  - CC\* (lab), 726
- CD standard, 745
- CD4007 (lab), 544
- CE\*, 649
- CEM-1205C lab), 899
- Chebyshev filter, 387
- chopper op-amp, 317
- clamp, diode (lab)
  - see “diode clamp”, 136
- clipping
- differential amplifier, 220
- clock, 579
- CMRR
  - in op-amp (worked example), 240
- CMRR, op-amp from array (lab), 218
- combinational logic, 520
- common emitter amplifier (lab), 174
- common-emitter amplifier
  - ... modest gain, 157
  - bypassed-emitter, 197
  - distortion, 194
    - remedy:  $R_E$ , 195
- common-emitter amplifier (lab), 172
- common-mode amplifier (discrete)
  - common-mode gain, 205
- common-mode gain
  - measuring (lab), 212
- comparator, 320–326
  - ... contrasted with op-amp, 320
  - in SiLabs controller (lab), 897
- digital
  - magnitude (design problem), 560–562
  - worked example, 559
- hysteresis, 324–326
  - AC, 326
  - how much?, 325
  - Woody Allen, 325
  - Schmitt trigger, 324
- comparator (lab), 337–338
- compensation capacitor
  - op-amp (lab), 218
- compliance
  - output voltage, 222
- conditional branch, 874–875
- counter, 583–586
  - 16-bit
    - async load (lab), 622, 625
    - reset, sync (lab), 622
    - sync load (lab), 622
  - 16-bit (lab), 621–626
  - application
    - stopwatch (lab), 631–633
  - $\text{Carry}_{\text{in}}$  &  $\text{Carry}_{\text{out}}$ , 611
  - carry-out glitch (lab), 630
  - cascading, 611
  - load, 614
  - ripple, 583
  - ripple (lab) , 591
  - ripple versus synchronous, 606
  - synchronous, 584–586
  - synchronous (lab) , 591–592
  - synchronous clear, 613
  - counter (lab), 591–592
  - CPLD, 597
  - crossbar (lab), 798
  - crossbar switch
    - SiLabs output port enable, 872
    - SiLabs port enable, 775
  - crossover distortion
    - op-amp remedy, 259
  - crossover frequency, 312
  - crystal oscillator (lab), 788

- CS\*, 649
- current limit
  - op-amp output, 242
- current mirror, 222
  - as load for op-amp first stage, 240
- current source
  - op-amp, 257
  - single-transistor, 155
- current source (lab), 172
- current-hogging, 469
- current-to-voltage converter (op-amp), 258
- D flip flop, 579
- D flip-flop, 579
- D flip-flop (lab), 588–589
- DA (lab), 839, 853
- DAC
  - see “↔ digital conversion: DAC designs”, 697
- DAC
  - SiLabs (lab) , 935–942
- DAC (lab), 724–725
- DAC reconstruction filter, 917
- Darlington
  - switch, applied (worked example), 351
- Darlington transistor pair, 349
- debounce
  - pseudo (lab), 932
  - spst RC debouncer, 873
- debouncer, 577, 582
- debouncer (lab), 592–594
- debug
  - DAC kinks can show wiring errors (lab), 927
  - folded pin, 671
  - oscillation frequency as clue, 673
  - power through I/O pin, 672
- decibel, 64
- decibel: two definitions, 41
- decoder
  - 2-to-4, 553
- decoder
  - I/O (lab), 834
- decoding (address and control), 675
- decompensated op-amp, 384
- decoupling capacitor, 75
- decoupling capacitor (lab), 176
- decoupling of power supply (lab), 176
- decoupling power supplies (lab), 262
- delay loop, Silabs (lab), 801
- delta-sigma ADC, 706–712
- deMorgan, 520
  - theorem, 522
- depletion mode, 498
- DG403 (lab), 489
- DG403 analog switch, 475
- difference amplifier, 189
  - op-amp version, 301
- difference amplifier (discrete), 201–206
  - ... evolves into op-amp, 206
  - design, 204–206
  - differential gain, 205
- differential amplifier, 189
  - clipping, 220
  - op-amp version, 301
- differential amplifier (discrete), 201–206
  - ... evolves into op-amp, 206
  - design, 204–206
  - differential gain, 205
- differential amplifier (lab), 209–213
- differential gain
  - measuring (lab), 213
- differentiator
  - op-amp, 300
  - passive *RC*, 55
- differentiator (lab), 79–80
- Digikey, 463
- digital
  - alternatives to binary, 516
  - binary, 514
  - contrasted with analog, 513
  - resolution, 515
  - why, 514
- digital logic
  - minimizing, 569
- Dilbert, 776
- diode
  - zener, 122
- diode (lab) , 29
- diode circuits, 118
- diode clamp, 119
- diode clamp (lab), 136–137
- diode drop, 119
- DIP package
  - breadboarding, 210
- directives, 817
- discrete transistor (defined), 152
- display board (lab), 627
- distortion
  - differential amplifier, 220–222
  - symmetric, 221
- dropout voltage (lab), 454
- DS89C430 (lab), 785
- DSP, 957
- dual-slope ADC, 703
- dynamic RAM, 653
- dynamic resistance, 122
- E12 resistor values, 38
- EA\* (lab), 786
- Early effect, 224–227
  - calculating  $R_{out}$ , 226
  - emitter resistors as remedy, 227
  - Wilson mirror, 227
- Ebers–Moll, 190
  - $r_e$ , 193
- Ebers–Moll view of transistor, 190
- Ebers–Moll
  - $I_S$ , 192
  - I versus V curve, 192
  - reconciling with  $I_C = \beta \times I_B$ , 201
- edge triggering
  - advantages, 603
  - how implemented, 605

- edge- versus level-sensitive input, 580
- edge-triggering, 579
- electret microphone (lab), 309
- electronic justice, 196
- emitter follower, 157
  - ... as impedance changer, 159
  - clipping, 164
  - input impedance, 162
  - push-pull, 165
- emitter follower (lab), 170–172
- EPROM, 652
- EQU (lab), 850
- exponential
  - charge and discharge, 54
    - estimating, 55
  - function, 54
- $f_{3dB}$ 
  - placing (worked example), 101
- FB73-110 ferrite bead (lab), 376
- feedback
  - ... versus open-loop, 250
  - effect on  $R_{out}$ , 252
  - examples without op-amps, 250
  - generally, in electronics, 249
  - positive, 320
  - quantitative view
    - A, 396
    - B, 396
    - benefit from phase shift, 399–400
    - loop gain, 397, 399
  - the golden rules, 251
- feedthrough, analog switch (lab), 491
- ferrite bead (lab), 376
- FET, 152
  - similarities to bipolar transistors, 466
  - structure, 497
  - virtues, 468
- Field Effect Transistor, 466
- filter
  - software
    - FIR, 957
    - IIR, 956
- filter, DAC reconstruction, 917
- finite state machine, 655
- FIR filter, 957
- Firewire, 973
- flag
  - hardware (lab), 883
  - flag (hardware), 873, 880
  - flash ADC, 701
  - flip flop
    - clock, 579
    - D type, 579
    - dangers
      - slow clock edge, 607
    - debouncer, 577, 582
    - edge- versus level-sensitive input, 580
    - edge-triggering, 579
    - jam clear, 580
    - master-slave, 579
  - setup time, 586
  - shift register, 586
  - SR latch, 576
  - T type
    - built from D, 585
    - transparent latch, 578
  - flip-flop, 575
    - D, 579
    - D type (lab), 588–589
    - debouncer (lab), 592–594
    - divide-by-two (lab), 589
    - do-this/do-that (generalized), 601
    - edge-sensitive “flag”, 600
    - one-shot, synchronous (lab), 595–596, 633
    - pathology: slow clock edge (lab), 589, 590
    - propagation delay (lab), 589
    - setup time, 605
    - shift-register (lab), 594–595
    - SR, 599
    - SR (lab), 588
      - sync set, async clear, 600
      - sync set, sync clear, 601
      - T type, 584
      - T type (lab), 590
  - float
    - function generator common (lab), 211
  - floating logic inputs (lab), 541–543
  - FM demodulation
    - PLL (lab), 732
  - FM demodulator
    - group audio project, 506
  - FM using ‘555
    - see “oscillator...”, 342
  - folded pin, 671
  - follower (op-amp), 252
  - Ford, Henry, 520
  - Fourier (lab), 132
  - Fourier series, 117
    - square wave, 117
  - FPGA, 526, 598
  - frequency compensation (op-amp), 380–384
  - frequency domain (lab), 81
  - FSM, 655
  - full-wave rectifier, 120
  - fuse
    - duration of overload, 126
    - slow-blow, 126
  - GAL, 597
  - gate array, 526
  - glitch (digital), 608
    - asynchronous carry-out, 612
    - redundant cover as remedy, 609
  - GLUEPAL
    - Verilog code (lab), 803
    - pinout (lab), 803
  - GLUEPAL (lab), 781–785
  - golden rules (feedback), 251
  - ground, 6
    - scope probe (optimal), 789
    - two senses, 20

- ground loop, 391–392
- ground noise, 391
- grounded-emitter amplifier, 191, 193–195
- Harvard Class computer, 771
- hazard (digital), 608
- HDL, 1053, 1080
- heat sink
  - gasket, 463
- HFA3096 array (lab), 209
- high-pass filter (lab), 82–83
- hysteresis (lab), 338
- I/O
  - A register, 822
  - 8051, 821
  - DPTR, 821
  - using buses, 820, 821
    - port address, 822
    - waveforms, 824
    - without buses, 821
- I/O decoder (lab), 834
- I/O decoding
  - 8051 “lazy”, 818, 820
- IC current source, 443
  - JFET type, 443
  - LT3092, 443
  - REF200, 443
- ICM7555 (lab), 341
- IF
  - bit test equivalents (lab), 849
- IGBT, 470
- IIR filter, 956
- impedance
  - RC* circuit, 68
    - worst-case, 68
    - ... in a direction, 164
    - ... output, 14
    - capacitor, 59
- impedance relations: a rule of thumb, 21
- INA149 difference amplifier, 276
- INCLUDE
  - (RIDE assembler/compiler/simulator), 947
- INCLUDE (assembler/compiler), 817
- indirect addressing, 823, 860–861
- inductor, 112
- input protection clamp (lab), 542
- instantiation (in Verilog), 1056–1058
- integrator
  - op-amp, 294–299
  - passive *RC*, 57
- integrator (lab), 80
- interfacing
  - ADC & DAC to micro
    - big board, 912
    - SiLabs, 915–916
  - ADC &DAC to micro
    - Big Board, 911
- interfacing among logic families
  - 3V with 5V, 692
  - CMOS can behave like TTL, 690
  - low-voltage (<5V), 692–693
  - TTL to CMOS (5V), 690–691
- interfacing among logic families , 689–693
- interrupt, 829, 906–912
  - on timer overflow, SiLabs (lab), 891
  - SiLabs (lab) , 932–935
    - application examples, 906
    - edge-sensitive, 909
    - enabling, 909
    - implementation, 907–909
    - in C, 911
    - latency, 907
    - priority, 909–910
  - interrupt (lab) , 884–886
  - interrupt priority, SiLabs (lab), 935
  - inverting amplifier (op-amp), 254
  - IR remote (lab), 1016
  - IRLIB9343 (lab), 453
  - IRLZ34 (lab), 486
  - ISA/EISA bus, 766
  - ISA/EISA port, 767–770
  - ISR (lab), 886
  - JFET, 466, 497
    - linear region, 499
  - JFET as Variable Resistance, 499
  - JTAG, 973
  - justification
    - left/right, DAC, SiLabs (lab), 936
  - keypad (lab), 628
  - keypad scan, 1006
  - KiBi, 654
  - Kirchhoff's Laws, 9
  - KRESET\* (lab), 786
  - latched display (lab), 833
  - latency (interrupt), 907
  - LCD
    - interface, 1007
  - lead-lag filter, 720–721
  - LED
    - bi-color (lab), 896
  - left-justify (ADC/DAC), 917
  - LF411 (lab), 262
  - line noise, 390–391
  - little  $r_e$ , 193
  - LM311 (lab), 337
  - LM317, 440
  - LM358 (lab), 308
  - LM385–2.5 (lab), 452
  - LM386, 920
  - LM386 (lab), 931
  - LM4667 (lab), 495
  - LM4667 switching amplifier, 471
  - LM50 temperature sensor, 348
  - LM723 (lab), 452
  - LM741 (lab), 262
  - LM78xx, 439
  - LMC6482 (lab), 453
  - LMC7555 (lab), 341
  - load (counter), 614
  - loader (Dallas micro), 993
    - debugging

- COM port trouble (windows), 1000–1001
- flash error, 999
- USB-to-serial translation , 993–994
- loader program (lab), 976
- LOADER\* (lab), 786
- loading, 14
- logic families, 528
  - TTL and CMOS circuitry, 528
- logic gate
  - active pullup, 533
  - noise immunity
    - differential transmission, 532
    - hysteresis, 514, 531
  - open drain/open collector, 533
  - speed versus power consumption, 535
  - three-state, 535
  - threshold, 529
- logic gates
  - noise margin, 529
- logic probe (lab), 537
- loop gain, 397, 399
- low-pass filter
  - microcontroller version (lab), 931
- low-pass filter (lab), 81–82
- LT1073 regulator (lab), 458
- LT1215 (lab), 378
- LT3092, 443
- LTC1150 (lab), 305
- LVDS, 532
- macrocell, 597, 598
- Mao, Chairman, 901
- masking (software), 875–880
- master–slave flop, 579
- MAX294, 917–919
- MAX294 (lab), 931
- MAX294 frequency response, 747
- memory
  - as data organization, 651
  - RAM (lab), 661–663
- meter movement (analog), 27
- microcomputer
  - ... as state machine, 760
  - address multiplexing (8051), 772
- Big Board lab computer
  - first test program, 815
  - single-step logic, 773
- big-board lab computer
  - first test program, 818
  - single-step logic, 772
- bootstrap startup, 762
- bus activity (ISA/EISA), 768–770
- elements of a computer, 760
  - ... minimal, 760
- Harvard Class vs Von Neumann, 771
- history
  - microcontroller, 759
  - microprocessor, 758
  - pre-microprocessor, 757
- microcontroller
  - ... contrasted with microprocessor, 763
- choosing a controller, 762, 765
- microprocessor
  - ... contrasted with microcontroller, 763
- processor control signals, 765–767
  - 68000 (Motorola), 767
  - 8051, 770
  - address, 767
  - application examples, 767
  - I/O vs memory, 767
  - ISA/EISA bus, 766
  - single-chip controller
    - first test program, 774–776, 818
- microcontroller
  - ... contrasted with microprocessor, 763
  - history, 759
  - low-cost, 759
- microprocessor
  - ... contrasted with microcontroller, 763
  - history, 758
  - Miller effect, 371, 470
  - MJE2955 (lab), 378
  - MJE3055 (lab), 174, 378
  - module (Verilog), 1053
  - MOSFET, 152, 497
    - RON*, 469
    - analog switch, 474–485
      - application: multiplexer, 477
      - application: sample-and-hold, 478–485
      - application: switched cap filter, 477
      - charge injection, 479, 483
      - CMOS, 474
      - imperfections, 475
      - body diode, 468, 474
    - CMOS
      - logic gate, 473
    - IGBT, 470
    - input capacitance, 470
    - logic gate, 473
    - power switch, 469
      - application: switching amplifier, 471
      - paralleling, 469
    - symbols, 467
  - moving pointer, 959–966
    - end tests, 964–966
    - store and playback
      - big-board version, 963
      - BSiLabs version, 964
  - table copy
    - assembly language, 960
    - in C, 961
  - MOVX at Rn, 962
  - MOVX at Rn (lab), 928
  - MOVX RAM, SiLabs(lab), 983
  - multimeter (lab), 27, 29
  - multiplexer
    - decoder included, 551
    - implemented with gates, 553
    - implemented with three-states, 553
    - implemented with transmission gates, 553
  - multiplexing, 550
    - address (lab), 786

- multiplexing
  - LCD data (lab), 840
- multiplier
  - worked example, 563
- MXD1210 (lab), 832
- NAND latch (lab), 588
- negative feedback
  - in ordinary usage, 248–249
- noise
  - “line”, 390–391
  - ground, 393
  - ground loop, 391–392
  - ground noise, 391
  - parasitic oscillation, 394–395
  - power supply (lab), 176–177
  - RF pickup, 390, 393
- non-inverting amplifier (op-amp), 252
- NOSYMBOLS
  - (RIDE assembler/compiler/simulator), 947
- Nyquist sampling theorem, 694
- OE\*, 649
- offset binary, 922
- offset current, 290
- offset voltage ( $V_{OS}$ ), 286
- Ohm’s Law
  - why it holds, 7
- Ohm’s law, 5
- one-shot, synchronous (lab), 595–596, 633
- op-amp
  - stability
    - split feedback (worked example), 403
  - open-collector (lab), 538
  - operational amplifier
    - ... designed from discrete transistors, 206
    - AC amplifier, 301
    - active rectifier, 281
    - amplifier, inverting (lab), 265
    - amplifier, non-inverting (lab), 265
    - amplifier, summing (lab), 266
    - as comparator (lab), 336
    - chopper, 317
    - current source, 257
    - current source (lab), 271–272
    - current-to-voltage converter, 258
    - current-to-voltage converter (lab), 269–271
    - detailed schematic (‘411), 395
    - difference amplifier, 301
    - differential amplifier, 301
    - differentiator, 300
    - differentiator (lab), 306–307
    - feedback generalized, 259
    - finite gain
      - effect of phase shift, 402
    - follower, 252
    - follower (lab), 263
    - frequency compensation, 380–384
      - ... imposes integration, 380–381
      - uncompensated and decompensated op-amps, 384
    - golden rules
      - conditional application, 281
  - when they apply, 256
- imperfections, 284
  - balancing paths for  $I_{bias}$ , 288
  - bias current ( $I_{bias}$ ), 288
  - DC, 284
  - dynamic, 284
  - gain rolloff (GBW product), 290
  - input and output voltage range, 292
  - noise, 292
  - offset current ( $I_{offset}$ ), 290
  - offset voltage, 286
  - output-current limit, 291
  - slew rate, 290
- integrator, 294–299
  - integrator (lab), 303–306
    - offset trim, 304
    - self-trimming op-amp, 305
  - integrator tests op-amp, 298
- inverting amplifier, 254
  - made from transistor array (lab), 214–219
  - non-inverting amplifier, 252
- open-loop (lab), 263
  - phase shifter (lab), 266–267
  - photodetector (lab), 269–271
  - power booster, 258
  - push–pull buffer (lab), 268
  - rail-to-rail, 293
- single-supply AC amplifier (lab), 308–309
  - slew rate (lab), 308
  - source of name, 251
  - specifications, ordinary and premium, 294
  - summing amplifier, 255
  - transresistance amplifier, 258
  - virtual ground, 255
- OR as Set/Pass\* function, 575
- ORG
  - (RIDE assembler/compiler/simulator), 947
- ORG (assembler/compiler), 817
- OS-CON capacitor (lab), 459
- oscillator, 326–335
  - applied as suntan alarm, SiLabs (lab), 899
  - implemented with SiLabs comparator (lab), 897
  - FM using ‘555 (lab), 342
  - IC: ‘555, 329
  - IC: recent, 330
  - relaxation (IC inverter), 328
  - relaxation (op-amp), 327
  - sinusoid: Wien bridge, 331–334
  - triangle (lab), 342
- oscillator (lab)
  - IC oscillator: ‘555, 341–343
  - op-amp relaxation, 338
  - PWM motor drive, 340
  - RC: IC Schmitt trigger, 339–341
  - sinusoid: Wien bridge, 343–344
- oscilloscope
  - probe, 109
- oscilloscope (lab: first view), 32
  - triggering, 32–33
- oscilloscope advice
  - triggering, 1099–1103

- “auto” vs “norm”, 1102
- vertical mode, 1101
- oscilloscope probe
  - compensation, 112
  - output current limit
    - op-amp (lab), 264
  - output impedance, 14
  - overflow (worked), 644
  - oversampling, 709
- PAL, 526, 597
- parasitic oscillation, 394–395
  - discrete follower, 367–371
  - discrete follower (lab), 374–376
  - general remedies, 372
  - generally, 356
  - op-amp
    - capacitive load as problem, 362–365
    - capacitive load: remedy 1, feed back less, 363
    - capacitive load: remedy 2, move feedback, 364
    - capacitive load: remedy 3, split feedback, 364
    - capacitive load: remedy 4, specialized driver, 365
    - frequency compensation as remedy, 359–360
    - gain roll-off as remedy, 361
    - generally, 356–359
    - phase lag as cause, 358
  - op-amps
    - stability criteria, generally, 365–367
  - operational amplifier (lab), 377–379
    - remedy: snubber, 379
    - remedy: split feedback, 379
  - remedy: base resistor (lab), 376
  - remedy: ferrite bead (lab), 376
- parasitic oscillation (lab)
  - comparator, 337
- PCA, SiLabs (lab), 895
- phase margin, 383
- phase shift
  - hiding from it, 60
  - rules of thumb, 69
- phase splitter, 189–190
- phase splitter (worked), 182
- phase-locked loop, 716–722
  - applications, 720
  - FM demodulation (lab), 732
  - loop filter (lab), 730–731
  - phase detector
    - edge-sensitive, 717
    - edge-sensitive compared to XOR, 717
    - XOR, 716
    - XOR (lab), 732
  - stability, 720–722
    - lead-lag filter, 720–721
- phase-locked loop (lab), 729–733
- phasor diagram, 70
- PID
  - ‘I: integral of error (lab), 432
  - controller design, 410
  - D: derivative of error
    - calculating (lab), 429
  - D: derivative of error (lab), 428
- effect of derivative, 415–420
- formal description, 411
- I: integral of error (lab), 430
- integral, 420
- motor control loop, 408
- P: proportional to error (lab), 427–428
- phase margin, 413
- sample applications, 408
- setting D gain, 417
- the problem, 407
- PLD, 526, 597–1079
  - structure, 598–599
- PLL
  - see “phase-locked loop”, 716
- POP
  - SiLabs (lab), 846
- positive feedback
  - hysteresis, 324–326
  - oscillators, 326–335
- potentiometer, 12
  - as variable resistor, 12
  - construction, 13
- power, 4, 8
  - $P = IV$  justified, 9
- power dissipation
  - variable resistor, 459
- power supply
  - filter capacitor, 124
  - fuse, 125
  - split, 120
  - transformer current rating, 125
  - transformer voltage, 123
  - unregulated, 123–126
- power, in resistor, 8
- priority
  - interrupt, natural (lab), 935
- probe
  - oscilloscope, 109
- probe compensation, 112
- program “loop: origin of term, 815
- program microcontroller
  - Dallas 89C430
    - hardware (lab), 1013
  - Dallas DS89C430 (lab), 1012
- programmable logic array, 526
- project
  - examples
    - etch-a-sketch, 1027
    - game: asteroids on scope, 1042
    - game: pacman on scope, 1041
    - inverted pendulum, 1039
    - laser character display, 1025–1026
    - sound source detector, 1026
    - spinning LED display, 1036
    - vehicles, 1036–1039
      - X-Y table, 1028
    - inverted pendulum, 1041
  - projects
    - hardware
      - displays, 1048
      - motors, 1044, 1045

- muscle wire, 1045
- stepper motor drive, 1049–1051
- nitinol actuator, 1045
- software
  - LCD drive, keypad scan, 1052
- transducers
  - accelerometer, 1047
  - color discriminator, 1046
  - force, 1047
  - gyro, 1047
  - infrared, 1046
  - magnetic field, 1047
  - speech recognition, 1048
  - ultrasonic, 1046
- projects (general advice), 1025
- PROM, 652
- propagation delay (lab), 589
- PSEN\* (lab), 786
- PSENDRV\* (lab), 786
- pseudo-static RAM, 653
- PSOC (Cypress), 1023
- pulse duration program (lab), 1018
- pulse-width measuring program (lab), 1014
- pulse-width modulation, 700
- PUSH
  - SiLabs (lab), 846
- push-pull
  - SiLabs port option, 871
- push-pull follower
  - ... simple, 158
- PWM
  - controller hardware, SiLabs (lab) , 894–897
  - configuration, SiLabs (lab), 895
  - see “pulse-width modulation”, 700
- Q, 115–116
- Q (quality factor), 131–133
- QAM, 516
- Quality factor, 115
- quiescent defined, 178
- race (digital), 608
- radio
  - AM demodulation, 127, 130
  - AM receiver, 126–130
- radio (lab)
  - see “AM radio”, 135
- rail-to-rail op-amp, 293
- RAM
  - block diagram, 649
  - synchronous SRAM, 652
  - types: static vs dynamic, 653
  - vs ROM, 652
- RAM (lab), 661–663
- ramp waveform, 53
- RC
  - time constant, 55
- RC circuit
  - impedance, 68
  - worst-case, 68
- reactance, 59
  - capacitor, 59
- reaction timer
  - controller version (lab), 1016
- reaction timer (lab), 750
- rectifier
  - full-wave, 120
  - half-wave, 119
- rectifier, full-wave (lab), 134
- rectifier, half-wave (lab), 133
- redundant cover, 609
- REF200, 443
- REF200 current-source IC, 463
- reflections, 1092
- relaxation: see *oscillator*, 327
- relay, 486
- RESET vector, 815
- RESET51 (lab), 786
- resistance, 7
  - dynamic, 7
  - parallel, 10
  - shortcuts, 11
- resistor
  - “E12” values, 37
  - “ten percent” values, 37
  - carbon composition, 35
  - color code, 36
  - fabrication, 7
  - metal-film, 35
  - power, 38
  - tolerance, 36
- resonance, 114
- resonant *RLC* circuit, 113–118
- resonant circuit (lab), 131–133
- RETI, 910
- RETI (lab), 886
- reverb, 958
- RIDE
  - .LST file, 951
  - “WATCH” window, 953
  - assembler directive, 947
  - simulation, 951–955
- RIDE (assembler/compiler/simulator), 946–955
- ringing, 117
- ringing (lab), 133
- ringing of LC circuit, 138
- ripple counter, 583
  - contrasted with synchronous, 606
- ripple counter (lab), 591
- RLC* circuit
  - ringing, 117
- RLC (lab)
  - see resonant circuit, 131
- ROM
  - varieties: EEPROM, 652
  - varieties: EPROM, 652
  - varieties: Flash, 652
  - vs RAM, 652
- Romeo and Juliet, 574
- Romeo and Juliet , 690
- RS232, 966
- RS232, SiLabs (lab) , 986–989

- sample and hold, 705
- sample-and-hold
  - charge injection, 479, 483
  - errors, 480
- sampling
  - aliasing, 735, 738–739
  - analogy with amplitude modulation, 740–743
  - artifacts of sampling, described in frequency domain, 739
  - filtering artifacts, 735
  - seen as multiplication, 742–743
- sampling rate, 694
- SAR
  - see binary search ADC, 705
- SAR (lab), 724
- saturation (bipolar)
  - effect upon  $R_{in}$ , 199
- saturation voltage (discrete transistor) (lab), 175
- Schmitt trigger, 324
- Schmitt trigger (lab), 338
- scope multiplexer (lab), 752
- self-checking testbench, 1088
- self-checking testbench (in Verilog), 1058–1060
- sequential circuit, 575
- SerDes, 966
- serial buses, 966–974
  - $I^2C$ , 973
    - ... a comparison, 974
    - “one-wire”, 973
  - Firewire and Thunderbolt, 973
  - IR remote, 972
  - JTAG, 973
  - SerDes, 966
  - several serial buses, compared, 973
  - SPI, 969–972
    - UART (RS232), 966
    - USB, 968
  - serial link
    - LCD, 1007
  - servomotor (lab), 981
  - SET\*, RESET\* (lab), 589
  - setup time, 586, 605
  - shadow RAM, 653
  - Shannon
    - see Nyquist sampling theorem, 694
  - shift register, 586
  - shift-register (lab), 594–595
  - simulation
    - RIDE assembler/compiler/simulator, 951–955
    - sinewave generator (lab), 751
    - single-breadboard counter lab, 620
    - single-slope ADC, 616
    - single-step
      - SiLabs IDE, 806
      - slow clock edge (lab), 590
      - slow-blow fuse, 126, 143
      - SPI, 969–972
        - SPI RAM, 1009
        - SPI bus (lab), 979
        - SPI RAM
          - hardware (lab), 1018
        - SPI, SiLabs (lab) , 984
    - split feedback (lab), 379
    - split feedback (worked example), 403
    - split power supply, 120
    - SR flip-flop (lab), 588
    - SR latch, 576
    - SR latch (lab), 588
    - stack, 826
      - for short-term storage, generally, 827
    - state machine, 655–660
      - (lab), 663–669
      - RAM-based (lab), 665–669
    - state machine (in Verilog), 1071
    - static RAM, 653
    - STEP PAL
      - schematic (lab), 803
      - single-step (lab), 787
      - Verilog code (lab), 804
    - STEP PAL (lab) , 787–790
    - stopwatch (lab), 631–633
    - storage scope program (lab), 978
    - subroutine, 826, 830
      - equivalent to function in C, 829
      - SiLabs (lab), 844
      - simulation, 828
    - subroutine (lab), 842
    - summing circuit, 255
    - suntan alarm (lab), 899
    - sweeping frequencies (lab), 81
    - sweeping function generator frequencies, 93
      - analog generator
        - analog scope: timed display, 97
        - analog scope: XY, 95–96
        - digital scope, 97
      - artifacts caused by fast sweep, 96, 98
      - digital generator
        - digital scope, 98
    - switch
      - bipolar transistor, 166
      - switch debouncer, 577, 582
      - switch, bipolar transistor (lab), 174, 176
      - switched-capacitor DAC, 699
      - switching amplifier, 471
      - switching amplifier (lab), 495
      - symbols, descriptive (assembler/compiler), 818
      - SYNC\_OUT (function generator output), 33
      - synchronizer
        - on carry-out (worked), 646
      - synchronizer (lab), 595
      - synchronous
        - meaning, 584
        - synchronous carry
          - for overflow (worked), 645
        - synchronous carry-out, 612
        - synchronous circuit
          - advantages, 603
        - synchronous counter, 584–586
          - contrasted with ripple, 606
        - synchronous counter (lab), 591–592
        - synchronous SRAM, 652
        - T flip-flop, 590

- T network, 297
- T-flop, 584
- temperature effects
  - current mirror, 223
- temperature instability, 196–201
  - remedy
    - $R_E$ , 197
    - compensation with second transistor, 200
    - explicit feedback, 199
  - temperature response (bipolar), 196
- temperature stability
  - diff-amp (worked example), 239
- Terminal (SiLabs utility) (lab), 987, 992
- test loop (lab), 791
- testbench (in Verilog), 1055
- thermal calculation: MOSFET (lab), 486
- thermal runaway
  - op-amp push-pull, 242
- thermally conductive gasket, 463
- Thevenin
  - model, 15
  - resistance, 15
    - shortcut, 16
    - shortcut: justifying, 15
  - voltage, 15
- Thevenin model (lab), 26–27
- three-state, 535
  - buffer keypad (lab), 662
  - where needed, 648
- three-state (lab), 545
- three-state buffer (lab), 545
- Thunderbolt, 973
- time constant, 55
- time constant (lab), 78–79
- time-domain (lab), 78
- timer
  - code, SiLabs (lab), 891, 893
  - timer, 8051 (lab), 980–982
- TIP110 Darlington transistor pair, 349
- tolerance (resistor), 36
- tolerance codes, capacitor, 89
- tracking ADC, 705
- transistor (bipolar)
  - beta, 158–160
  - Early effect, 224–227
    - calculating  $R_{out}$ , 226
    - emitter resistors as remedy, 227
    - limit to amplifier gain, 230
    - remedies, 227–230
    - Wilson mirror, 227
  - first model, 154
  - symbol, 154
  - temperature effects
    - mirror, 223
- transistor pinout (lab)
  - by experiment, 169
- transistor summary
  - Early Effect, 235
  - impedances, common-emitter amp, 234
  - impedances, diff-amp, 234
  - Miller Effect, 235
- switch, 235
- transistor switch
  - bipolar, 166
- transistors (bipolar)
  - ... why they are hard, 189
  - common-emitter amplifier
    - bypassed-emitter, 197
    - Ebers–Moll model, 190
    - effect of saturation upon  $R_{in}$ , 199
    - grounded-emitter amplifier, 193–195
    - phase splitter, 189
    - temperature instability, 196–201
  - transmission gate, 466
- transmission lines, 23, 1089
  - reflections, 1092
  - series termination, 1095
- transparent latch, 578
- transresistance amplifier, 258
- tri-state, 535
- triangle waveform, 53
- truth table, 520
- TTL
  - syncing output from function generator, 33
  - TTL (function generator output), 33
- two's-complement, 518
  - worked example, 555–556
- two's-complement (lab), 841
- UART, 966
- uncompensated op-amp, 384
- universal gate, 521
- USB, 968
- variable resistor, 12
- VCO
  - group audio project, 504, 505
- VCVS (lab), 374
- VCVS filter, 354, 386
- VCVS filter (lab), 373
- Verilog, 526, 527, 571, 1053–1079
  - “always @” form, 1060–1062
  - “case”, 1072
  - “parameter”, 1072
  - behavioral versus structural design, 1064–1065
  - blocking vs non-blocking assignments, 1077–1079
  - case, 1071
  - flip-flop, 1060–1062
  - hierarchical design, 1065–1070
  - instantiation, 1056–1058
  - state machine, 1071
    - bus arbiter example, 1075
  - synchronous carry\_out, 1072
  - template files, 1076
  - testbench, 1055
    - initialize, 1062, 1069
    - self-checking, 1058–1060
    - tabular output, 1057
- verilog
  - schematic views, 1083
  - simulation, 1085
  - simulation procedure, 1087
  - synthesize, 1082

testbench, 1086  
  self-checking, 1088  
VHDL, 526  
virtual ground, 255  
volatility (of memory), 653  
voltage divider, 11  
voltage divider (lab), 26  
voltage regulator  
  317 (adjustable), 441  
  78xx (fixed), 439  
  crowbar (lab), 457  
  crowbar circuit, 444  
  current limit, 436  
  dropout voltage, 437  
  evolving a design , 434–437  
IC regulator  
  adjustable, 440  
  fixed, 439  
LM317 (adjustable), 440  
low-dropout regulator, 438  
stabilization, 436  
switching, 445–450  
  configurations: boost, buck, invert, 446  
  efficiency, 447  
  inverting (lab), 461  
  step-down (“buck”) (lab), 460  
  step-up (“boost”) (lab), 458  
  web applications for design, 449  
Williams, Jim, 450  
switching (lab), 457  
thermal calculation (lab), 454  
thermal design, 441  
three-terminal, adjustable (lab), 456  
three-terminal, fixed (lab), 454–456  
voltage reference IC, 435  
zener, 434  
voltage, defined, 6  
Von Neumann computer, 771  
VP01 (lab), 271, 453  
watch  
  SiLabs IDE, 807  
watchdog (microcontroller), 777  
watchdog timer (lab), 798  
waveform  
  ramp, 53  
  triangle, 53  
WE\*, 649  
Wien bridge, 331  
Wien bridge oscillator (lab), 343–344  
Wilson mirror, 227  
wired OR, 534  
Woody Allen, 325  
worst-case impedance, 68  
XC9572, 1081  
XC9572XL, 1081  
Xilinx, 598  
Xilinx ISE, 1081  
XOR as Invert/Pass\* function, 574  
 $Z_C$ , 60  
zener diode, 122