

## Contents

<i>Preface</i>	<i>page</i> xx
<i>Overview, as the Course begins</i>	xxv
<b>Part I Analog: Passive Devices</b>	<b>1</b>
<b>1N DC Circuits</b>	<b>3</b>
1N.1 Overview	3
1N.2 Three laws	5
1N.3 First application: voltage divider	11
1N.4 Loading, and “output impedance”	14
1N.5 Readings in AoE	24
<b>1L Lab: DC Circuits</b>	<b>25</b>
1L.1 Ohm’s law	25
1L.2 Voltage divider	26
1L.3 Converting a meter movement into a voltmeter and ammeter	27
1L.4 The diode	29
1L.5 $I$ versus $V$ for some mystery boxes	30
1L.6 Oscilloscope and function generator	32
<b>1S Supplementary Notes: Resistors, Voltage, Current</b>	<b>35</b>
1S.1 Reading resistors	35
1S.2 Voltage versus current	38
<b>1W Worked Examples: DC circuits</b>	<b>42</b>
1W.1 Design a voltmeter, current meter	42
1W.2 Resistor power dissipation	44
1W.3 Working around imperfections of instruments	45
1W.4 Thevenin models	47
1W.5 “Looking through” a circuit fragment, and $R_{in}$ , $R_{out}$	48
1W.6 Effects of loading	49
<b>2N RC Circuits</b>	<b>51</b>
2N.1 Capacitors	51
2N.2 Time-domain view of RCs	53
2N.3 Frequency domain view of RCs	58
2N.4 Blocking and decoupling	74

viii	<b>Contents</b>	
	2N.5 A somewhat mathy view of <i>RC</i> filters	76
	2N.6 Readings in AoE	77
<b>2L</b>	<b>Labs: Capacitors</b>	78
	2L.1 Time-domain view	78
	2L.2 Frequency domain view	81
<b>2S</b>	<b>Supplementary Notes: RC Circuits</b>	85
	2S.1 Reading capacitors	85
	2S.2 <i>C</i> notes: trying for an intuitive grip on capacitors' behavior	90
	2S.3 Sweeping frequencies	93
<b>2W</b>	<b>Worked Examples: RC Circuits</b>	100
	2W.1 <i>RC</i> filters	100
	2W.2 <i>RC</i> step response	105
<b>3N</b>	<b>Diode Circuits</b>	108
	3N.1 Overloaded filter: another reason to follow our 10× loading rule	108
	3N.2 Scope probe	109
	3N.3 Inductors	112
	3N.4 <i>LC</i> resonant circuit	113
	3N.5 Diode Circuits	118
	3N.6 The most important diode application: DC from AC	119
	3N.7 The most important diode application: (unregulated-) power supply	123
	3N.8 Radio!	126
	3N.9 Readings in AoE	130
<b>3L</b>	<b>Lab: Diode Circuits</b>	131
	3L.1 <i>LC</i> resonant circuit	131
	3L.2 Half-wave rectifier	133
	3L.3 Full-wave bridge rectifier	134
	3L.4 Design exercise: AM radio receiver (fun!)	135
	3L.5 Signal diodes	136
<b>3S</b>	<b>Supplementary Notes and Jargon: Diode Circuits</b>	138
	3S.1 A puzzle: why <i>LC</i> 's ringing dies away despite Fourier	138
	3S.2 Jargon: passive devices	139
<b>3W</b>	<b>Worked Examples: Diode Circuits</b>	141
	3W.1 Power supply design	141
	3W.2 $Z_{IN}$	144
<b>Part II</b>	<b>Analog: Discrete Transistors</b>	149
<b>4N</b>	<b>Transistors I</b>	151
	4N.1 Overview of Days 4 and 5	151
	4N.2 Preliminary: introductory sketch	154

	Contents	ix
4N.3	The simplest view: forgetting beta	155
4N.4	Add quantitative detail: use beta explicitly	158
4N.5	A strikingly different transistor circuit: the switch	166
4N.6	Recapitulation: the important transistor circuits at a glance	167
4N.7	AoE Reading	168
<b>4L</b>	<b>Lab: Transistors I</b>	169
4L.1	Transistor preliminaries: look at devices out of circuit	169
4L.2	Emitter follower	170
4L.3	Current source	172
4L.4	Common-emitter amplifier	172
4L.5	Transistor switch	174
4L.6	A note on power supply noise	176
<b>4W</b>	<b>Worked Examples: Transistors I</b>	178
4W.1	Emitter follower	178
4W.2	Phase splitter: input and output impedances of a transistor circuit	181
4W.3	Transistor switch	185
<b>5N</b>	<b>Transistors II</b>	188
5N.1	Some novelty, but the earlier view of transistors still holds	188
5N.2	Reviewish: phase splitter	189
5N.3	Another view of transistor behavior: Ebers–Moll	190
5N.4	Complication: distortion in a high-gain amplifier	194
5N.5	Complications: temperature instability	196
5N.6	Reconciling the two views: Ebers–Moll meets $I_C = \beta \times I_B$	201
5N.7	“Difference” or “differential” amplifier	201
5N.8	Postscript: deriving $r_e$	207
5N.9	AoE Reading	208
<b>5L</b>	<b>Lab: Transistors II</b>	209
5L.1	Difference or differential amplifier	209
<b>5S</b>	<b>Supplementary Notes and Jargon: Transistors II</b>	220
5S.1	Two surprises, perhaps, in behavior of differential amp	220
5S.2	Current mirrors; Early effect	222
5S.3	Transistor summary	230
5S.4	Important circuits	232
5S.5	Jargon: bipolar transistors	235
<b>5W</b>	<b>Worked Examples: Transistors II</b>	237
5W.1	High-gain amplifiers	237
5W.2	Differential amplifier	238
5W.3	Op-amp innards: diff-amp within an IC operational amplifier	239

x	<b>Contents</b>	
<b>Part III</b>	<b>Analog: Operational Amplifiers and their Applications</b>	243
<b>6N</b>	<b>Op-amps I</b>	245
	6N.1 Overview of feedback	245
	6N.2 Preliminary: negative feedback as a general notion	248
	6N.3 Feedback in electronics	249
	6N.4 The op-amp golden rules	251
	6N.5 Applications	252
	6N.6 Two amplifiers	252
	6N.7 Inverting amplifier	254
	6N.8 When do the Golden Rules apply?	256
	6N.9 Strange things can be put into feedback loop	259
	6N.10 AoE Reading	261
<b>6L</b>	<b>Lab: Op-Amps I</b>	262
	6L.1 A few preliminaries	262
	6L.2 Open-loop test circuit	263
	6L.3 Close the loop: follower	263
	6L.4 Non-inverting amplifier	265
	6L.5 Inverting amplifier	265
	6L.6 Summing amplifier	266
	6L.7 Design exercise: unity-gain phase shifter	266
	6L.8 Push-pull buffer	268
	6L.9 Current to voltage converter	269
	6L.10 Current source	271
<b>6W</b>	<b>Worked Examples: Op-Amps I</b>	273
	6W.1 Basic difference amp made with an op-amp	273
	6W.2 A more exotic difference amp	276
	6W.3 Problem: odd summing circuit	277
<b>7N</b>	<b>Op-amps II: Departures from Ideal</b>	280
	7N.1 Old: subtler cases, for analysis	281
	7N.2 Op-amp departures from ideal	284
	7N.3 Four more applications	294
	7N.4 Differentiator	300
	7N.5 Op-amp Difference Amplifier	301
	7N.6 AC amplifier: an elegant way to minimize effects of op-amp DC errors	301
	7N.7 AoE Reading	302
<b>7L</b>	<b>Labs: Op-Amps II</b>	303
	7L.1 Integrator	303
	7L.2 Differentiator	306
	7L.3 Slew rate	308
	7L.4 AC amplifier: microphone amplifier	308
<b>7S</b>	<b>Supplementary Notes: Op-Amp Jargon</b>	310

	<b>Contents</b>	xi
<b>7W</b>	<b>Worked Examples: Op-Amps II</b>	311
	7W.1 The problem	311
	7W.2 Op-amp millivoltmeter	314
<b>8N</b>	<b>Op-Amps III: Nice Positive Feedback</b>	319
	8N.1 Useful positive feedback	319
	8N.2 Comparators	320
	8N.3 RC relaxation oscillator	327
	8N.4 Sine oscillator: Wien bridge	331
	8N.5 AoE Reading	335
<b>8L</b>	<b>Lab. Op-Amps III</b>	336
	8L.1 Two comparators	336
	8L.2 Op-amp RC relaxation oscillator	338
	8L.3 Easiest RC oscillator, using IC Schmitt trigger	339
	8L.4 Apply the sawtooth: PWM motor drive	340
	8L.5 IC RC relaxation oscillator: '555	341
	8L.6 '555 for low-frequency frequency modulation ("FM")	342
	8L.7 Sinewave oscillator: Wien bridge	343
<b>8W</b>	<b>Worked Examples: Op-Amp III</b>	345
	8W.1 Schmitt trigger design tips	345
	8W.2 Problem: heater controller	348
<b>9N</b>	<b>Op-Amps IV: Parasitic Oscillations; Active Filter</b>	353
	9N.1 Introduction	353
	9N.2 Active filters	354
	9N.3 Nasty "parasitic" oscillations: the problem, generally	356
	9N.4 Parasitic oscillations in op-amp circuits	356
	9N.5 Op-amp remedies for keeping loops stable	361
	9N.6 A general criterion for stability	365
	9N.7 Parasitic oscillation without op-amps	367
	9N.8 Remedies for parasitic oscillation	370
	9N.9 Recapitulation: to keep circuits quiet...	372
	9N.10 AoE Reading	372
<b>9L</b>	<b>Labs. Op-Amps IV</b>	373
	9L.1 VCVS active filter	373
	9L.2 Discrete transistor follower	374
	9L.3 Op-amp instability: phase shift can make an op-amp oscillate	377
	9L.4 Op-amp with buffer in feedback loop	378
<b>9S</b>	<b>Supplementary Notes. Op-Amps IV</b>	380
	9S.1 Op-amp frequency compensation	380
	9S.2 Active filters: how to improve a simple RC filter	384
	9S.3 Noise: diagnosing fuzz	389
	9S.4 Annotated LF411 op-amp schematic	395
	9S.5 Quantitative effects of feedback	396

xii	<b>Contents</b>	
<b>9W</b>	<b>Worked Examples: Op-Amps IV</b>	401
	9W.1 What all that op-amp gain does for us	401
	9W.2 Stability questions	402
<b>10N</b>	<b>Op-Amps V: PID Motor Control Loop</b>	407
	10N.1 Examples of real problems that call for this remedy	408
	10N.2 The PID motor control loop	408
	10N.3 Designing the controller (custom op-amp)	410
	10N.4 Proportional-only circuit: predicting how much gain the loop can tolerate	412
	10N.5 Derivative, D	415
	10N.6 AoE Reading	420
<b>10L</b>	<b>Lab. Op-Amps V</b>	421
	10L.1 Introduction: why bother with the PID loop?	421
	10L.2 PID motor control	422
	10L.3 Add derivative of the error	428
	10L.4 Add integral	430
	10L.5 Scope images: effect of increasing gain, in P-only loop	432
<b>11N</b>	<b>Voltage Regulators</b>	433
	11N.1 Evolving a regulated power supply	434
	11N.2 Easier: 3-terminal <i>IC</i> regulators	439
	11N.3 Thermal design	441
	11N.4 Current sources	443
	11N.5 Crowbar overvoltage protection	444
	11N.6 A different scheme: switching regulators	445
	11N.7 AoE Readings	450
<b>11L</b>	<b>Lab: Voltage Regulators</b>	451
	11L.1 Linear voltage regulators	451
	11L.2 A switching voltage regulator	457
<b>11W</b>	<b>Worked Examples: Voltage Regulators</b>	462
	11W.1 Choosing a heat sink	462
	11W.2 Applying a current-source IC	463
<b>12N</b>	<b>MOSFET Switches</b>	465
	12N.1 Why we treat FETs as we do	465
	12N.2 Power switching: turning something ON or OFF	469
	12N.3 A power switch application: audio amplifier	471
	12N.4 Logic gates	473
	12N.5 Analog switches	474
	12N.6 Applications	475
	12N.7 Testing a sample-and-hold circuit	480
	12N.8 AoE Reading	485

	<b>Contents</b>	xiii
<b>12L</b>	<b>Lab: MOSFET Switches</b>	486
	12L.1 Power MOSFET	486
	12L.2 Analog switches	489
	12L.3 Switching audio amplifier	495
<b>12S</b>	<b>Supplementary Notes: MOSFET Switches</b>	497
	12S.1 A physical picture	497
<b>13N</b>	<b>Group Audio Project</b>	503
	13N.1 Overview: a day of group effort	503
	13N.2 One concern for everyone: stability	506
	13N.3 Sketchy datasheets for LED and phototransistor	507
<b>13L</b>	<b>Lab: Group Audio Project</b>	508
	13L.1 Typical waveforms	508
	13L.2 Debugging strategies	509
<b>Part IV</b>	<b>Digital: Gates, Flip-Flops, Counters, PLD, Memory</b>	511
<b>14N</b>	<b>Logic Gates</b>	513
	14N.1 Analog versus digital	513
	14N.2 Number codes: Two's-complement	518
	14N.3 Combinational logic	520
	14N.4 The usual way to do digital logic: programmable arrays	526
	14N.5 Gate types: TTL and CMOS	528
	14N.6 Noise immunity	530
	14N.7 More on gate types	533
	14N.8 AoE Reading	535
<b>14L</b>	<b>Lab: Logic Gates</b>	537
	14L.1 Preliminary	537
	14L.2 Input and output characteristics of integrated gates: TTL and CMOS	540
	14L.3 Pathologies	541
	14L.4 Applying IC gates to generate particular logic functions	543
	14L.5 Gate innards; looking within the black box of CMOS logic	544
<b>14S</b>	<b>Supplementary Notes: Digital Jargon</b>	548
<b>14W</b>	<b>Worked Examples: Logic Gates</b>	550
	14W.1 Multiplexing: generic	550
	14W.2 Binary arithmetic	554
<b>15N</b>	<b>Flip-Flops</b>	567
	15N.1 Implementing a combinational function	568
	15N.2 Active-low, again	569
	15N.3 Considering gates as "Do this/do that" functions	573
	15N.4 XOR as Invert/Pass* function	574

xiv	<b>Contents</b>	
	15N.5 OR as Set/Pass* function	575
	15N.6 Sequential circuits generally, and flip-flops	575
	15N.7 Applications: more debouncers	582
	15N.8 Counters	583
	15N.9 Synchronous counters	584
	15N.10 Another flop application: shift-register	586
	15N.11 AoE Reading	587
<b>15L</b>	<b>Lab: Flip-Flops</b>	588
	15L.1 A primitive flip-flop: <i>SR</i> latch	588
	15L.2 <i>D</i> type	588
	15L.3 Counters: ripple and synchronous	591
	15L.4 Switch bounce, and three debouncers	592
	15L.5 Shift register	594
<b>15S</b>	<b>Supplementary Note: Flip-Flops</b>	597
	15S.1 Programmable logic devices	597
	15S.2 Flip-flop tricks	599
<b>16N</b>	<b>Counters</b>	603
	16N.1 Old topics	603
	16N.2 Circuit dangers and anomalies	607
	16N.3 Designing a larger, more versatile counter	610
	16N.4 A recapitulation of useful counter functions	614
	16N.5 Lab 16L's divide-by- <i>N</i> counter	615
	16N.6 Counting as a digital design strategy	616
<b>16L</b>	<b>Lab: Counters</b>	617
	16L.1 A fork in the road: two paths into microcontrollers	617
	16L.2 Counter lab	619
	16L.3 16-bit counter	621
	16L.4 Make horrible music	629
	16L.5 Counter applications: stopwatch	631
<b>16W</b>	<b>Worked Examples: Applications of Counters</b>	634
	16W.1 Modifying count length: strange-modulus counters	634
	16W.2 Using a counter to measure period, thus many possible input quantities	636
	16W.3 Bullet timer	642
<b>17N</b>	<b>Memory</b>	648
	17N.1 Buses	648
	17N.2 Memory	651
	17N.3 State machine: new name for old notion	655
<b>17L</b>	<b>Lab: Memory</b>	661
	17L.1 RAM	661
	17L.2 State machines	663
	17L.3 State machine using a PAL programmed in Verilog	669



	Contents	xv
<b>17S</b>	<b>Supplementary Notes: Digital Debugging and Address Decoding</b>	671
	17S.1 Digital debugging tips	671
	17S.2 Address decoding	675
<b>17W</b>	<b>Worked Examples: Memory</b>	678
	17W.1 A sequential digital lock	678
	17W.2 Solutions	681
<b>Part V</b>	<b>Digital: Analog–Digital, PLL, Digital Project Lab</b>	687
<b>18N</b>	<b>Analog ↔ Digital; PLL</b>	689
	18N.1 Interfacing among logic families	689
	18N.2 Digital ⇔ analog conversion, generally	693
	18N.3 Digital to analog (DAC) methods	697
	18N.4 Analog-to-digital conversion	701
	18N.5 Sampling artifacts	712
	18N.6 Dither	714
	18N.7 Phase-locked loop	716
	18N.8 AoE Reading	723
<b>18L</b>	<b>Lab: Analog ↔ Digital; PLL</b>	724
	18L.1 Analog-to-digital converter	724
	18L.2 Phase-locked loop: frequency multiplier	729
<b>18S</b>	<b>Supplementary Notes: Sampling Rules; Sampling Artifacts</b>	734
	18S.1 What’s in this chapter?	734
	18S.2 General notion: sampling produces predictable artifacts in the sampled data	734
	18S.3 Examples: sampling artifacts in time- and frequency-domains	735
	18S.4 Explanation? The images, intuitively	739
<b>18W</b>	<b>Worked Examples: Analog ↔ Digital</b>	745
	18W.1 ADC	745
	18W.2 Level translator	748
<b>19L</b>	<b>Digital Project Lab</b>	749
	19L.1 A digital project	749
<b>Part VI</b>	<b>Microcontrollers</b>	755
<b>20N</b>	<b>Microprocessors 1</b>	757
	20N.1 Microcomputer basics	757
	20N.2 Elements of a minimal machine	760
	20N.3 Which controller to use?	762
	20N.4 Some possible justifications for the hard work of the big-board path	764
	20N.5 Rediscover the micro’s control signals. . .	765
	20N.6 Some specifics of our lab computer: big-board branch	771
	20N.7 The first day on the SiLab branch	773
	20N.8 AoE Reading	778

xvi	<b>Contents</b>	
<b>20L</b>	<b>Lab: Microprocessors 1</b>	780
	20L.1 Big-board Dallas microcomputer	780
	20L.2 Install the GLUEPAL; wire it partially	781
	20L.3 SiLabs 1: startup	792
<b>20S</b>	<b>Supplementary Notes: Microprocessors 1</b>	803
	20S.1 PAL for microcomputers	803
	20S.2 Note on SiLabs IDE	805
<b>20W</b>	<b>Worked Examples: A Garden of Bugs</b>	809
<b>21N</b>	<b>Microprocessors 2. I/O, First Assembly Language</b>	813
	21N.1 What is assembly language? Why bother with it?	813
	21N.2 Decoding, again	818
	21N.3 Code to use the I/O hardware (big-board branch)	821
	21N.4 Comparing assembly language with C code: keypad-to-display	824
	21N.5 Subroutines: CALL	826
	21N.6 Stretching operations to 16 bits	830
	21N.7 AoE Reading	831
<b>21L</b>	<b>Lab: Microprocessors 2</b>	832
	21L.1 Big-board: I/O. Introduction	832
	21L.2 SiLabs 2: input; byte operations	844
<b>21S</b>	<b>Supplementary Notes: 8051 Addressing Modes</b>	857
	21S.1 Getting familiar with the 8051's addressing modes	857
	21S.2 Some 8051 addressing modes illustrated	867
<b>22N</b>	<b>Micro 3: Bit Operations</b>	869
	22N.1 BIT operations	869
	22N.2 Digression on conditional branching	874
<b>22L</b>	<b>Lab Micro 3. Bit Operations; Timers</b>	881
	22L.1 Big-board lab. Bit operations; interrupt	881
	22L.2 SiLabs 3: Timers; PWM; Comparator	886
<b>22W</b>	<b>Worked Examples. Bit Operations: An Orgy of Error</b>	901
	22W.1 The problem	901
	22W.2 Lots of poor, and one good, solutions	901
	22W.3 Another way to implement this "Ready" key	904
<b>23N</b>	<b>Micro 4: Interrupts; ADC and DAC</b>	905
	23N.1 Big ideas from last time	905
	23N.2 Interrupts	906
	23N.3 Interrupt handling in C	911
	23N.4 Interfacing ADC and DAC to the micro	912

	Contents	xvii
	23N.5 Some details of the ADC/DAC labs	917
	23N.6 Some suggested lab exercises, playing with ADC and DAC	921
<b>23L</b>	<b>Lab Micro 4. Interrupts; ADC and DAC</b>	926
	23L.1 ADC → DAC	926
	23L.2 SiLabs 4: Interrupt; DAC and ADC	931
<b>23S</b>	<b>Supplementary Notes: Micro 4</b>	946
	23S.1 Using the RIDE assembler/compiler and simulator	946
	23S.2 Debugging	951
	23S.3 Waveform processing	955
<b>24N</b>	<b>Micro 5. Moving Pointers, Serial Buses</b>	959
	24N.1 Moving pointers	959
	24N.2 DPTR can be useful for SiLabs '410, too: tables	964
	24N.3 End tests in table operations	964
	24N.4 Some serial buses	966
	24N.5 Readings	974
<b>24L</b>	<b>Lab Micro 5. Moving Pointers, Serial Buses</b>	975
	24L.1 Data table; SPI bus; timers	976
	24L.2 SiLabs 5: serial buses	982
<b>24S</b>	<b>Supplementary Note: Dallas Program Loader</b>	993
	24S.1 Dallas downloader	993
	24S.2 Hardware required	993
	24S.3 Procedure to try the loader: two versions	994
	24S.4 Debugging: LOADER420, in case you can't write to flash	999
	24S.5 Debugging in case of trouble with COM port assignments	1000
<b>24W</b>	<b>Worked Example: Table Copy, Four Ways</b>	1003
	24W.1 Several ways to copy a table	1003
<b>25N</b>	<b>Micro 6: Data Tables</b>	1006
	25N.1 Input and output devices for a microcontroller	1006
	25N.2 Task for big-board users: standalone micro	1008
	25N.3 Task for SiLabs users: off-chip RAM	1009
<b>25L</b>	<b>Lab: Micro 6: Standalone Microcontroller</b>	1012
	25L.1 Hardware alternatives: two ways to program the flash ROM	1012
	25L.2 SiLabs 6: SPI RAM	1018
	25L.3 Appendix: Program Listings	1021
<b>26N</b>	<b>Project Possibilities: Toys in the Attic</b>	1022
	26N.1 One more microcontroller that may interest you	1023
	26N.2 Projects: an invitation and a caution	1025
	26N.3 Some pretty projects	1025

xviii	<b>Contents</b>	
	26N.4 Some other memorable projects	1030
	26N.5 Games	1041
	26N.6 Sensors, actuators, gadgets	1043
	26N.7 Stepper motor drive	1049
	26N.8 Project ideas	1051
	26N.9 Two programs that could be useful: LCD,Keypad	1052
	26N.10 And many examples are shown in AoE	1052
	26N.11 Now go forth	1052
<b>A</b>	<b>A Logic Compiler or HDL: Verilog</b>	1053
	A.1 The form of a Verilog file: design file	1053
	A.2 Schematics can help one to debug	1054
	A.3 The form of a Verilog file: simulation testbench	1055
	A.4 Self-checking testbench	1058
	A.5 Flip-flops in Verilog	1060
	A.6 Behavioral versus structural design description: easy versus hard	1064
	A.7 Verilog allows hierarchical designs	1065
	A.8 A BCD counter	1068
	A.9 Two alternative ways to instantiate a sub-module	1070
	A.10 State machines	1071
	A.11 An instance more appropriate to state form: a bus arbiter	1073
	A.12 Xilinx ISE offers to lead you by the hand	1076
	A.13 Blocking versus non-blocking assignments	1077
<b>B</b>	<b>Using the Xilinx Logic Compiler</b>	1080
	B.1 Xilinx, Verilog, and ABEL: an overview	1080
<b>C</b>	<b>Transmission Lines</b>	1089
	C.1 A topic we have dodged till now	1089
	C.2 A new case: transmission line	1090
	C.3 Reflections	1092
	C.4 But why do we care about reflections?	1094
	C.5 Transmission line effects for sinusoidal signals	1097
<b>D</b>	<b>Scope Advice</b>	1099
	D.1 What we don't intend to tell you	1099
	D.2 What we'd like to tell you	1099
<b>E</b>	<b>Parts List</b>	1105
<b>F</b>	<b>The Big Picture</b>	1113
<b>G</b>	<b>"Where Do I Go to Buy Electronic Goodies?"</b>	1114
<b>H</b>	<b>Programs Available on Website</b>	1116

	<b>Contents</b>	xix
<b>I</b>	<b>Equipment</b>	1119
	I.1 Uses for This List	1119
	I.2 Oscilloscope	1119
	I.3 Function generator	1120
	I.4 Powered breadboard	1120
	I.5 Meters, VOM and DVM	1121
	I.6 Power supply	1121
	I.7 Logic probe	1121
	I.8 Resistor substitution box	1121
	I.9 PLD/FPGA programming pod	1122
	I.10 Hand tools	1122
	I.11 Wire	1122
<b>J</b>	<b>Pinouts</b>	1123
	J.1 Analog	1123
	J.2 Digital	1125
<i>Index</i>		1128