

Contents

Preface	xi
1 Computer Measurement	1
1 Ports and Expansion Slots	1
2 GPIB Standard	2
3 Parallel I/O Ports	3
2 Introduction to Digital Electronics	4
1 Basic Logic Gates	5
2 Integrated Circuits, Breadboarding and Troubleshooting	9
3 Sequential Logic and Digital Clocks	13
4 Flip-flops	16
5 Electrical Properties of TTL Integrated Circuits	22
6 Hexadecimal, Binary and Decimal Numbers	27
7 74192 and 74193 Counters	30
8 74138 Decoder/demultiplexer	37
9 74152 Data Selector/multiplexer	41
10 74373 Latch/buffer and 74244 Buffer	44
11 Conclusions	47
Exercises	47
3 Parallel I/O Ports	52
1 Specifications	52
2 Port Design for the IBM PC Expansion Slot	53
3 Port Design for the Apple II Expansion Slot	63
4 Commercial Parallel I/O Ports	71
5 Software	73
Exercises	83
4 Tutorial on the AD573 ADC	85
1 Operation and Interface	86
2 Software	90
3 Example Application - A Voltmeter	94
4 Troubleshooting Voltmeter Hardware and Software	95
5 Conclusions	98
Exercises	98
5 Tutorial on the 6264 RAM	100
1 Operation	100
2 Address Generator	103
3 Parallel Ports Interface	104

4 Software	109
5 Troubleshooting the Interface and Software	112
6 Example Application - A Digital Recorder	115
7 Troubleshooting the Recorder	125
8 Summary	127
Exercises	127
6 Tutorial on the Intel 8253 PIT	129
1 Basic Operations	129
2 Output Pattern Generation	130
3 Using Counters for Measurement	135
4 Programming, Loading and Reading	137
5 Parallel Ports Interface	142
6 Program, Load and Read Software	143
7 Troubleshooting Hardware and Software	150
8 Example Application - A Scaler	152
9 Troubleshooting the Scaler	158
10 A Potential Fatal Fault	158
Exercises	160
7 Control/Data Interface	162
1 Overview	162
2 PIT Controls	165
3 Memory Controls	174
4 Read ADC Controls	177
5 START/STOP*	179
6 Monitor Inputs	181
7 CDI Circuit and Software	181
8 Construction	189
9 Testing and Troubleshooting	196
Exercises	200
8 ADC Module	203
1 Circuit	203
2 Layout and Components	205
3 Construction	206
4 Testing and Troubleshooting	208
5 Conclusions	209
Exercises	209
9 Comprehensive Measurement System	211
1 Overview	211
2 Counter	213
3 Timer	228
4 Voltage Measurer	235
5 Complete CMS Circuit	250
6 Example of Integrated Measurement	250

7 Construction	257
8 Testing and Troubleshooting	262
9 Conclusions	267
Exercises	268
10 Fast Voltage Measurer	276
1 Introduction	276
2 Memory and Address Generator Circuitry	277
3 Measurement and Storage Circuitry	280
4 Initiation and Termination Circuitry	283
5 Read Memory Circuitry	287
6 Software	290
7 Example Measurement	295
8 Construction	297
9 Testing and Troubleshooting	304
10 Conclusions	308
Exercises	308
Appendix A References	311
Appendix B Vendors	313
Appendix C IC Pin Assignments	314
Appendix D IBM Paralel Ports	319
1 Components and Layout	319
2 Connectors and Cable	320
3 Wiring	323
4 Testing and Troubleshooting	326
Appendix E Apple II Parallel Ports	333
1 Components and Layout	333
2 Connectors and Cable	334
3 Wiring	335
4 Testing and Troubleshooting	337
Appendix F Computer Architecture	344
1 Components	344
2 Memory Write and Read Machine Cycles	346
3 I/O on Computers with Motorola Microprocessors	347
4 I/O on Computers with Intel Microprocessors	348
5 Computer Expansion Slots	349
Index	350