

Index

- 1N4148 diode, 409–414
- 1N5817 Schottky diode, 357–362
- 2N3553 npn transistor, 371–372
- 2N3906 pnp transistor, 373–378
- 2N4124 npn transistor, 379–384

- acoustics, 131
 - L_p (Sound Pressure Level), 134
 - transmission line analogy, 131–134
- active circuit, 142
- active region
 - BJT, 145–146
 - JFET, 249
- admittance, 57
 - normalized, 91
- alternating current (AC), 34
- Ampere's Law, 279
- amplifier, 10
 - audio, 245, 250–253
 - buffer, 18, 178–179
 - Class-A, 156–158, 180
 - Class-B, 180, 193–196
 - Class-C, 180, 182–185
 - Class-D, 188–189
 - Class-E, 190–192
 - Class-F, 192–193
 - common-emitter, 154–155, 182
 - differential, 168–170
 - driver, 18, 175–177
 - emitter follower, 166–168
 - power, 18, 185–188, 199–200
 - source follower, 174–175
- amplitude modulation (AM), 8
- antenna, 305–306
 - dipole, 283, 290–292
 - isotropic, 282
 - monopole (whip), 292–293, 305–306
 - receiving, 283–284
 - transmitting, 282–283
 - whip (monopole), 292–293, 305–306
 - Yagi, 293–294
- antenna gain, 282
- antenna loading, 293
- antenna noise, 266
- antenna theorem, 287–288
- Armstrong, Howard, inventor, 15
- attenuator, 39
 - attenuator noise, 267
- audio amplifier, 245, 250–253
- automatic gain control (AGC), 17, 254–256
- autotransformer, 305
- available power, 39, 85

- bands, frequency, 7
- bandwidth, 13
- base, 143
- base resistance, 161–162
- beacons, radio, 306–308
- beat frequency oscillator (BFO), 16, 239–240
- bipolar junction transistor (BJT), 143–146
 - collection efficiency α , 144
 - current gain β , 144
 - regions of operation, 146
- Bode plot, 252
- bridge (full-wave) rectifier, 35
- brightness B , 288
- broad-band receiver, 231
- buffer amplifier, 18, 178–179
- Burdick, Wayne, designer, xiv, 1, 128
- Butterworth (maximally flat) filter, 97
- bypass capacitor, 178

- call signs, 310–311
- capacitor, 28, 152
- characteristic impedance, 75
- charge-storage delay, 185
- Chebyshev (equal ripple) filter, 97
- Chebyshev polynomial, 98
- Clapp oscillator, 207–210
- Class-A amplifier, 156–158, 180
- Class-B amplifier, 180, 193–196
- Class-C amplifier, 180, 182–185
- Class-D amplifier, 188–189
- Class-E amplifier, 190–191
- Class-F amplifier, 192–193

- Cohn (crystal) filter, 110–111
 collector resistance, 165
 common-collector amplifier (emitter follower), 166–168
 common-emitter amplifier, 154–155, 182
 comparator, 223
 complex numbers, 49
 conductance, 20, 57
 critical angle θ_c , 302
 critical frequency f_c , 299
 crystal, 107–108
 crystal oscillator, 214–217
 current, 4
 current divider, 26
 current mirror, 245–247
 cut-off frequency, 13
 cut-off voltage in a JFET V_c , 171
- D layer in ionosphere, 294–295
 decibels (dB), 10–11
 describing function, 213
 differential amplifier, 168–170
 diode, 33
 pn, 34
 Schottky, 34
 snubber, 34, 47–48
 varactor, 34, 210, 219
 Zener, 34
 dipole antenna, 283, 290–292
 direct-conversion receiver, 13, 226
 direct current (DC), 34
 dispersion, 80
 distributed capacitance, inductance, 72
 driver amplifier, 18, 175–177
 driver transformer, 124–126
 drain, 171
 duty cycle, 193
 dynamic range (DR), 273
- E layer in ionosphere, 294–295
 Early voltage, 165
 effective area A , 284
 effective earth radius (8,500 km), 286–287
 effective length h , 283–284
 emitter degeneration, 162–166, 177–178
 emitter follower, 166–168
 equipment for measurements, 315
 Euler's formula, 53
 EZNEC antenna calculations, 294, 305
- F layers in ionosphere, 294–295
 fading, 261
 field-effect transistor (FET), 170–174, 191
 filter, 12
 band-pass, 12, 104
 band-stop, 104
 Butterworth, 97
 Chebyshev, 97
 Cohn (crystal), 110–111
 equal-ripple, 99
 harmonic, 112–114
 high-pass, 58
 intermediate frequency (IF), 110–111, 114–118
 ladder, 97–99
 low-pass, 12, 57–59
 notch, 89
 radio frequency (RF), 16, 66–68, 126–130
 transmit, 17, 68–70
 filter design, 100
 filter tables, 101
 Fourier coefficients, 329–331
 narrow pulses, 333–334
 rectified cosine, 332–333
 square wave, 331–332
 frequency, 5
 critical f_c , 299
 cut-off, 13
 fundamental, 184
 image, 14, 230
 intermediate (IF), 226
 radio (RF), 13
 resonant, 59, 62
 frequency modulation (FM), 8
 frequency-shift keying (FSK), 9
 Friis formula, 284–285
 full-wave (bridge) rectifier, 35
 fundamental frequency, 184
- gain,
 amplifier, 10–11, 158–159
 antenna, 282
 gain limiting, 211–214, 221–225
 gate, 171
 Gerke, Frederick, 308–309
 Gilbert Cell, 226–228
 ground, 2
- Hajimiri, Ali, 218
 half-wave rectifier, 34
 harmonic filter, 112–114
 harmonics, 184
 heterodyning, 11
- image frequency, 14, 230
 immitance, 101
 impedance, 56
 characteristic, 75
 inverter, 109–110

- normalized, 91
 parallel-to-series conversion, 65–66
 wave, 280
- inductance formulas, 119–120
 inductor, 35
 integrated circuit (IC), 142, 222
 integrator, 58
 interference, 261
 intermediate frequency (IF), 226
 intermodulation, 270–272
 ionograms, 299–300
 ionosphere, 294–297
- Johnson noise, 261, 264–266
 junction field-effect transistor (JFET),
 170–174
 as a variable resistor, 249
- key clicks, 233–236
 keying waveform, 243
 Kirchhoff's laws, 2–5
- L_p (Sound Pressure Level), 134
 ladder filter, 97–99
 large-signal transconductance G_m , 213
 Lee, Tom, 218
 lightning noise, 266
 line-of-sight range, 285–287
 linear region, JFET, 249
 LM386N-1 audio amplifier, 245,
 399–407
 LM393N comparator, 223
 look-back resistance, 26
 loss, 13
 loss resistance R_l , 280
 loudspeakers, 138–140
 lower-sideband receiver, 17
 lumped element, 72
- magnetizing current, 121, 123–124
 masking of sounds, 136–137
 maximum usable frequency (MUF), 301
 Maxwell's equations, 278
 Miller capacitance, 164
 Minimum Detectable Signal (MDS), 262
 Minimum Detectable Intermodulation
 (MDI), 274
 mixer, 11, 226
 Product Detector, 16, 239–241
 RF, 16, 237–239
 transmit, 17, 242–244
 mixer mathematics, 228–229
 modulation, 8
 monopole antenna, 292, 305–306
- Morse, Samuel, inventor, 308
 Morse code, 308–309
 Morse code vocabulary, 312–313
 MOSFET, 191
 muting circuit, 257–258
- Nahin, Paul, author, xiii, 19, 65, 92
 noise, 261
 antenna, 266
 attenuator, 267
 cascading components, 268
 noise bandwidth, 276
 Noise-Equivalent Power (NEP), 262
 noise figure, 269
 noise phasors, 263–264
 noise power density (N), 262
 noise temperature, 265–266
 NorCal 40A transceiver kit, 315
 normalized admittance, 91
 normalized impedance, 91
 Norton equivalent circuit, 23
 Nyquist's noise formula, 264–267
- Ohm's law, 20
 open circuit, 23
 operational amplifier (op amp), 247–249
 golden rules, 248
 oscillation criteria, 204
 oscillator, 14
 beat-frequency (BFO), 16, 239–240
 Clapp, 207–210
 Colpitts family, 207
 crystal, 214–217
 Hartley family, 207
 synthesized, 210
 transmit, 17, 242
 variable-frequency (VFO), 16, 210,
 219–221
 oscillator starting conditions, 210
- parallel resonance, 62, 68–70
 parallel-to-series conversion, 65–66
 pass band, 12
 passive circuit, 142
 peak voltage, 5–6
 phase, 50
 phase noise, 217
 phase-shift keying (PSK), 9
 phasing dots, 121
 phasor, 53
 noise, 263–264
 wave, 77–78
 phon, 134–135
 plane wave, 279
 polarization, 279

- power, 2, 5
 available, 39, 85
 average, 21
 complex (phasor), 63
 in transmission lines, 76–77, 85–86
 reactive, 64
 power amplifier, 18, 185–188, 199–200
 prefixes, 3
 product detector, 239–241
 propagation, 306–308
Puff circuit simulator, 335–354
 artwork, 353
 component sweep, 353
 device file format, 348
 in *Windows*, 336–337
 parts, 345
 time-domain plots, 353
 units in, 346
 push-pull amplifier, 188, 196
- Q (quality factor), 60–61, 63–65, 89–90
- RC circuits, 31, 57
 RL circuits, 37
 radiation resistance R_r , 280
 radio frequency (RF), 13
 radio frequency filter, 16, 66–68
 radio frequency mixer, 237–239
 radio waves, 278–280, 297
 reactance, 56
 receiver
 broad-band, 231
 direct-conversion, 13, 226
 lower-sideband, 17
 superheterodyne, 15, 226
 triple-conversion, 232
 upper-sideband, 17
 receiver-incremental tuning (RIT), 222
 receiver switch, 147, 149–151
 receiving antenna, 283–284
 reciprocity in antennas, 288–290
 rectifier, 34
 half-wave, 34
 full-wave (bridge), 35
 reflection coefficient ρ , 83
 refractive index n , 298
 rejection, 13
 resistance, 20, 56
 resonance,
 parallel, 62, 68–70
 series, 59, 66–68
 transmission line, 86–89, 95–96
 resonant frequency, 59, 62
 reverse active region, BJT, 146
 rms voltages, 137–138
- SA602AN mixer, 214, 237, 415–425
 saturation conductance, resistance, 147
 saturation current, 160
 saturation region
 BJT, 146
 JFET, 249
 scattering parameters, 340–341
 series resonance, 59, 66–68
 short-circuit, 24
 sidetone, 258
 signal-to-noise ratio (SNR), 261–262
 Snell's law, 301
 snubber diode, 34, 47–48
 solar flux, 296
 soldering, 66–67
 solid angles, 281
 Sound Pressure Level L_p , 134
 sounders for telegraphy, 308
 source follower, 174–175
 source resistance, 22
 source (transistor), 171
 sources,
 dependent, 145
 ideal, 23
 speakers, 138–140
 speed of light, 6
 spurious response (“spur”), 230
 steradians, 281
 superheterodyne receiver, 15, 226
 susceptance, 57
 standing wave ratio (SWR), 94, 141
 stop band, 12
 sunspot cycle, 296–297
- telegraphist's equations, 73–74
 temperature coefficients, 210–211
 thermal modeling (transistor), 196–198, 200–203
 thermal voltage V_t , 160
 Thevenin equivalent circuit, 23
 Thevenin's theorem, 26
Titanic, RMS, 1
 transatlantic telegraph cable, 82
 transconductance g_m , 162, 172, 213
 transformer, 120–121
 driver, 124–126
 ideal, 122–123
 impedance, 122–123
 tuned, 124, 126–130

-
- transistor,
 bipolar-junction (BJT), 143–146
 field-effect, (FET), 170–174, 191
transistor switch, 146–149
transmission coefficient τ , 83
transmission line,
 attenuation constant α , 79
 dispersion, 80
 equations, 73–74
 high-resistance approximation, 82
 large-reactance approximation, 81
 load, 90
 phase constant β , 77
 power, 76–77, 85–86
 propagation constant k , 79
 quality factor Q , 89–90
 resonance, 86–89, 95–96
 zero-dispersion condition, 81
transmit filter, 17, 68–70
transmit mixer, 16, 242–244
transmit oscillator, 17, 242
transmit switch, 151–153
transmitting antenna, 282–283
triple conversion receiver, 232
- Uda, Shintaro, 293, 305
units, 3
upper-sideband receiver, 17
- Vail, Alfred, inventor, 308
variable-frequency oscillator (VFO),
 16, 210, 219–221
vendors for parts, 316
virtual ground, 248
voltage, 2
 peak, 5–6
 root-mean-square (rms),
 137–138
voltage divider, 25–26
- wave impedance, 280
wave phasors, 77–78
whip antenna, 292–293, 305–306
- Y factor for measuring noise, 270
Yagi, Hidetsugu, 293
Yagi antenna, 293–294