

Contents

<i>Preface</i>	<i>page</i>	<i>xiii</i>
1	The Wireless World	1
1.1	Kirchhoff's Laws	2
1.2	Frequency	5
1.3	Modulation	8
1.4	Amplifiers	10
1.5	Decibels	10
1.6	Mixers	11
1.7	Filters	12
1.8	Direct-Conversion Receivers	13
1.9	Superheterodyne Receivers	15
1.10	The NorCal 40A	17
2	Components	20
2.1	Resistors	20
2.2	Sources	22
2.3	Dividers	25
2.4	Look-Back Resistance	26
2.5	Capacitors	28
2.6	Energy Storage in Capacitors	30
2.7	RC Circuits	31
2.8	Diodes	33
2.9	Inductors	35
2.10	Energy Storage in Inductors	36
2.11	RL Circuits	37
	PROBLEM 1. Resistors	39
	PROBLEM 2. Sources	40
	PROBLEM 3. Capacitors	41
	PROBLEM 4. Diode Detectors	44
	PROBLEM 5. Inductors	45
	PROBLEM 6. Diode Snubbers	48
3	Phasors	49
3.1	Complex Numbers	49
3.2	Exponential Function	52

3.3	Phasors	53
3.4	Impedance	56
3.5	RC Filters	57
3.6	Series Resonance	59
3.7	Parallel Resonance	62
3.8	Phasor Power	63
	PROBLEM 7. Parallel-to-Series Conversion	65
	PROBLEM 8. Series Resonance	66
	PROBLEM 9. Parallel Resonance	68
4	Transmission Lines	71
4.1	Distributed Capacitance and Inductance	71
4.2	Telegraphist's Equations	73
4.3	Waves	74
4.4	Phasors for Waves	77
4.5	General Lines	78
4.6	Dispersion	80
4.7	Reflections	83
4.8	Available Power	85
4.9	Resonance	86
4.10	Quality Factor	89
4.11	Lines with Loads	90
	PROBLEM 10. Coaxial Cable	92
	PROBLEM 11. Waves	94
	PROBLEM 12. Resonance	95
5	Filters	97
5.1	Ladder Filters	97
5.2	Filter Tables	100
5.3	Examples	101
5.4	Band-Pass Filters	104
5.5	Crystals	107
5.6	Impedance Inverters	109
	PROBLEM 13. Harmonic Filter	112
	PROBLEM 14. IF Filter	114
6	Transformers	119
6.1	Inductance Formulas	119
6.2	Transformers	120
6.3	Ideal Transformers	122
6.4	Magnetizing Current	123
	PROBLEM 15. Driver Transformer	124
	PROBLEM 16. Tuned Transformers	126
7	Acoustics	131
7.1	Equations of Sound	131
7.2	Hearing	134

7.3	Masking	136
7.4	rms Voltages	137
	PROBLEM 17. Tuned Speaker	138
	PROBLEM 18. Acoustic Standing-Wave Ratio	141
8	Transistor Switches	142
8.1	Bipolar Transistors	143
8.2	Transistor Models	144
8.3	Transistor Switches	146
	PROBLEM 19. Receiver Switch	149
	PROBLEM 20. Transmitter Switch	151
9	Transistor Amplifiers	154
9.1	Common-Emitter Amplifier	154
9.2	Maximum Efficiency of Class-A Amplifiers	156
9.3	Amplifier Gain	158
9.4	IV Curves	159
9.5	Base Resistance	161
9.6	Emitter Degeneration	162
9.7	Emitter Follower	166
9.8	Differential Amplifier	168
9.9	Field-Effect Transistors	170
9.10	Source Follower	174
	PROBLEM 21. Driver Amplifier	175
	PROBLEM 22. Emitter Degeneration	177
	PROBLEM 23. Buffer Amplifier	178
10	Power Amplifiers	180
10.1	Class-C Amplifiers	182
10.2	NorCal 40A Power Amplifier	185
10.3	Class D	188
10.4	Class E	190
10.5	Class F	192
10.6	Class B	193
10.7	Thermal Modeling	196
	PROBLEM 24. Power Amplifier	199
	PROBLEM 25. Thermal Modeling	200
11	Oscillators	204
11.1	Criteria for Oscillation	204
11.2	Clapp Oscillator	207
11.3	Variable-Frequency Oscillator	210
11.4	Gain Limiting	211
11.5	Crystal Oscillators	214
11.6	Phase Noise	217
	PROBLEM 26. VFO	219
	PROBLEM 27. Gain Limiting	221

× CONTENTS

12	Mixers	226
	12.1 Gilbert Cell	226
	12.2 Mixer Mathematics	228
	12.3 Spurious Responses	230
	12.4 Broad-Band Receivers	231
	12.5 Key Clicks	233
	PROBLEM 28. RF Mixer	237
	PROBLEM 29. Product Detector	239
	PROBLEM 30. Transmit Mixer	242
13	Audio Circuits	245
	13.1 Audio Amplifier	245
	13.2 Op Amps	247
	13.3 JFETs as Variable Resistors	249
	PROBLEM 31. Audio Amplifier	250
	PROBLEM 32. Automatic Gain Control	254
	PROBLEM 33. Alignment	256
14	Noise and Intermodulation	261
	14.1 Noise	261
	14.2 Noise Phasors	263
	14.3 Nyquist's Formula	264
	14.4 Attenuator Noise	267
	14.5 Cascading Components	268
	14.6 Measuring Noise	270
	14.7 Intermodulation	270
	14.8 Dynamic Range	273
	PROBLEM 34. Receiver Response	274
	PROBLEM 35. Intermodulation	276
	PROBLEM 36. Demonstration	277
15	Antennas and Propagation	278
	15.1 Radio Waves	278
	15.2 Impedance	280
	15.3 Directions and Solid Angles	281
	15.4 Transmitting Antennas	282
	15.5 Receiving Antennas	283
	15.6 Friis Formula	284
	15.7 Antenna Theorem	287
	15.8 Reciprocity	288
	15.9 Dipoles	290
	15.10 Whip Antennas	292
	15.11 Ionosphere	294
	15.12 Radio Waves in the Ionosphere	297
	15.13 Critical Frequency	299
	15.14 Maximum Usable Frequency	301

	CONTENTS	xi
PROBLEM 37. Antennas	305	
PROBLEM 38. Propagation	306	
PROBLEM 39. Listening	308	
A Equipment and Parts	315	
A.1 Equipment	315	
A.2 Vendors	316	
A.3 Parts	316	
B Fourier Series	329	
B.1 Fourier Coefficients	329	
B.2 Square Wave	331	
B.3 Rectified Cosine	332	
B.4 Narrow Pulses	333	
C Puff 2.1	335	
C.1 Windows	336	
C.2 Getting Started	337	
C.3 Scattering Parameters	340	
C.4 Examples	341	
C.5 Parts Window	344	
C.6 Layout Window	349	
C.7 Board Window	351	
C.8 Plot Window	352	
C.9 Component Sweep	353	
D Component Data	355	
Table D.1. Resistors, inductors and capacitors	356	
Table D.2. Iron and ferrite cores	356	
1N5817 Schottky barrier rectifier	357	
MVAM108 silicon tuning diode	363	
P2N2222A general purpose npn silicon transistor	365	
2N3553 2.5-W high-frequency npn silicon transistor	371	
2N3906 general purpose pnp silicon transistor	373	
2N4124 general purpose npn silicon transistor	379	
J309 n-channel VHF/UHF JFET	385	
MC78L08AC three-terminal low-current, positive-voltage regulator	391	
LM386N-1 National Semiconductor low-voltage audio power amplifier	399	
1N4148 high-speed diode	408	
SA602AN double-balanced mixer and oscillator	415	
<i>Index</i>	427	