

Contents

<i>List of figures</i>	<i>page xi</i>
<i>List of tables</i>	xv
<i>About the authors</i>	xvi
<i>To the Reader</i>	xvii
<i>Acknowledgments</i>	xviii
<i>Introduction</i>	xix

1	Equipment familiarization: multimeter, breadboard, and oscilloscope	1
1.1	Multimeter	1
1.2	Breadboard	2
1.2.1	Measuring voltage	4
1.2.2	Measuring current; resistance and Ohm's law	5
1.2.3	Measuring resistance	8
1.3	Oscilloscope	8
1.3.1	Probes and probe test	10
1.3.2	Display	11
1.3.3	Vertical controls	11
1.3.4	Horizontal sweep	12
1.3.5	Triggering	12
1.3.6	Additional features	13
2	RC circuits	15
2.1	Review of capacitors	15
2.1.1	Use of capacitors; review of AC circuits	17
2.1.2	Types and values of capacitors	19

vi	Contents	
	2.2 Review of current, voltage, and power	20
	2.2.1 Destructive demonstration of resistor power rating	21
	2.3 Potentiometer as voltage divider	22
	2.3.1 DC voltage divider	23
	2.3.2 AC voltage divider	23
	2.4 <i>RC</i> circuit	24
	2.5 <i>RC</i> circuit as integrator	24
	2.6 Low-pass filter	25
	2.7 <i>RC</i> circuit as differentiator	27
	2.8 High-pass filter	28
	2.9 Summary of high- and low-pass filters	28
3	Diodes	31
	3.1 Semiconductor basics	31
	3.2 Types of diodes	35
	3.3 Rectification	36
	3.4 Diode action – a more sophisticated view	37
	3.5 Measuring the diode characteristic	38
	3.6 Exploring rectification	40
	3.7 Input and output impedance	45
4	Bipolar transistors	47
	4.1 Bipolar-junction-transistor basics	47
	4.1.1 Basic definitions	50
	4.1.2 Simplest way to analyze transistor circuits	51
	4.1.3 Ebers–Moll transistor model	52
	4.2 Experiments	54
	4.2.1 Checking transistors with a meter	54
	4.2.2 Emitter follower	55
	4.2.3 Common-emitter amplifier	57
	4.2.4 Collector as current source	59
	4.2.5 Transistor switch	60
	4.3 Additional exercises	61
	4.3.1 Darlington connection	61

vii	Contents	
	4.3.2 Push–pull driver	62
	4.3.3 Common-base amplifier	63
5	Transistors II: FETs	65
	5.1 Field-effect transistors	65
	5.1.1 FET characteristics	66
	5.1.2 Modeling FET action	68
	5.2 Exercises	69
	5.2.1 FET characteristics	69
	5.2.2 FET current source	70
	5.2.3 Source follower	71
	5.2.4 JFET amplifier	73
6	Transistors III: differential amplifier	75
	6.1 Differential amplifier	75
	6.1.1 Operating principle	76
	6.1.2 Expected differential gain	76
	6.1.3 Measuring the differential gain	77
	6.1.4 Input offset voltage	78
	6.1.5 Common-mode gain	78
	6.2 Op amps and their building blocks	79
	6.2.1 Current mirror	79
	6.2.2 Differential amplifier with current-source loads	80
	6.2.3 Improved current mirror	82
	6.2.4 Wilson current mirror	82
7	Introduction to operational amplifiers	85
	7.1 The 741 operational amplifier	85
	7.1.1 741 pinout and power connections	86
	7.1.2 An ideal op amp	87
	7.1.3 Gain of inverting and noninverting amplifiers	88
	7.1.4 Op amp ‘golden rules’	90
	7.1.5 The nonideal op amp	90

viii	Contents	
	7.2 Experiments	91
	7.2.1 Testing open-loop gain	91
	7.2.2 Inverting amplifier	92
	7.2.3 Noninverting amplifier	93
	7.2.4 Voltage follower	94
	7.2.5 Difference amplifier	95
	7.3 Additional experiments	97
	7.3.1 Current source	97
	7.3.2 Noninverting summing amp with difference amplifier	98
8	More op amp applications	101
	8.1 Op amp signal processing	101
	8.1.1 Differentiator	102
	8.1.2 Integrator	103
	8.1.3 Logarithmic and exponential amplifiers	105
	8.2 Experiments	106
	8.2.1 Differential and integral amplifiers	106
	8.2.2 Logarithmic and exponential amplifiers	108
	8.2.3 Op amp active rectifier	108
	8.2.4 Op amp with push–pull power driver	109
	8.3 Additional exercises	111
9	Comparators and oscillators	113
	9.1 Experiments	113
	9.1.1 Op amp as comparator	113
	9.1.2 Unintentional feedback: oscillation	115
	9.1.3 Intentional positive feedback: Schmitt trigger	116
	9.1.4 <i>RC</i> relaxation oscillator	117
	9.1.5 555 timer IC	118
	9.2 Additional experiments	121
	9.2.1 Alarm!	121
	9.2.2 Sine/cosine oscillator	122
	9.2.3 Active bandpass filter	123

Cambridge University Press

0521815363 - Hands-On Electronics: A One-Semester Course for Class Instruction or Self-Study

Daniel M. Kaplan and Christopher G. White

Table of Contents

[More information](#)

ix	Contents	
10	Combinational logic	125
	10.1 Digital logic basics	125
	10.1.1 Logic levels	126
	10.1.2 Logic families and history	127
	10.1.3 Logic gates	129
	10.1.4 Summary of Boolean algebra	130
	10.2 CMOS and TTL compared	131
	10.2.1 Diode logic	131
	10.2.2 Transistor–transistor logic (TTL)	132
	10.2.3 Complementary MOSFET logic (CMOS)	133
	10.2.4 Powering TTL and TTL-compatible integrated circuits	136
	10.3 Experiments	137
	10.3.1 LED logic indicators and level switches	137
	10.3.2 MOSFETs	138
	10.3.3 CMOS NAND gate	140
	10.3.4 Using NANDs to implement other logic functions	140
	10.3.5 TTL quad XOR gate	141
	10.4 Additional exercises	142
	10.4.1 7485 4-bit magnitude comparator	142
11	Flip-flops: saving a logic state	143
	11.1 General comments	144
	11.1.1 Schematics	144
	11.1.2 Breadboard layout	144
	11.1.3 Synchronous logic	144
	11.1.4 Timing diagrams	144
	11.2 Flip-flop basics	145
	11.2.1 Simple RS latch	145
	11.2.2 D-type flip-flop	147
	11.3 JK flip-flop	148
	11.4 Tri-state outputs	149

Cambridge University Press

0521815363 - Hands-On Electronics: A One-Semester Course for Class Instruction or Self-Study

Daniel M. Kaplan and Christopher G. White

Table of Contents

[More information](#)

x	Contents	
	11.5 Flip-flop applications	151
	11.5.1 Divide-by-four from JK flip-flops	151
	11.5.2 Contact bounce	152
	11.5.3 Electronic coin toss	153
12	Monostables, counters, multiplexers, and RAM	155
	12.1 Multivibrators	156
	12.2 Counters	156
	12.3 Experiments	157
	12.3.1 Bi-quinary ripple counter	157
	12.3.2 Monostable multivibrator	159
	12.3.3 Multiplexer and finite-state machine	162
	12.3.4 RAM	162
13	Digital ↔ analog conversion	167
	13.1 A simple D/A converter fabricated from familiar chips	168
	13.2 Tracking ADC	170
	13.3 080x ADC and DAC chips	171
	13.3.1 Successive-approximation ADC	171
	13.4 Additional exercises	177
	13.4.1 Digital recording	177
	13.4.2 Successive-approximation ADC built from components	178
	<i>Further reading</i>	183
	<i>Appendix A Equipment and supplies</i>	185
	<i>Appendix B Common abbreviations and circuit symbols</i>	188
	<i>Appendix C RC circuits: frequency-domain analysis</i>	191
	<i>Appendix D Pinouts</i>	194
	<i>Glossary of basic electrical and electronic terms</i>	197
	<i>Index</i>	199