

Contents

| | | |
|----------|--|-----------|
| | <i>List of figures</i> | page xi |
| | <i>Preface</i> | xxi |
| | <i>Acknowledgements</i> | xxii |
| 1 | Basic concepts | 1 |
| | 1.1 Radio waves | 1 |
| | 1.2 Noise | 9 |
| | 1.3 Sensitivity and selectivity | 13 |
| | 1.4 Non-linearity in RF systems | 14 |
| | 1.5 Digital modulation | 19 |
| | 1.6 Spread spectrum systems | 20 |
| | 1.7 Cellular radio | 23 |
| | 1.8 Radar systems | 24 |
| 2 | Frequency selective circuits and matching | 28 |
| | 2.1 Series resonant circuits | 28 |
| | 2.2 Parallel resonant circuits | 33 |
| | 2.3 Inductive transformers | 34 |
| | 2.4 Tuned transformers | 36 |
| | 2.5 Capacitive transformers | 37 |
| | 2.6 L-network matching | 38 |
| | 2.7 π - and T-networks | 39 |
| | 2.8 Matching examples | 41 |
| | 2.9 Component reality | 44 |
| 3 | Active devices and amplifiers | 49 |
| | 3.1 The semiconductor diode | 49 |
| | 3.2 Bipolar junction transistors | 50 |

| | | |
|-------------|---|------------|
| viii | Contents | |
| | 3.3 The Miller effect and BJT amplifiers | 57 |
| | 3.4 Differential amplifiers | 64 |
| | 3.5 Feedback | 67 |
| | 3.6 Field-effect transistors | 71 |
| | 3.7 FET amplifiers | 76 |
| | 3.8 Amplifier noise | 82 |
| 4 | Mixers, modulators and demodulators | 86 |
| | 4.1 Diode mixers | 86 |
| | 4.2 Transistor mixers | 89 |
| | 4.3 Transconductance mixers | 93 |
| | 4.4 Amplitude modulation | 95 |
| | 4.5 Angle modulation | 101 |
| | 4.6 Gain and amplitude control | 103 |
| | 4.7 A simple receiver design | 105 |
| 5 | Oscillators and phase locked loops | 108 |
| | 5.1 Feedback | 108 |
| | 5.2 The Colpitts oscillator | 109 |
| | 5.3 Stability and phase noise in oscillators | 117 |
| | 5.4 Voltage controlled oscillators | 120 |
| | 5.5 Negative resistance approach to oscillators | 121 |
| | 5.6 Phase locked loops | 123 |
| | 5.7 Analysis of a phase locked loop | 123 |
| | 5.8 Phase locked loop components | 125 |
| | 5.9 Phase locked loop applications | 127 |
| 6 | Transmission lines and scattering matrices | 132 |
| | 6.1 The transmission line model | 132 |
| | 6.2 Time-harmonic variations | 135 |
| | 6.3 Real transmission lines | 139 |
| | 6.4 Impedance transformation | 142 |
| | 6.5 Reflection coefficients | 145 |
| | 6.6 S parameters | 148 |
| | 6.7 S parameter amplifier design | 154 |
| | 6.8 The measurement of S parameters | 161 |

| ix | Contents | |
|-----------|---|------------|
| | 6.9 Some useful multiport networks | 162 |
| | 6.10 Reflection coefficient approach to microwave oscillators | 166 |
| 7 | Power amplifiers | 171 |
| | 7.1 Class A | 171 |
| | 7.2 Class B | 173 |
| | 7.3 Class C | 176 |
| | 7.4 Class E | 178 |
| | 7.5 A design example | 179 |
| | 7.6 Transmission line transformers | 181 |
| 8 | Filters | 187 |
| | 8.1 Filter characteristics | 187 |
| | 8.2 Low- and high-pass filters | 191 |
| | 8.3 Band-pass filters | 194 |
| | 8.4 Conversion of filters to microstrip form | 196 |
| 9 | Electromagnetic waves | 204 |
| | 9.1 Maxwell's equations | 204 |
| | 9.2 Power flow | 206 |
| | 9.3 Electromagnetic waves | 206 |
| | 9.4 Oblique incidence | 215 |
| | 9.5 Guided wave propagation | 218 |
| | 9.6 Wave sources | 224 |
| 10 | Antennas | 228 |
| | 10.1 Dipole antennas | 228 |
| | 10.2 Effective length and gain | 235 |
| | 10.3 The monopole antenna | 238 |
| | 10.4 Feeding an antenna | 243 |
| | 10.5 Array antennas | 247 |
| | 10.6 Travelling wave antennas | 258 |
| | 10.7 Aperture antennas | 260 |
| | 10.8 Patch antennas | 261 |

| | | |
|-----------|--|------------|
| x | Contents | |
| <hr/> | | |
| 11 | Propagation | 266 |
| | 11.1 Reciprocity theorem | 266 |
| | 11.2 Some consequences of reciprocity | 269 |
| | 11.3 Line-of-sight propagation and reflections | 271 |
| | 11.4 Diffraction | 275 |
| | 11.5 Refraction | 277 |
| | 11.6 Ground wave propagation | 286 |
| | 11.7 Propagation by scattering | 287 |
| <hr/> | | |
| 12 | Digital techniques in radio | 293 |
| | 12.1 The processing of digitised signals | 293 |
| | 12.2 Analogue-to-digital conversion | 298 |
| | 12.3 Digital receivers | 301 |
| | 12.4 Direct digital synthesis | 305 |
| | <i>Index</i> | 307 |

Figures

| | | |
|------|--|---------------|
| 1.1 | Radiation of a radial pulse. | <i>page</i> 2 |
| 1.2 | Electromagnetic field generated by a system of accelerating charge. | 3 |
| 1.3 | Development of oscillating dipole field. | 4 |
| 1.4 | A dipole antenna and its gain pattern. | 5 |
| 1.5 | Circuit model of a transmit system. | 6 |
| 1.6 | Conventions for effective length. | 6 |
| 1.7 | A dipole antenna used to collect energy from an electromagnetic wave. | 7 |
| 1.8 | Circuit model of receive system. | 7 |
| 1.9 | Reciprocity principle. | 8 |
| 1.10 | Transmit/receive system. | 8 |
| 1.11 | Noise sources. | 9 |
| 1.12 | Typical antenna noise temperatures for a dipole and a variety of sources. | 10 |
| 1.13 | Cascaded amplifiers. | 12 |
| 1.14 | Measurement of noise figure using matched sources at different temperatures. | 13 |
| 1.15 | Simple receiver architecture. | 14 |
| 1.16 | Superheterodyne receiver. | 14 |
| 1.17 | Set-up for measuring third-order intercept point. | 17 |
| 1.18 | Graph depicting the third-order intercept point and 1 dB compression point. | 18 |
| 1.19 | A direct conversion receiver together with the performance of its individual stages. | 18 |
| 1.20 | Formation of a spread baseband signal. | 21 |
| 1.21 | A simple DSSS transmitter. | 22 |
| 1.22 | A simple DSSS receiver. | 22 |
| 1.23 | A cellular radio system. | 23 |
| 1.24 | A general radar configuration. | 25 |
| 1.25 | Moving target. | 26 |
| 2.1 | Series resonant circuit. | 29 |
| 2.2 | Transient response. | 30 |

xii **List of figures**

| | | |
|------|--|----|
| 2.3 | Behaviour of transfer function around resonance. | 31 |
| 2.4 | Series resonant circuit with non-ideal source. | 32 |
| 2.5 | Notch filter example. | 32 |
| 2.6 | Parallel resonant circuit. | 33 |
| 2.7 | Transformer conventions. | 34 |
| 2.8 | Ideal transformer. | 35 |
| 2.9 | Non-ideal transformer. | 35 |
| 2.10 | Tuned transformer. | 36 |
| 2.11 | Model of tuned transformer. | 36 |
| 2.12 | Capacitive transformer. | 37 |
| 2.13 | Resonant capacitive transformer. | 37 |
| 2.14 | L matching network. | 38 |
| 2.15 | π -network. | 40 |
| 2.16 | Analysis of π -network. | 40 |
| 2.17 | T-network. | 40 |
| 2.18 | Analysis of a T-network. | 41 |
| 2.19 | L-network example. | 42 |
| 2.20 | π -network example. | 42 |
| 2.21 | Analysis of π -network example. | 43 |
| 2.22 | Final π -network. | 43 |
| 2.23 | Single layer solenoid and spiral inductor. | 44 |
| 2.24 | Toroidal inductor and realistic inductor model. | 45 |
| 2.25 | Toroidal transformer and circuit model. | 46 |
| 2.26 | Parallel plate and parallel wire capacitors. | 47 |
| 2.27 | High frequency circuit models of realistic resistors and capacitors. | 47 |
| 3.1 | Junction diode. | 50 |
| 3.2 | High frequency model of a diode. | 50 |
| 3.3 | Bipolar junction transistor (BJT). | 51 |
| 3.4 | Typical BJT characteristics. | 51 |
| 3.5 | BJT load line. | 52 |
| 3.6 | Typical bias circuit. | 53 |
| 3.7 | Alternative bias circuits for a BJT common-emitter amplifier. | 54 |
| 3.8 | A common-emitter amplifier. | 54 |
| 3.9 | Simple BJT models. | 55 |
| 3.10 | Small signal model of common-emitter amplifier. | 55 |
| 3.11 | High frequency BJT model. | 56 |
| 3.12 | Alternative bias circuits for a BJT common-emitter amplifier. | 56 |
| 3.13 | Feedback amplifier and Miller equivalent. | 57 |
| 3.14 | Common-emitter amplifier model. | 58 |
| 3.15 | Miller transformed model. | 58 |
| 3.16 | A more complete BJT model. | 59 |

xiii **List of figures**

| | | |
|------|---|----|
| 3.17 | A common-base amplifier. | 61 |
| 3.18 | Common-base amplifier model. | 61 |
| 3.19 | The cascode amplifier. | 62 |
| 3.20 | The emitter follower amplifier. | 63 |
| 3.21 | Emitter follower amplifier model. | 63 |
| 3.22 | A BJT differential amplifier. | 65 |
| 3.23 | Differential amplifier with current source. | 66 |
| 3.24 | A current mirror ($I_0 = (V_{CC} - V_{BE})/R$ and $V_{BE} \approx 0.7\text{ V}$). | 66 |
| 3.25 | Active loads. | 67 |
| 3.26 | Differential amplifier with active loads. | 67 |
| 3.27 | A high frequency amplifier. | 68 |
| 3.28 | A feedback system. | 68 |
| 3.29 | BJT amplifier with feedback. | 69 |
| 3.30 | The calculation of resistances for bandwidth calculations. | 70 |
| 3.31 | The n-channel junction field-effect transistor (JFET). | 71 |
| 3.32 | The n-channel enhancement MOSFET (nMOS). | 72 |
| 3.33 | The p-channel enhancement MOSFET (pMOS). | 72 |
| 3.34 | Typical FET characteristics. | 73 |
| 3.35 | Typical $I_D - V_{GS}$ curves for (a) a JFET, (b) an nMOS enhancement FET and (c) a pMOS enhancement FET. | 73 |
| 3.36 | Bias configuration and bias spread characteristics. | 74 |
| 3.37 | FET load line. | 74 |
| 3.38 | Alternative biasing for a JFET. | 75 |
| 3.39 | Low frequency FET model. | 75 |
| 3.40 | Common-source amplifier. | 76 |
| 3.41 | Model of an FET device at RF frequencies. | 77 |
| 3.42 | Common-gate amplifier. | 79 |
| 3.43 | FET cascode amplifier. | 79 |
| 3.44 | Dual-gate MOSFET amplifier. | 80 |
| 3.45 | Source follower amplifier. | 81 |
| 3.46 | A CMOS differential amplifier. | 81 |
| 3.47 | FET active loads. | 82 |
| 3.48 | Amplifier with noise model. | 82 |
| 3.49 | Circuit of d.c.-coupled amplifier for Question 4. | 84 |
| 3.50 | An FET model that is appropriate at very high frequencies. | 84 |
| 4.1 | Diode mixer. | 87 |
| 4.2 | Balanced mixer based on a diode pair. | 88 |
| 4.3 | Diode ring mixer. | 88 |
| 4.4 | A typical single FET mixer. | 89 |
| 4.5 | Dual-gate MOSFET mixer. | 91 |
| 4.6 | BJT mixer. | 91 |

xiv **List of figures**

| | | |
|------|---|-----|
| 4.7 | Alternative BJT mixer. | 92 |
| 4.8 | A basic transconductance mixer. | 93 |
| 4.9 | Gilbert cell mixer. | 94 |
| 4.10 | Simple AM transmitter. | 95 |
| 4.11 | Simple AM detector. | 96 |
| 4.12 | Synchronous detector. | 96 |
| 4.13 | Sideband structure. | 97 |
| 4.14 | Simple SSB transmitter. | 97 |
| 4.15 | Variable frequency SSB transmitter. | 98 |
| 4.16 | Phasing SSB generation. | 98 |
| 4.17 | Analysis of the phasing technique. | 99 |
| 4.18 | Phasing SSB demodulation. | 100 |
| 4.19 | An RC network 90° phase shifter. | 100 |
| 4.20 | Traditional SSB receiver. | 100 |
| 4.21 | Phase modulator. | 102 |
| 4.22 | Simple FM demodulation. | 102 |
| 4.23 | Detector frequency response. | 103 |
| 4.24 | Automatic gain control. | 104 |
| 4.25 | Filter and amplifier for AGC. | 104 |
| 4.26 | Limiting amplifier. | 105 |
| 4.27 | A simple direct conversion receiver. | 105 |
| 4.28 | Modern form of DC receiver. | 106 |
| 5.1 | General feedback system. | 109 |
| 5.2 | Colpitts oscillator. | 110 |
| 5.3 | Simple model of Colpitts oscillator. | 110 |
| 5.4 | FET Colpitts with bias circuits. | 111 |
| 5.5 | General Colpitts oscillator. | 111 |
| 5.6 | Clapp and Hartley feedback circuits. | 112 |
| 5.7 | FET differential oscillator. | 112 |
| 5.8 | The drain current for a Colpitts oscillator. | 114 |
| 5.9 | Alternative Colpitts oscillator. | 114 |
| 5.10 | Source follower amplifier. | 115 |
| 5.11 | Simplified Colpitts oscillator model. | 115 |
| 5.12 | An FET Colpitts oscillator that allows output to be taken from the drain. | 116 |
| 5.13 | Oscillator with series LCR feedback. | 117 |
| 5.14 | Phase noise. | 118 |
| 5.15 | Illustration of reciprocal mixing. | 119 |
| 5.16 | Crystal resonator model. | 120 |
| 5.17 | Crystal Colpitts oscillator. | 120 |
| 5.18 | A Colpitts VCO. | 121 |

| xv | List of figures | |
|------|--|-----|
| 5.19 | Gunn diode. | 121 |
| 5.20 | Oscillator based on the Gunn diode. | 122 |
| 5.21 | Negative resistance circuit based on an FET. | 122 |
| 5.22 | General phase locked loop. | 123 |
| 5.23 | Response of a phase locked loop to a step change in reference phase. | 125 |
| 5.24 | Phase comparator. | 126 |
| 5.25 | Loop filter. | 126 |
| 5.26 | Phase/frequency detector based on D flip-flops and a charge pump. | 127 |
| 5.27 | Signal levels in the phase/frequency detector. | 128 |
| 5.28 | A simple FET PLL. | 129 |
| 5.29 | Phase locked loop FM demodulator. | 129 |
| 5.30 | Phase locked loop AM detector. | 129 |
| 5.31 | Frequency synthesiser. | 129 |
| 5.32 | Frequency dividers based on D flip-flops. | 130 |
| 6.1 | Coaxial and twin parallel wire transmission lines. | 133 |
| 6.2 | Lumped component model of transmission line. | 133 |
| 6.3 | Propagation on a transmission line with resistive load. | 135 |
| 6.4 | Terminated transmission line. | 136 |
| 6.5 | The input impedance of a loaded line ($Z_{in} = R_{in} + X_{in}$). | 138 |
| 6.6 | Microstrip transmission line. | 140 |
| 6.7 | Realistic model of transmission line. | 141 |
| 6.8 | The short-circuited line. | 142 |
| 6.9 | The open-circuited line. | 143 |
| 6.10 | The $\lambda/4$ transformer. | 143 |
| 6.11 | Stub matching. | 144 |
| 6.12 | Replacing the stub by a lumped component. | 144 |
| 6.13 | Matching example. | 145 |
| 6.14 | Reflection coefficient description of a one-port network. | 146 |
| 6.15 | A complex tuned circuit and associated Smith chart. | 147 |
| 6.16 | Smith charts. | 147 |
| 6.17 | Source and load connected by a transmission line. | 147 |
| 6.18 | S matrix description of two-port network. | 149 |
| 6.19 | Z matrix description of two-port network. | 149 |
| 6.20 | Symmetric T-network example. | 150 |
| 6.21 | Configuration for the derivation of S parameters. | 151 |
| 6.22 | A simple two-port model of an FET. | 152 |
| 6.23 | General amplifier with source and load. | 154 |
| 6.24 | Transistor amplifier. | 154 |
| 6.25 | Smith chart representation of amplifier stability. | 157 |
| 6.26 | Final amplifier design. | 160 |
| 6.27 | A simple directional coupler. | 161 |

xvi **List of figures**

| | | |
|------|--|-----|
| 6.28 | Set-up for the measurement of S parameters. | 162 |
| 6.29 | Microstrip form of Wilkinson power divider. | 162 |
| 6.30 | Microstrip form of directional coupler. | 163 |
| 6.31 | Analysis of microstrip coupler in terms of even and odd modes. | 164 |
| 6.32 | A branch line quadrature hybrid. | 165 |
| 6.33 | A microwave mixer that is based on a 90° hybrid and diode pair. | 165 |
| 6.34 | Microstrip circulator with application. | 166 |
| 6.35 | Amplifier configuration. | 167 |
| 6.36 | An FET negative resistance oscillator. | 167 |
| 6.37 | Model of FET negative resistance generator. | 168 |
| 6.38 | Microstrip implementation of a negative resistance oscillator. | 168 |
| 6.39 | Circuit for Smith chart example in Question 5. | 169 |
| 6.40 | Circuits for two-port S matrix calculations in Question 6. | 169 |
| 7.1 | Basic power amplifier circuit. | 172 |
| 7.2 | Class A operation. | 172 |
| 7.3 | Class B operation. | 174 |
| 7.4 | Push-pull class B amplifier. | 175 |
| 7.5 | A bias circuit for class B operation. | 176 |
| 7.6 | Class C amplifier. | 177 |
| 7.7 | Class E amplifier. | 179 |
| 7.8 | Power amplifier example. | 180 |
| 7.9 | Design of an output matching network. | 180 |
| 7.10 | Input matching network. | 181 |
| 7.11 | Transmission line transformer model. | 182 |
| 7.12 | Twisted pair transmission line. | 183 |
| 7.13 | Practical transformer. | 183 |
| 7.14 | 4:1 transformer. | 184 |
| 7.15 | 9:1 transformer. | 184 |
| 7.16 | Power combiner. | 184 |
| 7.17 | A 1:1 BALUN. | 185 |
| 8.1 | Ideal filters. | 188 |
| 8.2 | A simple low-pass filter. | 188 |
| 8.3 | A simple high-pass filter. | 188 |
| 8.4 | Two-pole filter example. | 189 |
| 8.5 | Transducer gain for two-pole filter. | 189 |
| 8.6 | Typical low-pass filter characteristics. | 190 |
| 8.7 | Comparison of Butterworth and Chebyshev filters. | 191 |
| 8.8 | Low-pass Butterworth filter characteristics. | 191 |
| 8.9 | Low-pass filters for $K = 1$ and $K = 2$. | 192 |
| 8.10 | Low-pass filters for $K = 3$ and $K = 5$. | 192 |
| 8.11 | Alternative low-pass Butterworth configurations. | 193 |

xvii **List of figures**

| | | |
|------|---|-----|
| 8.12 | High-pass filters for $K = 1$ and $K = 2$. | 194 |
| 8.13 | High-pass filters for $K = 3$ and $K = 5$. | 194 |
| 8.14 | High-pass filter characteristics. | 195 |
| 8.15 | Band-pass filter derived from a low-pass filter. | 195 |
| 8.16 | Transformation of filter characteristics. | 195 |
| 8.17 | Circuit with three-element filter. | 197 |
| 8.18 | Correspondence between lumped components and transmission lines. | 197 |
| 8.19 | Basic three-element filter. | 197 |
| 8.20 | Some of Kuroda's identities. | 198 |
| 8.21 | Filter with transmission line extensions. | 199 |
| 8.22 | Filter after application of Kuroda identities. | 199 |
| 8.23 | Transmission line realisation. | 199 |
| 8.24 | Prototype lumped component filter. | 199 |
| 8.25 | Prototype transmission line filter. | 200 |
| 8.26 | Final transmission line filter. | 200 |
| 8.27 | Microstrip realisation of the filter. | 201 |
| 8.28 | Simple parallel microstrip filter. | 201 |
| 8.29 | Parallel microstrip filter. | 202 |
| 9.1 | A plane electromagnetic pulse. | 208 |
| 9.2 | The decomposition of linear polarisation into circularly polarised modes. | 210 |
| 9.3 | Dispersion of pulses. | 211 |
| 9.4 | Group speed for a simple two-component signal. | 212 |
| 9.5 | Reflection and transmission at a plane interface. | 212 |
| 9.6 | Transmission through a screen. | 213 |
| 9.7 | Attenuation in a current carrying conductor. | 215 |
| 9.8 | The skin effect on a wire conductor. | 215 |
| 9.9 | Oblique incidence of plane waves. | 216 |
| 9.10 | Coaxial waveguide. | 218 |
| 9.11 | Microstrip geometry and fields. | 219 |
| 9.12 | Hollow rectangular waveguide. | 219 |
| 9.13 | Rectangular cavities with loop and probe coupling. | 222 |
| 9.14 | Dominant modes in rectangular and circular hollow waveguides. | 222 |
| 9.15 | High Q bandstop microstrip formed with dielectric resonator. | 223 |
| 9.16 | High stability oscillator that uses a dielectric resonator. | 223 |
| 9.17 | Field zones in relation to the radiating sources. | 225 |
| 10.1 | A snapshot of the electric field near a dipole. | 229 |
| 10.2 | Circuit model of antenna with transmission line. | 229 |
| 10.3 | The distribution of current on dipole antennas. | 230 |
| 10.4 | Half-wave dipole represented as a series of ideal dipoles. | 230 |
| 10.5 | Dipole and coordinate system. | 231 |

xviii **List of figures**

| | | |
|-------|---|-----|
| 10.6 | The folded dipole. | 233 |
| 10.7 | Magnetic dipole antenna and practical realisation. | 234 |
| 10.8 | Biconical and bow tie dipoles. | 235 |
| 10.9 | Gain surface of a short dipole. | 237 |
| 10.10 | Gain of a short dipole in a cross-section through the dipole axis. | 238 |
| 10.11 | Gain pattern of a half wavelength dipole. | 239 |
| 10.12 | Gain pattern of a $5/4$ wavelength dipole. | 239 |
| 10.13 | Image current concept. | 240 |
| 10.14 | Connection between monopole and dipole antennas. | 240 |
| 10.15 | Shortening a monopole antenna. | 241 |
| 10.16 | Broadband conical and discone antennas. | 241 |
| 10.17 | Ground reflections from a dipole antenna element. | 242 |
| 10.18 | The effect of a finitely conducting plane. | 242 |
| 10.19 | Antennas located over a lossy plane. | 243 |
| 10.20 | Matching a short monopole to a standard load. | 244 |
| 10.21 | A balanced antenna when fed by (a) balanced and (b) unbalanced transmission lines. | 245 |
| 10.22 | Dipoles with coaxial feeds. | 246 |
| 10.23 | A half-wave dipole with offset feed. | 246 |
| 10.24 | A pair of phased dipoles. | 247 |
| 10.25 | Gain pattern of two dipoles in broadside configuration. | 248 |
| 10.26 | Gain pattern of two dipoles in endfire configuration. | 249 |
| 10.27 | Gain pattern of dipoles with 90° phasing and $\lambda/4$ spacing ($f = 150$ MHz). | 250 |
| 10.28 | The mutual impedance of half-wave dipoles in parallel and collinear configurations. | 250 |
| 10.29 | Gain pattern of five dipoles in broadside configuration. | 251 |
| 10.30 | A five-element array of dipoles. | 251 |
| 10.31 | Vertical pattern of broadside configuration. | 252 |
| 10.32 | Gain pattern of five dipoles in endfire configuration. | 253 |
| 10.33 | Gain pattern of five endfire dipoles with reduced spacing and phase increment. | 253 |
| 10.34 | Array factors for linear arrays with equally spaced elements. | 255 |
| 10.35 | Log periodic dipole antenna. | 255 |
| 10.36 | Typical gain pattern of an LPDA in a plane perpendicular to the antenna. | 256 |
| 10.37 | Typical gain pattern in the plane of the LPDA. | 256 |
| 10.38 | A general Yagi–Uda parasitic array antenna. | 257 |
| 10.39 | Beverage travelling wave antenna. | 258 |
| 10.40 | Helical antenna construction and gain. | 259 |
| 10.41 | Waveguide antenna and analysis. | 260 |

xix **List of figures**

| | | |
|-------|--|-----|
| 10.42 | A horn antenna and a reflector antenna. | 262 |
| 10.43 | Electric field between plates at resonance. | 262 |
| 10.44 | A practical patch antenna with microstrip feed. | 263 |
| 11.1 | The excitation of a waveguide. | 268 |
| 11.2 | Interaction of two antennas. | 270 |
| 11.3 | Communication system with two stations. | 271 |
| 11.4 | Propagation with ground reflections. | 272 |
| 11.5 | Propagation through an urban environment. | 273 |
| 11.6 | Propagation over a stretch of water. | 274 |
| 11.7 | Diffraction propagation over a building. | 275 |
| 11.8 | Huygen's principle and diffraction over a screen. | 276 |
| 11.9 | Propagation obscured by a screen. | 276 |
| 11.10 | The refraction of a plane wave at a plane interface. | 278 |
| 11.11 | The direction of propagation with refraction by a continuously varying medium. | 278 |
| 11.12 | Propagation through a spatially varying medium. | 280 |
| 11.13 | A ray path in a spatially varying medium. | 280 |
| 11.14 | Ducting propagation in the atmosphere. | 281 |
| 11.15 | The ionospheric F layer. | 282 |
| 11.16 | Ray paths in the ionosphere. | 283 |
| 11.17 | Ground wave propagation over a hill. | 286 |
| 11.18 | The scattering caused by a flat plate. | 288 |
| 11.19 | Total power scattered by a plate (normalised on the maximum power). | 289 |
| 11.20 | Propagation by scatter from a permittivity anomaly. | 290 |
| 11.21 | Scintillation caused by permittivity irregularity. | 291 |
| 12.1 | The frequency content of a real signal. | 294 |
| 12.2 | The sampling of an analogue signal. | 294 |
| 12.3 | Three signals with identical DFT due to aliasing. | 296 |
| 12.4 | Spectral contamination caused by aliasing. | 296 |
| 12.5 | A finite length discrete signal filtering system. | 298 |
| 12.6 | A simple one-bit analogue-to-digital converter. | 299 |
| 12.7 | A two-bit analogue-to-digital flash converter. | 299 |
| 12.8 | Digitisation of a general signal. | 300 |
| 12.9 | Sampled signals with quantisation noise. | 301 |
| 12.10 | Simple digital-to-analogue converter. | 302 |
| 12.11 | A direct conversion receiver with baseband analogue-to-digital conversion. | 302 |
| 12.12 | A direct digitising receiver. | 303 |
| 12.13 | A digital oscillator. | 304 |
| 12.14 | A direct digital synthesiser. | 305 |