

Cambridge University Press

0521815274 - Practical Interfacing in the Laboratory: Using a PC for Instrumentation, Data Analysis, and Control

Stephen E. Derenzo

Index

[More information](#)

Index

- A/D converter, 572, 601
- Absolute digital encoder, 231
- Absolute zero, 236
- Accident scenarios and prevention, 563, 564
- Accuracy
 - analog-to-digital converter, 163
 - control system, 423
 - digital-to-analog converter, 154
 - sensor, 227
- Acquisition time
 - (sample-and-hold), 177
- Actuator (definition), 226
- AD558 D/A converter
 - (use in Lab Exercise), 207
- AD582 sample-and-hold
 - (use in Lab Exercise), 214
- AD590 temperature transducer, 252
- AD625 instrumentation amplifier
 - (Lab Exercise), 144
 - (use in Lab Exercise), 306, 308, 313, 465
- AD670 A/D converter
 - (use in Lab Exercise), 214
- AD7820 A/D converter
 - (use in Lab Exercise), 214
- Adaptive quadrature integration code, 542
- Address
 - bus, 4
 - decoder, 4
- ADSL, 44
- Ag(AgCl) electrode, 272
 - (use in Lab Exercise), 329, 334, 349
- Aliasing, 396
- Aliasing in frequency, 404
- Alphas, 276
- AM9513 counter/timer, 16
 - (Lab Exercise), 65
 - sequence of operations (illus.), 17
- Amplifier circuits, 98
 - buffer, 80
 - Darlington,
- (use in Lab Exercise), 468, 488, 493
- differential, 79
- instrumentation, 89
- inverting, 76
 - (Lab Exercise), 130
- isolation, 93
- noise, 96
- noninverting, 78
 - (Lab Exercise), 132
- power, 117
- risetime, 88
- sample-and-hold, 178
- settling time, 88
- summing, 81
- Analog delay
 - (sample-and-hold), 176
- Analog filter, 116
 - (Lab Exercise), 152
 - anti-aliasing, 115, 404
 - band pass (definition), 99
 - bandwidth (definition), 99
 - Bessel, 111
 - Butterworth, 110
 - characteristics, 98
 - Chebyshev, 111
 - corner frequency, 98
 - high-order high-pass, 116
 - high-order low-pass, 110
 - high-pass (definition), 99
 - high-pass one-pole, 106
 - (Lab Exercise), 150
 - low-pass (definition), 99
 - low-pass one-pole, 105
 - (Lab Exercise), 148
 - low-pass two-pole
 - (Lab Exercise), 149
 - notch (definition), 99
 - notch, 107
 - (Lab Exercise), 150
 - passband (definition), 98

- Paynter, 111
 phase shift (definition), 98
 Sallen-Key, 111
 settling time (definition), 99
 transitional, 111
 Analog I/O
 Standard loop, 222
 Analog multiplexer, 186
 Analog output, 556, 557
 Analog position sensor, 229
 Analog-to-digital converter, 173
 (used in Lab Exercise), 203, 214
 dual-slope method, 167
 flash method, 170
 ideal response, 162
 integrating method, 167
 sigma-delta, 172
 subranging method, 171
 successive approximation method, 168
 tracking method, 165
 Anti-aliasing filter, 115, 396, 404, 574
 (Lab Exercise), 456, 466
 Butterworth design, 115
 Aperture delay
 (sample-and-hold), 176
 Aperture jitter
 (sample-and-hold), 176
 Aperture time
 (sample-and-hold), 176
 ASCII character codes
 (appendix), 569, 572
 ASCII code, 36
 Asynchronous, 35
 Atria (illus.), 335
 Average (sample mean), 364
 Average error of a control system, 423

 Band-pass filter (definition), 99
 Bandwidth
 (sample-and-hold), 174
 and risetime, 88
 Beer's law, 266
 Bessel filter, 111
 Beta of a thermistor, 247
 Betas, 276
 BI HOLD line (used in Lab Exercise), 66
 Bimetallic switch, 237
 Bimetallic temperature sensor, 238
 Binary numbers, 5
 (tables), 6, 8
 Binary-to-Gray code conversion, 7
 Binned data, 360
 Binomial distribution, 576
 Blood pressure (Lab Exercise), 339
 Bode plot, 88
 Brush position encoder, 231

 Buffer amplifier, 80
 (illus.), 80
 Bus
 address, 4
 data, 5
 input, 28
 (illus.), 28
 output, 11, 21, 24
 (illus.), 24
 Butterworth filter, 110
 Byte I/O, 21

 C programming hints
 (appendix), 510
 Calorie, 236
 Capacitor value codes, 566
 Cardiac cycle (table), 337
 Cardiac depolarization sequence, 335
 CD-ROM (compact disk-read only memory), 3
 CD-WORM (compact disk-write once read
 many), 4
 Celsius temperature scale, 235
 Charge transfer error
 (sample-and-hold), 177
 Chebyshev filter, 111
 Chi-squared, 379
 (table), 377, 378
 probability of exceeding, 379
 Chip (integrated circuit), 1
 Circulatory system (human)
 (illus.), 335
 Closed loop gain, 77
 CMRR (common mode rejection ratio), 90
 Common-mode
 rejection (equation), 90
 Common-mode gain (equation), 90
 Comparator, 164
 Compiler, 4
 Complex impedance of electrodes
 (Lab Exercise), 330
 Contact bounce, 33
 Control
 algorithm, 422
 analog, 420
 Fourier, 419
 ON-OFF, 424
 (Lab Exercise), 486, 492, 499
 PID, 426
 proportional, 426
 temperature, 427
 variable, 422
 Control delay
 (sample-and-hold), 176
 Control register, 19
 Conversion time (analog-to-digital converter),
 163

- Corner frequency, 88, 98
 Counter/timer, 18
 AM9513, 16
 (Lab Exercise), 58, 59
 applications, 14
 cascading (warning), 16
 Intel 8253, 15
 Crossover distortion, 118
 Current-to-voltage converter, 81
 Curve fitting, 374
 Curve shaper amplifier circuit, 84
 D-type flip-flop, 11, 21
 function table, 10
 microcomputer output (illus.), 10, 21
 D/A converter, 579
 Damped-harmonic oscillator, 300
 Data
 bus, 5
 register, 18
 Data-acquisition and control
 components, 1
 Data-acquisition circuit
 (Lab Exercise), 214
 Data-acquisition procedures
 digital, 33
 embedded processor, 33
 hardware-trigger DMA, 32
 hardware-trigger hardware-interrupt, 31
 hardware-trigger status-poll, 30
 software-trigger status-poll, 29
 Dead band
 control system, 425
 Debouncing, 34
 Deglitcher (for digital-to-analog converter), 155
 Degrees of freedom, 368, 369, 376
 Depolarization sequence of heart, 335
 Design factors
 sampling system, 414
 Dial thermometer (use in Lab Exercise), 305
 Diastolic blood pressure (Lab Exercise), 340
 Differential amplifier, 79
 Differential gain (equation), 90
 Differential linearity
 (Lab Exercise), 204
 Differential linearity error
 analog-to-digital converter, 163
 Differential linearity error
 digital-to-analog converter, 155
 Differentiating filter, 103
 Digital building blocks, 13
 Digital encoder, 230
 Digital filter
 (Lab Exercise), 471, 477
 finite impulse response (FIR), 416
 infinite impulse response (IIR), 417, 418
 low pass, 473
 Digital interfaces,
 (table), 45
 Digital-to-analog converter, 161
 (Lab Exercise), 203, 207, 449, 450
 characteristics, 154
 ideal response, 153
 multiplying, 154
 R-2R method, 158
 subranging method, 160
 weighted adder, 157
 Diphthong, 462
 Discrete Fourier transform, 401
 derivation, 400
 Disk memory, 3
 Dissipation constant
 (thermistor), 248
 DPSK (differential phase-shift keying modem), 36
 Droop
 (sample-and-hold), 175
 DT3010, 556, 557
 binary input, 553, 556
 pin assignments (table), 554, 555
 Dual-slope analog-to-digital converter, 167
 Duplex
 full, 35
 half, 40
 Duty factor, 424
 Dynode, 267
 ECL logic voltage ranges (table), 9
 Editor, 4
 Einthoven triangle (illus.), 338
 Electrical hazards and prevention, 560
 Electrocardiogram
 (Lab Exercise), 338
 Electrode
 Ag(AgCl), 272
 bare metal, 272
 circuit model, 274
 impedance (Lab Exercise), 332
 Electromagnetic isolation amplifier, 93
 Electromagnetic pickup
 (Lab Exercise), 140
 Electromagnetic spectrum, 274
 Electromyogram
 (Lab Exercise), 351
 processing circuit (illus.), 347
 Electronic ice point, 251
 Electronic transducer (definition), 226
 Electrooculogram
 (Lab Exercise), 352
 origin of signal, 352, 353
 End-point voltage
 A/D converter (Lab Exercise), 203
 D/A converter (Lab Exercise), 204

- Equilibrium temperature extrapolation equation
(Lab Exercise), 324
- Error
analog-to-digital converter, 162
control system, 423
digital-to-analog converter, 154
- Error signal, 486, 491
- Exclusive-OR gate, 12
- Expansion coefficients (table), 238
- Fahrenheit temperature scale, 236
- Fast Fourier transform, 409
(use in Lab Exercise), 454, 461
C code listing, 517
use of `fft.c` function, 455
windowing examples, 408
- Feedthrough
(sample-and-hold), 175
- Files (opening) (appendix), 515
- Filter
anti-aliasing, 396
anti-aliasing (Lab Exercise), 404, 456,
466
differentiating, 103
integrating, 103
- FireWire, 44
- Flash analog-to-digital converter, 170
- Flip-flop (edge-triggered), 11, 21
- Force transducer, 257, 583
(Lab Exercise), 311
(illus.), 312
- Formants of vowels
(table), 464
- Fourier control, 419
- Fourier convolution theorem, 391
- Fourier frequency convolution theorem, 394
- Fourier series expansion, 394
- Fourier transform of truncated time function, 398
- Fourier transforms, 412
- Framing error (UART), 36
- Frequency aliasing, 183, 396, 404
- Frequency response
high-pass filter, 103
low-pass filter, 101
- FSK (frequency shift keying modem), 36
- Full-duplex, 35
- Full-wave rectifier, 82
- Function table
D-type flip-flop, 10
one-shot, 13
transparent latch, 11
tri-state buffer, 10
- Gain
common-mode (equation), 90
differential (equation), 90
voltage, 77
- Gain error
analog-to-digital converter, 162
- Gain-bandwidth product
amplifier, 88
op amp, 87
- Gamma function code, 548
- Gamma rays, 275
- Gauge factor (strain gauge), 254
- Gaussian curve, 360
- Glitch (D/A converter)
(Lab Exercise), 209
- Glottis, 462
- GPIB bus, 42
- Gray code, 7, 20
(definition), 5
digital encoder (illus.), 232
(table), 8
- Gray-to-binary code conversion, 7
- Grounds (appendix), 504, 508
- Half-duplex, 40
- Handshaking
GPIB bus, 42
parallel input port, 26
(illus.), 27
parallel output port, 19
(illus.), 22
RS-232, 38
- Hann window, 399
- Harmonic oscillator (damped), 300
- Hazards (electrical), 560
- Heat pump
Peltier, 244
- Hexadecimal, 5
- High-pass filter
(definition), 99
one-pole, 106
- High-pass one-pole filter
(Lab Exercise), 150
- Human heart (Lab Exercise), 334
- Human reaction time
(Lab Exercise), 62
- Hysteresis
comparator, 164
control system, 425
sensor, 228
- IEEE-488 bus, 42
- Impulse response
high-pass filter, 102
low-pass filter, 101
- Incandescence, 268
- Including functions (appendix), 514
- Inertial navigation, 259
- Input bus
(illus.), 28
- Input impedance, 86

Cambridge University Press

0521815274 - Practical Interfacing in the Laboratory: Using a PC for Instrumentation, Data Analysis, and Control

Stephen E. Derenzo

Index

[More information](#)

606

Index

- Input offset voltage
 - op amp, 85
- Instrumentation amplifier, 93, 573, 587
 - (Lab Exercise), 144
- (use in Lab Exercise), 306, 308, 313, 465
 - common-mode rejection
 - (equation), 90
 - (Lab Exercise), 139
 - power-supply rejection
 - (Lab Exercise), 139
- Integrated-circuit chip, 1
- Integrating analog-to-digital converter, 167
 - Integrating filter, 103
- Intel 8253 counter/timer, 15
- Interference
 - electrical, 97
- Interrupt, 31
- Inverting amplifier, 76
 - (Lab Exercise), 130
- Ionic potential, 271
- ISDN, 44
- Isolation amplifier, 93
- Isolation transformer, 564
- Jitter
 - control system, 423
- Johnson noise (equation), 95
- Kelvin temperature scale, 235
- Korotkoff sounds
 - (Lab Exercise), 340
- Lag time
 - control system, 423
- Lambert–Beer law, 265
 - (Lab Exercise), 319
- Laser, 270
- Laser diode, 270
- Latch, 25
 - (illus.), 11, 12
 - function table, 11
- Latch (transparent), 11
- Least significant bit (LSB), 154
- Least-squares fitting, 375
 - curve, 374
 - (Lab Exercise), 450
 - straight line, 372
- LED (light emitting diode), 270
- LED controlled-current circuit (illus.), 318
- LF356 op amp
 - bypass capacitors, 129
 - offset adjust, 129
 - pinout, 129
- Library functions (appendix), 515
- Light emitting diode (LED) (Lab Exercise), 270, 317
- Line driver circuit, 37
- Linearity error
 - (sample-and-hold), 174
 - analog-to-digital converter, 163
 - digital-to-analog converter, 155
 - sensor, 227
- Liquid crystal thermometer, 235
- Low-pass filter
 - (definition), 99
 - one-pole, 105
 - (Lab Exercise), 148, 344, 345, 348, 471, 478
- Low-pass, one-pole filter
 - phase shift, 106
 - two-pole
 - (Lab Exercise), 149
- Luminescence, 269
- Luminous efficiency of light sources, 270
- Magnitude of a complex number (equation), 105
- Metal electrode, 272
- Metal-foil strain gauge, 253
- Microcomputer
 - (definition), 2
 - components, 1
- Microprocessor, 2
- Minimization function code, 520, 529
- Missed codes (analog-to-digital converter), 163
- Modem (modulator–demodulator), 36
- Monte Carlo simulation, 383
- Motor
 - stepper, 233
- Nasal pharynx, 462
- Nasal sounds, 462
- Negative feedback
 - amplifier circuit, 76
 - and virtual short rule, 77
- Neutrons, 275
- Noise,
 - amplifier, 96
 - Johnson (equation), 95
 - sensor, 227
 - shot (equation), 95
 - white and pink, 94
- Noninverting amplifier, 78
 - (Lab Exercise), 132
- Notch filter, 107
 - (definition), 99
 - (Lab Exercise), 150
- Null hypothesis, 368
- Null modem, 39
- Number of degrees of freedom, 368, 369, 376
- Numerical integration, 542
- Numerical methods (appendix), 517
- Numerical minimization, 381
- Numerical representation (Lab Exercise), 55

Cambridge University Press

0521815274 - Practical Interfacing in the Laboratory: Using a PC for Instrumentation, Data Analysis, and Control

Stephen E. Derenzo

Index

[More information](#)

607

Index

- Offset voltage, 91
 - instrumentation amplifier
 - (Lab Exercise), 138
 - function table, 13
 - op amp, 85
- ON-OFF control, 424
 - (Lab Exercise), 486, 492, 499
- One-shot, 12
- Op amp, 76, 86
 - dynamic response, 86
 - gain-bandwidth product, 87
 - ideal (definition), 76
 - measuring bias currents, 86
 - offset voltage, 85
 - open-loop gain, 76
 - realistic (definition), 76
 - slewing rate, 86
 - temperature variations, 85
 - unequal external resistance paths, 85
 - unity-gain frequency, 87
- Open-loop gain, 76
- Open-loop response, 422
 - (Lab Exercise), 488, 494, 501
- Opening files (appendix), 515
- Optical isolation amplifier, 94
- Optical position encoder, 231
- OR gate (exclusive and inclusive), 12
- Oral pharynx, 462
- Output impedance, 76
- Output offset voltage, 91
 - (sample-and-hold), 174
 - op amp, 85
- Overrun error (UART), 36
- P-wave, 337, 591
- Parallel input port, 553, 556
 - (illus.), 26
- Parallel input/output port, 18
 - (use in Lab Exercise), 67
- Parallel output port
 - (illus.), 22
- Parity error (UART), 36
- Parseval's theorem, 391
- Paynter filter, 111
- Peak detector circuit, 84
- Peltier
 - effect, 591
 - emf, 239
 - heat pump
 - (Lab Exercise), 322
 - thermoelectric device, 244
- Pendulum (use in Lab Exercise), 300
- Pharynx
 - nasal, 462
 - oral, 462
- Phase shift
 - low-pass, one-pole filter, 106
- Phase shift measurement
 - (Lab Exercise), 148
- Phonocardiogram (Lab Exercise), 339
- Photocathode, 267
- Photoconductive mode, 263
- Photodiode, 261
 - biasing circuit, 318
 - I–V* curve, 264
 - (Lab Exercise), 318
 - (Lab Exercise), 316
- Photomultiplier tube, 267
- Photovoltaic mode, 262
- Physiological effects of various currents, 561
- PID control, 426
- Piezoelectric transducer, 257
- Pink noise, 95
- Platinum resistance thermometer, 236
 - (use in Lab Exercise), 305
- Poisson statistics, 593
- Poisson's ratio, 254
- Polling, 29
- Port
 - serial I/O, 19
- Position encoder, 230
- Position sensors, 233
- Positive feedback
 - (in comparators), 164
- Potentiometer, 228
- Potentiometer as angle sensor
 - (Lab Exercise), 300
- Power amplifier, 117
- Power-supply sensitivity
 - analog-to-digital converter, 163
 - digital-to-analog converter, 155
- Pre-amplifier, 97
- Precision, 593
 - sensor, 227
- Pressure
 - transducer, 257
- Printf function
 - (appendix), 513
 - (use of), 55
- Proportional control, 426
 - (Lab Exercise), 486, 492, 499
- QRS-complex, 337, 594
- Quadratic approximation, 549
- Quantizing error
 - analog-to-digital converter, 162
 - digital-to-analog converter, 155
- R–2R resistor ladder (in digital-to-analog converter), 159
- Radiation
 - applications, 274
- Radioactive isotopes, 276
- Rankine temperature scale, 236

Cambridge University Press

0521815274 - Practical Interfacing in the Laboratory: Using a PC for Instrumentation, Data Analysis, and Control

Stephen E. Derenzo

Index

[More information](#)

608

Index

- Random access memory (RAM), 2
 Rectifier circuit
 (use in Lab Exercise), 349
 full-wave, 82
 Register
 control, 19
 data, 18
 input port, 20
 status, 19
 Relative-accuracy error
 analog-to-digital converter, 163
 digital-to-analog converter, 154
 Residual, 364, 372
 Resistive position sensor, 229
 Resistor color codes, 566
 Resolution
 analog-to-digital converter, 162
 digital-to-analog converter, 155
 Response curve
 sensor, 227
 Response function
 sensor, 227
 Response time, 422
 Electromyogram signal, 350
 Electrooculogram signal, 354
 sensor, 228
 Risetime
 amplifier, 88
 and bandwidth, 88
 control system, 423
 rms linearity error
 digital-to-analog converter, 156
 rms noise
 amplifier, 96
 RS-232 interface, 39
 bit sequence (illus.), 38
 connections (illus.), 39
 RS-422 and 423 interfaces, 39
 RS-485 bus, 40
 Saccadic eye motion (Lab Exercise), 355
 Sallen-Key filter, 111
 Sample mean, 364
 Sample-and-hold (S/H) amplifier, 595
 Sample-to-hold offset
 (sample-and-hold), 177
 Sampling
 analog waveforms, 180
 hardware controlled, 181
 oscilloscope, 396
 software controlled, 180
 system design factors, 414
 theorem, 404
 Sampling-speed limitations
 due to analog-to-digital converter, 178, 180
 due to Nyquist aliasing, 179, 185
 Scanf function (use of), 55
 Schmitt trigger, 165
 SCSI interface, 43
 Seebeck
 effect, 596
 emf, 240
 Self-heating of thermistor (Lab Exercise), 308
 Sense signal, 486, 491
 Sense variable, 422
 Sensitivity, 596
 sensor, 227
 Sensor, 596
 characteristics, 227
 (definition), 226
 Serial
 (definition), 35
 I/O port, 19
 Set point, 422, 486, 491
 Settling time
 (sample-and-hold), 174
 amplifier, 88
 control system, 423
 digital-to-analog converter, 156
 Shielding and grounds (appendix), 504, 508
 Shot noise (equation), 95
 Sign extension, 7
 Slewling rate
 (sample-and-hold), 175
 digital-to-analog converter, 156
 op amp, 86
 Soft palate, 462
 Spontaneous emission, 269
 Square wave response
 high- and low-pass filters, 103
 Stability
 control system, 423
 sensor, 227
 Standard analog I/O loop, 222
 Standard deviation, 364
 standard error of, 366
 Standard error of the mean, 365
 Standard error of the standard deviation, 366
 Status bit
 (used in Lab Exercise), 66
 Status polling, 29
 Status register, 19
 Step function response
 high-pass filter, 102
 low-pass filter, 100
 Step response
 control system, 422
 Stepper motor, 233
 Stimulated emission, 270
 Strain element (Lab Exercise), 311

- Stress (definition), 253
 Strobe line, 25
 Strobe pulse
 (used in Lab Exercise), 66
 Student's t ,
 definition), 367
 (Lab Exercise), 59
 code for computing probability of exceeding,
 546
 probability of exceeding, 370
 (table), (see Table 5.2b for $n_f > 15$), 370
 (table), (see Table 5.2a for $n_f < 20$), 370
 unpaired data, 366
 Subranging converter
 digital-to-analog, 160
 flash analog-to-digital, 171
 Successive approximation analog-to-digital converter, 168
 Summing amplifier, 81
 Switch
 bimetallic, 237
 debouncing, 34
 Switching transient time
 (sample-and-hold), 177
 Systolic blood pressure (Lab Exercise), 340
 T-wave, 338
 Temperature control, 427
 digital-to-analog converter, 156, 163
 (Lab Exercise), 489, 496, 503
 sensor, 234
 stability
 standards, 235
 Terminal
 video display, 35
 Thermistor, 250
 (Lab Exercise), 307
 resistance vs temperature
 (table), 247, 252
 Thermal dynamics, 249
 equilibrium, 599
 Thermistor, 599
 Thermistor bridge
 (equation), 248
 (illus.), 306
 optimization, 249
 self-heating
 (Lab Exercise), 308
 Thermocouple, 244, 599
 (Lab Exercise), 307
 polynomial coefficients, 241
 temperature vs potential
 (table), 241
 Thermoelectric heat pump
 (Lab Exercise), 322
 efficiency (Lab Exercise), 326
 Thermometer
 bimetallic, 237
 liquid crystal, 235
 liquid-filled, 234
 platinum resistance, 236
 solid state, 250–252
 theristor, 246
 thermocouple, 240
 Thompson emf, 238
 Time constant
 theristor, 248
 Time measurements, 277
 Time to first peak
 control system, 423
 Tracking analog-to-digital converter, 165
 Transducer, 226
 Transfer function
 sensor, 227
 Transition voltage
 analog-to-digital converter, 162
 (Lab Exercise), 203, 217
 Transitional filter, 111
 Transparent mode
 latch, 25
 function table, 11
 (illus.), 11, 12
 parallel input port, 28
 parallel output, 22
 Tri-state buffer
 function table, 10
 Tri-state buffer (definition), 9
 TTL logic voltage ranges (table), 9
 Two's complement, 5
 Type I and II errors, 368
 UART (universal asynchronous receiver/transmitter), 36
 Unity-gain
 amplifier, 80
 frequency, 87
 Sallen-Key filter, 111
 USB interface, 43
 Vacuum pumps, 260
 Vacuum sensors, 259
 Variance, 364
 Ventricles (illus.), 335
 Video display terminal, 35
 Virtual ground, 77
 Virtual short rule, 77
 VME-BUS, 42
 Vocal tract (illus.), 462
 Voiced sounds, 462
 Voltage follower, 80
 Voltage gain, 77
 Vowel, 462

Cambridge University Press

0521815274 - Practical Interfacing in the Laboratory: Using a PC for Instrumentation, Data Analysis, and Control

Stephen E. Derenzo

Index

[More information](#)

610

Index

- | | |
|---|-------------------------------------|
| Waveform generation
(Lab Exercise), 210 | WORM (write once read many) disk, 4 |
| Waveform recovery
(after A/D and D/A conversion),
164 | X-rays, 275 |
| (Lab Exercise), 467 | Young's modulus, 253 |
| Waveform sampling, 180 | Zero-offset error |
| Wheatstone bridge, 601 | analog-to-digital converter, 162 |
| White noise, 94 | digital-to-analog converter, 155 |