

Index

- adder
 - carry-lookahead, 131–133
 - full, 110, 129
 - half, 147
 - modulo- p , 524
 - ripple-carry, 130
 - serial-binary, 266–268
 - ternary, 148
- admissible pattern, 189
- algebraic divisor, 156, 234
 - double-cube, 234
 - multiple-cube, 234
 - single-cube, 234
- algebraic factorization, 234–236, 247–250
 - targeted, 248
- algebraic resubstitution, 234
- aliasing, 463
- alphabet
 - code, 504–506
 - input, 270, 313, 414, 432, 441
 - output, 271, 432
 - source, 504–506
- AND gate, 57
- AND operation, 38
- Arden's rule, 601
- asynchronous circuits, 109
 - sequential, 338–371
- at-speed test, 232, 461
- autonomous clock, 386
 - maximal, 387
- backtrack, 199, 215, 219, 230
- base, 3
- base function, 163
- binary arithmetic, 8–10
- binary-coded decimal (BCD) code, 10
- binary codes, 10–19
- binate function, 193, 246
- binate input, 247
- Boolean algebra, 58–60
- Boolean functions, 110
- branching, 92, 93
- bridging fault, 210
 - fault collapsing, 220
 - feedback, 211
 - gate-level, 224
 - I_{DDQ} testing, 210, 220–224
 - nonfeedback, 211
 - optimistic condition, 221
- built-in self-test (BIST), 461–464
 - aliasing, 463
 - degree of polynomial, 461
 - linear feedback shift register, 461
 - primitive polynomial, 462
 - reseeding, 463
 - response analyzer, 463
 - signature, 461
 - test pattern generator, 461
- burst
 - input, 359
 - output, 359
- burst-mode, 358–363
- canonical forms
 - product of sums, 47
 - sum of products, 47
- Cartesian product, 26
- cell library, 162
- cell table, 297
- chain-connected blocks, 32

- checking experiment, 431, 442–448
- checkpoint, 216
- clock, 109
- closed covering, 324
- code converter, 74–77
- codes
 - BCD, 10
 - binary, 10–19
 - block, 505
 - cyclic, 12
 - decipherable, 504–510
 - error-detecting and correcting, 14–19
 - Excess-3, 11
 - Gray, 12, 13
 - Hamming, 16
 - instantaneous, 505
 - reflected, 13
 - ringtail, 144
 - self-complementing, 11
 - synchronizable, 508–510
 - 2-out-of-5, 14
 - variable-length, 505
 - weighted, 10, 11
- cofactor, 243
- co-kernel, 156–161
- combinational logic, 37
- common subexpression, 153–158
- comparators, 113–115
- compatibility graph, 325–327
- compatibility relation, 27
- compatible pair, 322–329, 494–496
- compatible states, 318
 - maximal, 319
- complement
 - 1's, 5
 - 9's, 5
- complementation, 38
- complex gate, 139
- composite graph, 583
- composite machine, 405
 - decomposition of, 404–413
 - general, 411
- concatenation, 504, 577
- conflict, 215–219
- conjunctive normal form, 47
- connection matrix, 482
- consistency, 214
- contracted table, 485
- control assignment, 238
- controlling value, 226
- conversion of bases, 5–8
- counters, 284–288
- cover, 29, 78, 390
- crossing function, 598
- cube, 70
 - D*-, 218–220
 - privileged, 344
 - required, 341
 - singular, 218
 - test, 219
 - transition, 341
- cube-free expression, 156
- cube–literal incidence matrix, 157
- current monitoring, 220
- cut set, 140
- cycle, 354–356
 - of computation, 293
- cycle set, 532
- cyclic codes, 12
- D*-algorithm, 217–220
 - backtrack, 219
 - D*-drive, 219
 - D*-frontier, 219
 - D*-intersection, 218
 - implication, 219
 - line justification, 219
 - primitive *D*-cube of a fault, 218
 - propagation *D*-cube, 218
 - singular cover, 218
 - singular cube, 218
 - test cube, 219
- data selectors, 115–117
- De Morgan's theorem, 42, 43
- decoders, 119–125
 - BCD, 119
 - decimal, 119
- decomposition
 - of switching functions, 153, 161, 165
 - parallel, 393, 409–411
 - serial, 390, 404–409
 - Shannon's, 48
 - with specified components, 411–413
- definitely diagnosable machines, 450–453
- definiteness, 483–488
 - tests for, 486–488
- delay element, 268, 276, 338
- delay fault, 211
 - path, 212
 - transition, 212

- delay fault test, 224–232
 - nonrobust, 226
 - robust, 227
 - validatable nonrobust, 227
- delay operator, 526
- demultiplexer, 120–122
- design for testability, 458–460
 - full scan, 458
 - normal mode, 458
 - partial scan, 458
 - test mode, 458
- deterministic machine, 307
- dimension of a machine, 525
- direct sum, 333
- disjunctive normal form, 47
- distance, 15
 - minimal, 15
- distinguishing sequence, 312, 439
- distinguishing table, 550
- division operation, 5–9, 156
 - divisor, 156
 - quotient, 156
 - remainder, 156
- divisor, 156
 - algebraic, 156, 234
 - Boolean, 156
- don't-cares, 74
 - observability, 242
 - satisfiability, 242
- double-cube divisor, 234
- double-cube extraction, 234
- dual-expression extraction, 234
- duality, principle of, 40
- equivalence classes, 26, 313
- equivalence partition, 314
- equivalence relation, 25–27
- equivalent faults, 216
- error, 14–19
 - detection and correction of, 14–19
 - propagation, 214
- ESPRESSO, 95–97
 - expanded, 95
 - irredundant, 95
 - reduce, 95
- Euclidean algorithm, 561, 562
- Excess-3 code, 11
- excitation function, 272–280
- excitation table, 272
- excitation variables, 338
- EXCLUSIVE-OR operation, 51
- experiments, 431–435
 - adaptive, 432
 - checking, 431, 442–448
 - distinguishing, 439, 440
 - homing, 435–437
 - multiple, 432
 - preset, 432
 - synchronizing, 437–439
- expressions (*see* switching expressions)
- extended *D*-algorithm, 455
- extraction, 153, 159–161
 - cube, 159
 - dual expression, 234
 - kernel, 159
- factor, 155
 - algebraic, 156
 - Boolean, 156
- factored form, 152
- false vertex, 183
 - maximal, 183
- fanin, 109
- fanout, 109
- fanout-free circuit, 217
- fault, 206
 - bridging, 210
 - coverage, 213
 - delay, 211
 - list, 216
 - redundant, 236, 240
 - stuck-at, 206
 - stuck-on, 210
 - stuck-open, 208
- fault collapsing, 216
 - dominance, 216
 - equivalence, 216
- fault model, 206–212
 - bridging, 210, 211
 - delay, 211, 212
 - functional, 453
 - single-state-transition (SST), 453
 - stuck-at, 206
 - stuck-on, 210
 - stuck-open, 208
 - structural, 206–208
 - switch-level, 208–211
- fields, 559–561
 - finite, 559
 - Galois, 560
- finite memory, 478–483
 - tests for, 479–481

- finite-state machine, 265
 - deterministic, 307
 - head, 293
 - incompletely specified, 317–330
 - Mealy, 307
 - Moore, 307
 - nondeterministic, 572–577
 - nonwriting, 293
 - writing, 293
 - tape, 293
- five-valued logic, 217
- flip-flop, 276–280
 - D*, 279
 - edge-triggered, 279
 - JK*, 277
 - master–slave, 276–279
 - set–reset, 277
- flow table, 346–350
 - primitive, 348
 - reduced, 350
- four-phase clocking, 194
 - evaluate, 194
 - hold, 194
 - reset, 194
 - wait, 194
- functionally complete operations, 52
- function, 27
 - base, 163
 - binate, 193
 - crossing, 598
 - excitation, 272–280
 - linearly separable, 184
 - majority, 64, 175
 - minority, 177
 - output, 74, 307
 - self-dual, 62
 - state transition, 307
 - symmetric, 171
 - threshold, 178
 - transfer, 526
 - transmission, 54
 - unate, 104, 183
- full scan, 458
- fundamental mode, 339
 - multiple-input change, 339
 - single-input change, 339
- gate, 53
 - AND, 57
 - majority, 175
 - minority, 177
 - NAND, 125–128
 - NOR, 125–128
 - NOT, 58
 - OR, 57
 - threshold, 177
- geometric representation, 182
- Gray code, 12, 13
- greatest lower bound, 30, 381
 - of closed partitions, 381
- Hamming code, 16
- Hasse diagram, 29
- hazards, 226
 - dynamic, 226
 - function, 339
 - logic, 339
 - static, 226
- homing sequence, 436
- Huntington postulates, 65
- IDDQ* testing, 210
- illegal intersection, 344
- implicant, 78
 - dynamic-hazard-free, 344
- implication, 78, 214
 - backward, 214
 - conflict, 215–219
 - forward, 214
- implication table, 229, 392, 408
- implied pair, 322, 449, 494
- impulse response, 528
- incompletely specified machines, 317–330
- information-flow inequality, 400
- information losslessness, 491–499
 - of finite order, 493
 - tests for, 494–497
- initialization sequence, 454
- initialization vector, 209
- input alphabet, 270
- input-consistent partition, 386
- input variable, 76
- integration, 113
- internal state, 176, 267
- inverse machine, 499–504
 - for a linear machine, 529–531
- inverter, 109
- irredundant circuit, 68
- isomorphic machines, 444
- isomorphic systems, 53

- iterative array model, 455
- iterative networks, 296–300
 - cell inputs, 297
 - cell outputs, 297
 - cell table, 298
 - input carries, 297
 - output carries, 297
- justification, 214, 456
 - line, 214
- Karnaugh map, 68
- kernel, 156–161
- kernel–cube incidence matrix, 160
- Kleene’s theorem, 593
- latch, 272–276
 - master, 277
 - slave, 277
- lattice, 30–33
 - of closed partitions, 380–383
 - complemented, 33
 - distributive, 32
 - Mm -, 402
 - π -, 381
- leaf-DAG, 165
- least significant digit, 4
- least upper bound, 30
- linear feedback shift registers (LFSRs), 461
 - feedback polynomial, 461
 - primitive polynomial, 462
 - seed, 462
- linear separability, 184
- linear sequential machines, 461, 523
 - autonomous, 532
 - chain realization of, 533
 - controllable, 568
 - identification of, 550–556
 - inert, 525–527
 - observability, 543
 - predictability, 543
 - reduction of, 541–550
 - response of, 528, 540, 541
- literal, 41
 - redundant, 41
- logic hazard, 339
- static-0, 245, 341
- static-1, 341
- logic polarity, 108
- logic transformations, 151–155
 - decomposition, 161
 - elimination, 154
 - extraction, 159–161
 - factoring, 155–159
 - hazard-nonincreasing, 345
 - substitution, 162
- logical path, 226
- machines
 - common predecessor, 410
 - composite, 405
 - concurrently operating, 404
 - definite, 483–488
 - definitely diagnosable, 450–453
 - finite-memory, 478–483
 - finite-state, 265
 - identification of, 440–442
 - information lossless, 491–499
 - inverse, 499–504
 - linear sequential, 461, 523
 - Mealy, 307
 - minimal, 319–322
 - Moore, 307
 - predecessor, 378
 - sequential, 307
 - successor, 378
 - Turing, 293
 - two-way, 595
- majority
 - function, 64, 175
 - gate, 175
- mandatory assignments, 238
- map, 68–78
 - cyclic, 93
 - of five variables, 77
 - of four variables, 69
 - Karnaugh, 68
- map-entered variables, 93–95
- marker, left-end, 595
- match, 163, 166
- matrices, 119, 482
 - characteristic, 541
 - characterizing, 544
 - connection, 482
 - cube–literal incidence, 157
 - diagnostic, 542
 - kernel–cube incidence, 160
- maxterm, 47

- Mealy machine, 307
 - transformation to Moore machine, 334
- memory span, 478
 - with respect to input–output sequences, 478–483
 - with respect to input sequences, 483–488
 - with respect to output sequences, 488–491
- merger graph, 322, 323
- merger table, 327–330
- minimal machine, 319–322
- minority
 - function, 177
 - gate, 177
- minterm, 46
- multiple-input signature register (MISR), 463
- Mm* pairs, 398
- modulo-2 addition, 524
- MOBILE, 175
- Moore machine, 307
- MOS transistors and gates, 132–143
- most significant digit, 4
- multiple faults, 233
- multi-output circuit, 76
- multiplexer, 115
- multiplier, modulo- p , 524
- n -cube, 182
- NAND gate, 125–128
- NAND–NAND implementation, 233, 384
- NAND operation, 116
- networks
 - bridge, 139
 - electronic gate, 57
 - iterative, 296–300
 - non-series–parallel, 139, 140
 - series–parallel, 136–139
- network covering, 163, 167–169
- nine-valued logic, 456–458
- noncontrolling value, 226
- nonfeedback bridging faults, 211
- nonrobust test, 226
- NOR gate, 125–128
- NOR operation, 52
- NOT gate, 58
- NOT operation, 38
- null sequence, 334, 528
 - maximal, 529
- number systems, 3–10
 - binary, 4
 - decimal, 3
 - hexadecimal, 8
 - octal, 8
- observability don't-care set, 242
- observation assignment, 238
- OFF-set, 248
- on-input, 226
- ON-set, 248
- operation
 - AND, 38
 - division, 5–9, 156
 - EXCLUSIVE-OR, 51
 - functionally complete, 52
 - NAND, 116
 - NOR, 38
 - NOT, 38
 - OR, 38
 - star, 583
 - unary, 28
- optimistic condition, 221
- OR gate, 57
- OR operation, 38
- ordered pair, 25
- ordering, 28–30
 - partial, 28
 - total, 29
- output alphabet, 271
- output-consistent partition, 384
- output dependency, reduction of, 383–385
- output function, 74, 307
- output predecessor, 497
- output (compatible) states, 494
- output successor, 489
- output variable, 270
- path-delay fault, 212
- palindromes, 304, 331
- parity
 - even, 14
 - odd, 17
- parity bit, 14
- parity check, 14
 - generator, 111
- partial scan, 458

- partition, 28
 - basic, 381
 - blocks of, 397
 - closed, 376
 - equivalence, 314
 - greatest, 32
 - input-consistent, 386
 - least, 32
 - output-consistent, 384
 - refinement of, 314
 - state-consistent, 416
 - uniform, 28
- partition pair, 397
- path sensitization, 213–215
 - one-dimensional, 215
 - two-dimensional, 215
- pattern generators, 461–463
 - feedback polynomial, 461
 - linear feedback shift registers, 461
 - seed, 462
- pattern graph, 163
- perfect induction, 39
- physical path, 226
- polynomial, 3–6, 155, 461
 - feedback, 462
 - primitive, 462
- position number, 16
- positive unate function, 181
- predecessor machine, 378
- predecessor table, output, 497
- present state, 267
 - vector of, 538
- prime implicant, 78
 - essential, 79
- prime implicant chart, 86–93
 - augmented, 99
 - branching method, 92, 93
 - construction of, 86
 - cyclic, 93
 - reduction of, 90–92
- prime implicant function, 88
- primitive gates, 216
- priority encoder, 117–119
- product of sums, 47
 - canonical, 47
- propagation *D*-cube, 218
- propositional calculus, 88
- quantum cellular automata, 175
- Quine–McCluskey method, 81
- race, 354–356
 - critical, 355
 - noncritical, 355
- radix, 3
- radix point, 4
- rated clock scheme, 225
- realizable pattern, 196
- recognizers
 - deterministic, 570, 571
 - finite-state, 570–607
 - nondeterministic, 572–574
 - two-way, 595
 - conversion to one-way, 598–601
- rectangle covering, 157, 158
- prime, 157
- redundancy identification and removal, 236–244
 - direct, 239–244
 - don't-care-based, 242–244
 - dynamic, 241, 242
 - indirect, 237–239
 - static, 239–241
- redundant literal, 41
- regular expressions, 577–582
 - definition of, 579, 580
 - derivative of, 607
 - equivalent, 580
 - extended, 593
- regular set, 580
- relation, 25–28
 - antisymmetric, 26
 - binary, 25
 - compatibility, 27
 - equivalence, 26
 - reflexive, 26
 - symmetric, 26
 - transitive, 26
- relatively essential vertex, 248
- re-seeding, 463
- resonant tunneling diodes (RTDs), 175
- response analyzer, 461
- response compression, 461
 - aliasing, 463
 - multiple-input signature register, 463
- ring, 559
 - commutative, 559
- ripple-carry adder, 130, 131
- robust test, 227

- stuck-at fault, 206
 - multiple, 207
 - single, 207
- satisfiability don't-care set, 242
- scan design, 458–460
 - normal mode, 458
 - scan-in, 458
 - scan-out, 459
 - test mode, 458
- secondary variable, 268
- self-dual function, 62
- sensitizable path, 213
- sensitizing input values, 229–231
 - nonrobust, 231
 - robust, 229
- sequence detector, 280–283
- sequential circuit, 265
 - asynchronous, 338–371
- sequential machine, 307
 - linear, 461, 523
- serial-to-parallel converter, 112
- series-parallel switching circuits, 52
 - elementary, 53
- sets
 - Cartesian product, 26
 - complement, 24
 - disjoint, 26
 - elements of, 23
 - empty, 23
 - equal, 24
 - intersection of, 24
 - null, 23
 - partially ordered, 28
 - totally ordered, 29
 - universe, 24
 - union of, 24
- seven-segment display, 123
- Shannon's expansion theorem, 48
- shift register, 278
 - feedback, 461
 - feedforward, 525–527
- side input, 214
- signature, 461
 - golden, 461
- sine generator, 124, 125
- single-cube divisor (*see* algebraic divisor)
- single-electron box (SEB), 175, 176
- single-state-transition (SST) fault, 453
- singular cover, 218
- slack, 231
- sneak path, 141
- stable state, 338
- standard form, 316
- states, 267
 - adjacent, 356
 - accepting, 571
 - compatible, 318
 - closed set of, 324
 - complete, 360
 - distinguishable, 312
 - equivalent, 312
 - final, 272
 - initial, 272
 - input, 338
 - rejecting, 595
 - secondary, 338
 - stable, 338
 - total, 338
 - unstable, 339
- state assignment,
 - in asynchronous circuits, 356–358
 - race-free, 361
 - using partitions, 375–380
 - valid, 356
- state diagram, 267
- state justification, 456
- state-pair differentiating sequence (SPDS), 454
- state splitting, 320
 - application to parallel decomposition, 393–395
- state table, 266–268
- state transition, 267
 - function, 307
- state variables, 268
 - reduction of functional dependency of, 377–380
- static hazard, 226
- status
 - uncontrollability, 239
 - unobservability, 239
- strongly connected machine, 309
- structural testing, 206
- stuck-on fault, 210
- stuck-open fault, 208
- subject graph, 163
- subset, 24
 - proper, 24
 - self-dependent, 375
- subset construction procedure, 576

- subtractor, 147
 - half, 147
 - full, 147
- successor, 309
- successor machine, 378
- successor table, 489
 - output, 489
- sum of products, 46
 - canonical, 47
- switching algebra, 37–44
- switching expressions, 40
 - algebraic, 155
 - Boolean, 155
 - cube-free, 156
 - irredundant, 68
 - simplification of, 40
- switching functions, 44
 - canonical forms of, 46–49
 - decomposition of, 153
 - minimization of, 67–107
 - number of, 50
 - of two variables, 50, 51
- symmetric functions, 171
- synchronizing sequence, 437
- synchronous circuits, 266, 274
- synthesis for testability, 232–250

- table of combinations, 39
- tabulation procedure, 81–86
- tape, 293
- tautology, 183
- technology mapping, 162
- test
 - application time, 213
 - delay, 212
 - generation time, 213
 - I_{DDQ} , 210
 - nonrobust, 226
 - robust, 227
 - set, 213
 - transition, 212
 - two-pattern, 209
- test modes, 458
- test pattern, 461
- test vector, 209
- testing graph and testing table
 - for definiteness, 486–488
 - for diagnosability, 448–451
 - for finite memory, 479–483
 - for information losslessness, 494–497
- for output memory, 488–490
- for synchronizability, 508–510
- for unique decipherability, 505–508
- theorem
 - absorption, 40
 - combining, 79
 - consensus, 41
 - De Morgan's, 42, 43
 - dual, 32, 40
 - involution, 42
 - Kleene's, 593
 - Shannon's expansion, 48
- three-pattern test, 232
- threshold element, 173
- threshold function, 178
 - identification of, 186–189
- threshold network, 181
- tie set, 139
- transducer, 570
- transfer function, 526
- transfer sequence, 332
- transition, λ , 573
- transition diagram, 357
- transition faults, 212
 - slow-to-fall, 212
 - slow-to-rise, 212
- transition graph, 572
 - conversion to deterministic form, 574–577
- transition table, 269
- transmission function, 54
- tree
 - distinguishing, 439, 440
 - homing, 436, 437
 - successor, 433
 - synchronizing, 438
- tree matching, 166
- true vertex, 183
 - minimal, 183
- truth table, 39
- truth values, 38
- tunneling phase logic (TPL), 177
- Turing machine, 293
- two-level realization, 76
- two-pattern test, 209
 - initialization vector, 209
 - test vector, 209

- unate function, 181, 182
- uncertainty, 433

- uncertainty vector, 434
 - homogeneous, 434
 - initial, 433
 - nonhomogeneous, 436
 - trivial, 434
- uncontrollability analysis, 239
 - 0-uncontrollable, 239
 - 1-uncontrollable, 239
 - status, 239
- unobservability status, 239
- unstable state, 339
- untestable fault, 215
- validatable nonrobust test, 227
- variable clock scheme, 224, 225
- Venn diagram, 24
- weight, 10
- weight-threshold vector, 180
- wired-AND, 110
- wired-OR, 110
- writing machine, 293
- X-successor, 309