

Index

- Accumulator
 - Arithmetic 111
 - Modulo 53, 64–5, 273
 - Multiplexed 237, 252, 272
 - Partitioning 280–3
 - Segmentation – *see accumulator partitioning*
- Active filter 323, 326–9, 339
- Analogue-to-digital convertor (ADC) 6, 222
- Adder
 - Carry look-ahead 274–5
 - Carry propagation 274
 - Pipelined 275
- Arbitrary function generator (AFG) 18–19
- Aliasing
 - Amplitude envelope 112–14
 - Definition 73
 - Harmonic 170–2
 - Image frequencies 51, 54, 65
 - Mitigation 82, 86
- Amplitude
 - Accumulation 261
 - Control 76, 79
 - Definition 9
 - Modulation 133, 241, 243
 - Peak 9
 - Peak-to-peak 10
 - Quantisation 6, 55
 - RMS 10–11
 - Spectrum 28, 75, 77, 89, 122, 129, 135, 144
 - Stabilisation 335
- Analogue oscillators
 - Amplitude stabilisation 34–5
 - Charge-balancing 22, 38–9
 - Digital control 23, 34
 - Performance limitations 38–41
 - State variable 34
 - Switched integration 36
 - Voltage to frequency convertor (VFC), *see charge-balancing*
 - Wien bridge 32
- Analogue waveshaping 23–4, 32, 203–12
- Anti-alias filter
 - see reconstruction filter*
- Aperiodic signal 6–7
- Arbitrary waveform
 - Applications 41
 - Constraints 162
 - Regenerating DSO waveform 19, 62
 - Specification in the frequency domain 178
 - Specification in the time domain 172
- Automatic test equipment (ATE) 32, 42
- Auto-calibration 27
- Arbitrary waveform generator (AWG) 2, 7, 18
- Audio testing and measurement
 - Crosstalk 223, 241
 - Frequency response 223
 - Harmonic and intermodulation distortion 222, 229
 - Multi-tone 223–5
 - Single-tone 223
- Band-pass
 - Filter 19, 34, 214, 323
 - Signal 82, 251
 - Spectrum synthesis 43, 299, 302, 305
- Bandwidth
 - Harmonic 73, 86
 - Nyquist 51, 85
 - Reconstruction filter 134, 216, 323
 - Waveform synthesis 45, 50, 160
- Barkhausen stability criterion
 - Continuous-time form 20, 33
 - Discrete-time form 90
- Baseband signal 44
- Bill Hewlett 34
- Biquad-form
 - see direct-form*
- Block pipelining
 - see pipelining*
- Cardiac waveform 7, 10
- Carrier signal 43–4, 87, 215, 228, 241–3, 248
- Carry look-ahead
 - see adder*
- Chirp generation 246
- Clock generator 30, 213

- Computer music
 - Frequency and pitch 221–2
 - Harmonics and partials 220–1
 - Human perception considerations 221
 - Tuning 221–2
- Continuous-time 5, 14–15, 27, 49
- CORDIC 155
- Coupled-form
 - see recursive oscillators*
- Crest factor 10–11, 133, 135, 160, 224, 335
- Critical sampling 134, 160, 309
- Cut-off frequency 31, 34, 114, 217–19, 311, 322, 325, 328, 337, 339
- Digital to analogue convertor (DAC)
 - Capacitive 23
 - Current output 208, 332–3
 - Non-linearity 317
 - Output amplifier 321, 330
 - Output glitch 307, 310–11, 317
 - Reference voltage 23, 208, 307, 315, 330–1
 - Settling time 315
 - Voltage output 332
- DAC distortion mechanisms
 - Capacitance modulation 327
 - Differential non-linearity 317
 - Harmonic distortion 317, 319, 331, 334, 336
 - Integral non-linearity 317
 - Intermodulation distortion 321
 - Output amplifier 327–8, 336
 - Passive component effects 327–8
 - Power supply decoupling and grounding 40, 331
 - Reconstruction filter 327–8
- DC offset 307, 311–12, 335–6
- Direct digital frequency synthesis (DDFS) 2
- Direct digital synthesis (DDS) 2
- Deglitcher 307, 310, 332
- Discrete Fourier transform (DFT) 15
- Diagnostic testing 2, 19, 41
- Direct synthesis 24
- Direct-form
 - see recursive oscillators*
- Discontinuity
 - Amplitude 16, 81, 97–8
 - Phase 163
 - Recursive oscillator frequency change 96–7
- Discrete-time 5–6, 12, 50
- Distortion
 - Harmonic 34, 75, 82, 108, 126, 218, 222, 229, 238–9, 256, 317, 319, 331, 334, 336
 - Intermodulation 15, 39, 42
- Dither 127–8, 138–43, 159–60, 187, 191, 203, 213–14, 226, 318
- Dual port memory (DPM) 269–73, 301–2
- Drift 23, 32–3, 38–40, 45, 102, 211, 313–15, 334
- Digital signal processing (DSP) 5–6, 266, 273, 309
- Dynamic range
 - Amplitude control 10, 54, 75, 79
 - Defined 75
 - Frequency control 75, 77
 - Headroom 10, 134, 273
 - Noise floor 55
 - Phase offset control 78–9
 - Spurious-free – *see sFDR*
- Dynamic spectrum control 254–6
- Dynamic waveshape control 228
- ECG waveform 7
- Error mitigation
 - Frequency control 28, 32, 58
 - Noise shaping 127–8, 138
 - Phase dithering 127, 138
 - Phase offset control 78, 124
 - Phase truncation 122, 127, 138, 214, 223, 252
- Error
 - Aliasing 73, 77, 82
 - Amplitude 79
 - Amplitude quantisation 54
 - Control linearity 23, 38, 75, 82
 - DDS model 128
 - Phase noise 86
 - Phase truncation 28, 72, 83, 117
 - Spectrum 72, 85
 - Waveshape 83–6
- Fast Fourier transform (FFT) 119, 135
- Filter
 - Active 323, 325–9, 339
 - Anti-alias, *see reconstruction filter*
 - Class 323–4, 329, 337
 - Distortion mechanisms 327–8
 - Group delay 311, 322, 324–5
 - Order 323
 - Pass-band ripple 322, 324
 - Passive 323
 - Phase response 311, 322–3, 327
 - Reconstruction, *see reconstruction filter*
 - Roll-off slope 322–5
 - Sensitivity 325, 329, 339
 - Stop band 311, 322
 - Transition band 325
- Foldover
 - see aliasing*
- Fractional addressing 59, 64, 70
- Fractional phase component 83, 144, 295
- Fractional- N PLL 24, 26, 32, 45
- Frequency
 - Control range 99, 216
 - Control resolution 28, 32, 59
 - Definition 6
 - Modulation (FM) 31, 109, 111, 242, 274
 - Reference 24, 77
 - Frequency shift keying (FSK) 108, 244

- Frequency synthesiser 22, 24, 26, 32, 203, 205
 Fundamental frequency 13, 30, 50, 82, 119,
 163–4, 170, 172, 218, 237–9, 241, 249–50,
 260, 302, 319
- Gain error
see DAC
- Generic form
see recursive oscillators
- Gibbs phenomenon 170, 177–81
 Glitch, *see DAC output glitch*
- Harmonic
 Contiguous phase indexing 258
 Non-contiguous phase indexing 262
 Phase offset 260
- Hewlett–Packard 19, 31
 History of digital waveform generation 17
 Hybrid waveform synthesis 23
- Ideal arbitrary waveform DDS 184
 Ideal sinusoidal DDS 112
 Inverse discrete Fourier transform (IDFT) 4–5, 16,
 30, 60, 63, 82, 89, 239, 249–52
- Initial conditions
see recursive oscillators
- Initial phase 9, 12, 52, 116, 158, 243, 246
 Instantaneous frequency 6, 11, 87, 110, 213, 246,
 253
- Instantaneous phase 10–14
 Integer phase 71–2, 116, 128, 236, 295
 Integrator 22–3, 34, 207, 211
 Interleaved DAC 27
 Intermodulation distortion
see distortion
- Interpolation
see phase interpolation
- Jitter
 Filter 207, 217–18
 Phase noise 25, 28, 30, 86, 129, 205–6, 208,
 213–17, 323–4, 337
- Lagrange polynomial interpolation
see phase interpolation
- Lanczos sigma factor 177, 179, 181
 Linear wavetable combination 80, 228
 Linearity errors
see DAC non-linearity
- Lookup table
see wavetable
- Multiplying DAC (MDAC) 23, 211–12, 219, 308,
 334
 Metaparameter 74–5, 82, 239, 254–5
 Modified coupled-form
see recursive oscillators
- Modular arithmetic 12
 Modulo integer multiplication 263–4
- Numerically controlled oscillator (NCO) 2
 Negative frequency 111, 274
 Noise 6–7, 10, 20, 25, 28–9, 54, 60, 72, 75, 79, 83–4,
 86
 Non-harmonic signals 4, 7, 16, 82, 85, 138, 163, 215,
 218, 224, 226, 241, 251, 299, 304, 321, 337
 Nyquist bandwidth, *see Nyquist interval*
 Nyquist interval 51
- Oscillator
 Analogue 32, 34, 36, 38
 Recursive – *see recursive oscillators*
 Taxonomy 19
- Oversampling interpolating DAC 27, 308
 Oversampling ratio 134, 309
- Paged addressing 80, 228–30, 233
 Paged wavetable interpolation 80–1, 228, 233–6
 Paged wavetable interpolation memory 296
 Parallel processing 4, 30, 266–7
- Performance metrics
 Amplitude error sequence 54, 83
 Amplitude error spectrum 40, 85
 Phase noise 86
 Phase truncation noise 72, 83
 SFDR 28, 40, 85
 SNR 10, 43, 55, 83–4
 Waveshape error 83–5
- Period 6
 Periodic signal 7
 Permutation of error spurs 130, 135–6
- Phase
 Accumulator 25, 27–8, 65, 110, 128, 132, 205–6,
 213–14, 273, 281, 301
 Continuity 16, 61, 68–70, 103
 Discontinuity 96–7, 163
 Dithering, *see dithering*
 Interpolation 4, 59, 88, 109, 115, 122–4, 144–52,
 163, 166, 192, 195–203, 277–8, 283–96
 Noise, *see jitter*
 Offset 9, 50, 52, 65, 72, 74, 78–9, 93,
 124–7
 Quantisation, *see phase truncation*
 Truncation 4, 72, 83–6, 115–22
- Phase shift keying (PSK) 244–6
 Phase shift oscillator
see analogue oscillators
- Phase–amplitude mapping
 Arbitrary waveform 186–203
 Error mechanisms 73, 84, 117, 123, 153
 General 53, 59, 67–8
 Optimal form 112–14, 184–5
 Sine waveform 134–59
 Using the IDFT 249

- Phase domain processing
 - Definition 110, 127–8
 - High speed phase accumulators 280–3
 - Noise shaping 127
 - Computing the IDFT 249–50
- Piecewise-continuous waveshaping 233–6
- Pipelining
 - Block 268–73
 - Sample 268–9
 - Latency 30, 76, 78, 81, 257, 268–9, 281, 289, 301
 - Throughput enhancement 257, 268–9
- Phase-locked loop (PLL) 24
- PLL testing example 45–7
- Pole distribution
 - see recursive oscillators*
- Polynomial interpolation
 - see phase interpolation*
- Polyphase signals 126
- Positive frequency 111
- Processing overhead 88–9
- Pseudo-random sequence 42, 141–3, 187, 318

- Quadrant symmetry 134
- Quadrature phase 101, 125–6
- Quadrature up-conversion 44
- Quantisation, *see amplitude quantisation*
- Quasi-periodic signal 8

- R-2R DAC
 - see DAC*
- Reactive feedback oscillators
 - see analogue oscillators*
- Reconstruction filter 6, 27–8, 31, 40–1, 54, 307–8, 311, 322
- Recursive oscillators
 - Amplitude instability 100, 105, 107
 - Coupled-form 99–101
 - Direct-form 93–9
 - Frequency control 102, 105–7
 - General properties 91–3
 - Initial conditions 102–4
 - Modified coupled-form 101
 - Phase continuity 90, 100–4
 - Quantisation effects 101, 104–6
 - Waveguide-form 101–2
- Relaxation oscillator
 - see analogue oscillators*
- Rotation matrix
 - see recursive oscillators*

- Sample frequency 17, 25, 30, 51, 58–9, 61, 64–5, 67
- Sample pipelining
 - see pipelining*
- Sample rate
 - see sample frequency*
- Sawtooth wave 6–7, 13, 31, 36

- Settling time
 - see DAC settling time*
- Spurious-free dynamic range (SFDR) 28, 317–18, 321
- Signal
 - Definition 14–15
 - Emulation 41–3
 - Specification 14–17
- Sinc function 29, 51, 73, 114, 169, 226, 322
- Sine wavetable 61, 119, 152
- Signal-to-noise ratio (SNR) 10, 43, 46, 55, 83–4
- Spectrum synthesis, *see band-pass spectrum synthesis*
- Square and pulse waveforms 36, 181, 212, 214, 337–8
- State variable analogue oscillator
 - see analogue oscillators*
- State variables, *see recursive oscillators*
- Stop-band
 - see filter*
- Stop-band suppression
 - see filter*
- Symmetry
 - see quadrant symmetry*

- Tabulation
 - see wavetable*
- Taylor series 129, 286
- Time division multiplexing (TDM) 45, 257–8
- Transition region/band
 - see filter response*
- Triangle wave 31, 36, 205, 211–12
- Trigonometric identity phase–amplitude mapping
 - 109, 125, 148–52

- Unit delay 65, 91, 268
- Unit-circle 17, 94, 98–100, 105
- Unwrapped phase 12, 53, 69
- Up-conversion 41, 43–4

- Voltage-controlled oscillator (VCO)
 - see analogue oscillators*
- Vector memory
 - Architectures 277–80
 - Definition 266
 - Interpolated 285, 289–96
- Voltage to frequency converter (VFC)
 - see analogue oscillators*
- Voltage-controlled function generator
 - see analogue oscillators*

- Waveform function 12–14, 59–63
- Waveform specification
 - see arbitrary waveform*
- Waveguide-form
 - see recursive oscillators*
- Wavetable

-
- Addressing 88, 114–22
 - Amplitude quantisation 61
 - Concept 14, 49
 - Definition 55–6
 - Fill time 58–9, 277
 - Length 58–60
 - Phase–amplitude space 173
 - Wien-bridge oscillator
 - see analogue oscillators*
 - Window function 169, 177
 - Wrapped phase 12, 53, 68, 70
 - z -domain 100
 - z -transform 17, 93, 96