

# Index

---

## A

accuracy,  
 ADC voltage measurement, 86  
 CMS counter, 224  
 CMS timer, 235  
 CMS voltage measurer, 246  
 PIT counting, 136-137  
 active-low controls, 17  
 ADC (AD573), in PDC system  
     ADC module, the, 203-205  
     CMS, use in, 236-240  
     control through CDI, 174-177  
     FVM, use in, 280-282  
 ADC (AD573) integrated circuit  
     accuracy, 86  
     control and timing, 87-88  
     operation, 85-86  
     parallel ports interface, 88-90  
     pin assignments, 87  
     resolution, 86  
     software, 90-93  
     troubleshooting, 95-98  
     voltmeter application, 94  
 ADC module, for PDC  
     circuit, 204  
     components, 205-206  
     connector, 204  
     construction, 206-208  
     layout, 205  
     troubleshooting, 208-209  
 address bus  
     Apple II expansion slot, 63-68  
     IBM PC expansion slot, 53-57  
     microcomputer, 345  
 address generator, 103-104, 277-279  
 AD573, see ADC (AD573)  
 analog electronics, references, 311

analog-to-digital converter  
 see ADC (AD573)  
 see ADC module  
 see CMS module  
 see FVM module  
 AND, 5-7  
 Apple II expansion slot  
     addresses, 63-64  
     commercial ports for, 72  
     I/O port design for, 63-71  
     pin assignments, 65  
     read and write timing, 65-66  
 Apple II parallel I/O ports  
     addresses, 63-64  
     circuit, 70  
     connector and cables, 334-335  
     construction, 333-337  
     layout, 334  
     software, 75-81  
     testing, 73-75  
     troubleshooting, 337-343  
     wiring, 335-337  
 Apple II parallel I/O ports  
     commercial vendors for, 72  
 Applesoft BASIC, 73, 339-343  
 architecture, microcomputer, 344-349

## B

base clock, CMS, 212  
 BASIC, see QuickBASIC, Applesoft  
 bibliography, 311-312  
 bi-directional bus, see data bus  
 binary numbers, 27-30  
 breadboard systems, 10-11  
 buffers (74244, 74373), 44-46  
 bus, address, see address bus  
 bus, data, see data bus

**Index**

351

**C**

- card rack, for PDC modules, 208
- CDI module, for PDC
  - ADC control, 177-179
  - circuit, 182-183
  - components, 189-190
  - connector pin assignments, 190
  - construction, 191-196
  - layout, 190-191
  - memory control, 174-177
  - monitor (status) inputs, 181
  - parallel ports interface, 182-183
  - PIT control, 165-174
  - software, 185-189
  - start/stop, 179-181
  - troubleshooting, 196-200
- central processing unit, 344-345
- chip selects (CS<sub>i</sub>\*'s), CDI, 165-167
- circuit construction, see wiring
- CLEAR\* flip-flop, 16-19
- clock, digital
  - base, CMS module, 212
  - frequency division, 36
  - IC, 14
  - PIT generated, 132-135
- CMS module, for PDC
  - base clock, 212
  - CDI, interface to, 251
  - circuit, 251
  - components, 257
  - construction, 256-263
  - counts measurement, 213-228
  - integrated measurement, 250-256
  - layout, 258
  - overview, 211-212
  - time measurement, 228-235
  - troubleshooting, 262-267
  - voltage measurement, 235-250
- COMMON SHARED, 93
- comprehensive measurement system, see CMS
- connector, pin assignments, 317-318
  - ADC, 204
  - CDI, 190
  - expansion slots, 54, 65
  - parallel ports, 321, 335
- construction, see wiring circuits

- control lines, microcomputer, 345-346
- control/data interface, see CDI
- control-in from I/O ports, 52-53
- control-out
  - CO<sub>i</sub>\*'s from CDI, 165-167
  - I/O ports, to, 52-53
- control signal generation, 75-77
- counter
  - 74192-193 IC's, 32-34
  - address generator, used for, 103-104, 277-279
  - constructed from flip-flops, 30-32
  - PIT (8253) IC, 127-136
  - PIT scaler, 152-158
  - time measurement, used for, 36
- counter/timer, see PIT (8253)
- counts measurement, CMS module
  - capabilities, 224-225
  - circuit, 219
  - count interval, 213-214
  - frequency measurement, 222-224
  - minimum count interval, 224
  - software, 219-224
  - synchronization, 217
- counts measurement, via parallel ports, 135-137, 152-158
- CPU, microcomputer, 344-345

**D**

- data bus (d<sub>7</sub>...d<sub>0</sub>)
- Apple II expansion slot, 64-68
- bi-directional, setup, 46
- CDI, produced by, 165-167
- IBM PC expansion slot, 53-60
- microcomputer, 345
- parallel ports to ADC, 88-89
- parallel ports to memory, 105-106
- parallel ports to PIT, 142-143
- data-in from I/O ports, 52-53
- data input/output software, 80-81
- data-out to I/O ports, 52-53
- decimal numbers
  - conversions to, 28-29
- decoder
  - 74138 IC, 37-38
- decoding
  - count values, 34-36

352

Index

elementary circuits, 7  
 example problem, 37  
 glitches, 35  
 port numbers, IBM PC I/O, 56-57  
**DEFINT**, 74  
 demultiplexer, 74138 IC, 37-38  
 digital clock, see clock  
 digital recorder, via parallel ports  
     circuit and timing, 120-123  
     design, 117-118  
     software, 123-125  
     troubleshooting, 125-127  
 direct memory access, 346  
 disconnected inputs, of TTL IC's, 23

**E**

8253, see PIT (8253)  
 electrical properties, TTL, 22-27  
 encoding switch circuit, 39-41  
**EXCLUSIVE-OR**, 5-6, 9  
 expansion slots  
     Apple II computers, 63-66, 349  
     IBM PC computers, 53-56, 349  
     microcomputer, 2, 349

**F**

fanout, 12-13  
 fast voltage measurement, see FVM  
**573**, ADC IC, see ADC (AD573)  
 flip-flop, 16-22  
     clock/data operation, 19  
     counter, built from, 32  
     implementation with NOR, 17-18  
     memory built from, 19-20  
     set/clear operation, 16-18  
**7474**, 18-19  
     synchronization using, 21-22, 217  
     toggling, 20-21  
 frequency measurement, by CMS  
     counter, 225-228  
**FVM** module, for PDC  
     address generator, 277-279  
     capabilities, 294-295  
     CDI, interface to, 289  
     circuit, complete, 289  
     construction, 297-304  
     hardware storage, 280-283  
     initiation, 283-287

layout, 299  
 memory control, 277-279  
 read memory, 287-290  
 software, 290-297  
 termination, 287-289  
 troubleshooting, 304-308

**G**

game port, 1  
 gate delays, 26-27  
     decoding circuit, in, 36  
     flip-flop toggling, in, 21  
 glitches, 26  
**GPIOB**, 2

**H**

hardware voltage measurement, see FVM  
 hexadecimal numbers, 27-30  
     &H prefix for, in QuickBASIC, 74  
 Hi-Z outputs, 44-46

**I**

**IBM PC** expansion slot  
     input and output timing, 55  
     I/O port design, 53-63  
     port numbers, 56, 348-349  
**IBM PC** parallel I/O ports  
     commercial vendors for, 72  
**IBM PC** parallel I/O ports  
     circuit, 62  
     connectors and cables, 320-321  
     construction, 319-327  
     layout, 320  
     port numbers, 56  
     software, 75-81  
     testing, 73-75  
     troubleshooting, 326-332  
     wiring, 323-327  
**IBM PS/2** parallel I/O ports  
     commercial vendors for, 72  
**IF INKEY\$, 77**  
**INP**, 3, 53, 55, 75, 348  
 input/output  
     game port, via, 1  
     microcomputer, 347-349  
     parallel ports, via, 2-3, 52-53  
     serial, 1

**Index** 353

- integer numbers, DEFINT, 74
- integrated circuits, application
  - ADC (AD573), 85-88
  - ADC (AD0808), 85, 99
  - memory (6264), 100-103
  - microprocessor, 347-349
  - PIT (8253), 129-130
- integrated circuits, TTL
  - basic gates, 9
  - buffers, 44, 44-45
  - counter, 30-36
  - decoder, 37-38
  - digital clock, 14
  - disconnected inputs, 23
  - electrical properties, 22-27
  - fanout, 12-13
  - flip-flop, 18-19
  - gate delays, 26-27
  - glitches, 26
  - introduction to, 4
  - latch/buffer, 44-45
  - multiplexer, 41-43
  - noise, 26
  - pin assignments, 314-318
  - 7400 NAND, 9-10
  - 7402 NOR, 9-10
  - 7404 INVERTER, 9-10
  - 7408 AND, 9-10
  - 74138 decoder, 37-38
  - 74152 multiplexer, 41-43
  - 74192-193 counters, 32-34
  - 7421 four input AND, 9-10
  - 74244 buffer, 45
  - 7425 four input NOR, 9-10
  - 7432 OR, 9-10
  - 74373 latch/buffer, 44-45
  - 7474 flip-flop, 18-19
  - 7486 EXCL-OR, 9-10
- Intel, microprocessor I/O, 348-349
- interfaces
  - ADC to CMS, 251
  - ADC to FVM, 289
  - ADC (AD573) to parallel ports, 88-90
  - address generator to CDI, 289
  - address generator to parallel ports, 103-104
  - CDI to parallel ports, 182-183
  - CMS to CDI, 251
  - digital recorder to parallel ports, 120-121
  - FVM to CDI, 289
  - memory (6264) to parallel ports, 104-107
  - parallel ports to Apple II expansion slot, 66-71
  - parallel ports to IBM PC expansion slot, 56-62
  - PIT (8253) to parallel ports, 142-143
- interval timer, see PIT (8253)
- INVERTER, 5-6, 8
- L**
  - latch/buffer, 74373, 44-45
  - layout, parallel ports
    - Apple II, 334
    - IBM PC, 320
  - layout, PDC modules
    - ADC, 205
    - CDI, 191
    - CMS, 258
    - FVM, 299
  - LED's, 23-35
  - logic gates, basic, 4
    - AND, 5-7
    - EXCLUSIVE-OR, 5-6, 9
    - INVERTER, 5-6, 8
    - NAND, 5-6, 8
    - NOR, 5-6, 8
    - OR, 5-7
    - truth tables, 5
  - logic switches, 25
- M**
  - Macintosh I/O ports
    - commercial vendors for, 73
  - measurement circuits, 1
  - measurement, by PDC modules
    - count/rate vs. time, 213-224
    - frequency (by counting), 225-228
    - time between events, 228-235
    - voltage analyzer, 247-250
    - voltage and time, 250-256
    - voltage vs. time, 235-246
    - voltage vs. time, fast, 276-297

354

measurement, via parallel ports  
 counts by PIT, 135-136  
 counts/second, 152-158  
 digital recorder, 115-125  
 voltage, 85-94  
 memory, from flip-flops, 19-20  
 memory, microcomputer, 346-347  
 memory (6264), in PDC system  
     CDI control, 174-177  
     FVM, use in, 277-279  
 memory (6264) integrated circuit  
     address generator, 103-104  
     application, recorder, 115-127  
     pin assignments, 101  
     parallel ports interface, 104-107  
     read cycle, 102, 108-109  
     software, 107-115  
     troubleshooting, 112-115, 125-127  
     write cycle, 102-103, 107-109  
 microcomputer, architecture, 344-349  
 microprocessor, 344-345  
 mode control word, PIT, 139-140  
 modules, PDC, see PDC  
 monitor lines (M's), produced by  
     CDI module, 181  
 Motorola, microprocessor I/O, 347-348  
 multiplexer  
     serial communication, 42-43  
     74152 IC, 41-42

**N**

NAND, 5-6, 8  
 noise, in TTL circuits, 26  
 NOR, 5-6, 8  
 number systems, 27-30  
     conversions among, 28-30

**O**

one-shot, programmable, 130-132  
 OR, 5-7  
 oscillator, TTL clock, 14  
 OUT, 3, 53, 55, 74, 348

**P**

parallel data collector, see PDC

Index

parallel I/O ports  
 cables, 320-321, 334-335  
 circuit layout, 320, 334  
 commercial, 71-73  
 connector pin assignments, 321  
 construction, 319-332, 333-343  
 design, 53-63, 63-71  
 specifications, 52-53  
 testing, 73-75  
 troubleshooting, 326-332, 337-343  
 parallel I/O ports, interfaces to  
     ADC, 88-90  
     address generator, 103-104  
     CDI module, 196-200  
     digital recorder, 120-121  
     memory, 104-107  
     PIT, 142-143  
     start/stop flip-flop, 81-83  
 PDC modules  
     ADC, 203-210  
     CDI, 162-202  
     CMS, 211-275  
     FVM, 276-310  
 PDC, overview  
     block drawings, 163, 164  
     card rack, 208  
     construction, see modules  
     pin assignments, 317-318  
     power supply, 208  
 PEEK, 3, 65, 73, 341, 347  
 PIT (8253), in PDC system  
     CDI generated controls, 165-167  
     CDI software, 167-174  
     CMS, use in, 212-215, 229-230,  
         236-239  
     FVM, use in, 280-283  
 PIT (8253) integrated circuit  
     clock generation, 132-135  
     control signal generation, 130-132  
     counting, 135-137  
     load sequence, 140-141  
     mode control word, 139-140  
     parallel ports interface, 142-143  
     pin assignments, 137-138, 317  
     program sequence, 138-140  
     read sequence, 141-142  
     scaler application, 152-158  
     software, 145-150  
     troubleshooting, 150-152, 158

**I**nDEX

355

- programs, see software
- programmable interval timer, see PIT
- P**OKE, 3, 66, 73, 341, 347
- polling software, 78-80
- power supply, for PDC, 208
- PRESET\* flip-flop, 18-19
- Q**uickBASIC
  - ! suffix, real variables, 75
  - &H prefix, hex variables, 74
  - COMMON SHARED, 93
  - DEFINT, 74
  - IF INKEY\$, 77
  - IN, 3, 53, 55, 75, 348
  - OUT, 3, 53, 55, 74, 348
  - PEEK, 3, 65, 73, 341, 347
  - POKE, 3, 66, 73, 341, 347
- R**AM, see memory
- random access memory, see memory
- read enables (RE\*)'s generated by CDI, 177-178
- real numbers, in QuickBASIC, 75
- recorder, digital, see digital recorder
- reference manuals, 312
- references, 311-312
- resolution, ADC, 86
- S**caler, PIT application, 152-158
- sensors, references, 311
- sequential logic, 13-16
- serial communication, 1
  - example circuit, 42-43
- SET\* flip-flop, 16-19
- 7400 NAND, 9-10
- 7402 NOR, 9-10
- 7404 INVERTER, 9-10
- 7408 AND, 9-10
- 74138 decoder, 37-38
  - Apple II port controller, 68-70
  - CDI, use in, 165-166, 174-175
  - IBM PC port controller, 60-63
  - switch encoding, used for, 39-41
- 74152 multiplexer, 41-43
  - serial communication, 42-43
- 74192-193 counters, 32-34
  - address generator, use in, 103-104, 277-279
  - clock frequency division, 36
  - switch encoding, for, 39-41
- 7421 four input AND, 9-10
- 7425 four input NOR, 9-10
- 74244 tri-state buffer, 45-46
  - CDI buffers, used for, 184
- 7432 NOR, 9-10
- 74373 tri-state latch/buffer, 44-45
  - bi-directional bus, used for, 46
  - digital recorder, in, 121
  - parallel ports, in, 57-58, 66-67
- 7474 flip-flop, 18-19
- 7486 EXCL-OR, 9-10
- 6264 RAM IC, see memory (6264)
- software, CDI module
  - SHELL.BAS, 165-189
- software, CMS module
  - CMS.BAS, shell, 219
  - counter, demonstration, 222-224
  - frequency measurement, 226-228
  - timer, demonstration, 233-234
  - troubleshooting, 264-267
  - voltage & time measurement, 254-256
  - voltage analyzer, 248-249
  - voltage demonstration, 244-245
- software, for devices interfaced with parallel ports
  - ADC, 92-94
  - digital recorder, 123-125
  - memory, 109-112
  - PIT, 143-157
  - voltmeter, 90-94
- software, FVM module
  - voltage vs. time, fast, 296-297
  - troubleshooting, 305-308
- software, via parallel ports
  - control signal generation, 75-77
  - data I/O, 80-81
  - polling, 78-80
- start/stop (S/S\*), CDI, 179-181
- switch, logic, 25
  - encoding circuit, 39-41
- synchronization, 20-21, 217, 240, 286

356

[Index](#)**T**

- temporary bus master, 346
- testing, see troubleshooting
- time measurement, by CMS module
  - circuit, 230
  - events, 229-239
  - minimal time between events, 235
  - reference clock, 230-231
  - software, 231-235
- timer, see PIT (8253)
- timing diagrams
  - ADC cycles, 88
  - Apple II expansion slot cycles, 65-66
  - binary counting, of, 31
  - counts measurement, by CMS, 214
  - decoder circuit, of typical, 36
  - definition of, 14
  - fast voltage measurement, 283
  - IBM PC expansion slot cycles, 55-56
  - memory read and write cycles, 102-103
  - PIT outputs, modes 1, 2 and 3, 131-132
  - PIT program, load and read cycles, 139-141
  - time measurement, by CMS, 229
  - voltage measurement, by CMS, 236
- toggling, 20-21
- transducers, references, 311
- tri-state outputs, 44-46
- troubleshooting (and testing)
  - ADC interfaced to parallel ports, 95-98
  - ADC module, 208-209
  - Apple II parallel ports, 337-343
  - basic logic circuits, 11-12
  - CDI module, 196-200
  - circuits wired to parallel ports, in general, 81-83
  - CMS module, 262-267
  - counting and decoding circuits, in general, 41
  - digital recorder, interfaced to parallel ports, 125-127
  - FVM module, 304-308

- IBM parallel ports, 326-332
- memory interfaced to parallel ports, 112-115
- PIT interfaced to parallel ports, 150-152
- scaler, PIT application, 158
- sequential circuits, 15-16
- truth tables, 5
  - basic gates, of, 6
- TTL integrated circuits
  - disconnected inputs, 23
  - electronic properties of, 22-23
  - gate delays, 26
  - glitches, 26
  - noise, 26
  - wiring LED's to, 23-24
  - wiring logic switches to, 25

**V**

- vendors for
  - breadboard systems, 313
  - components, general, 313
  - parallel ports, 72-73
  - PDC components, 313
- voltage measurement, by CMS module
  - capabilities, 247-250
  - programmable rate, at, 236-238
  - software, 241-246
  - synchronization, 239-241
  - trigger, upon external, 239
  - voltage analyzer, 247-250
- voltage measurement, fast, see FVM
- voltage measurement, via parallel ports, 85-94

**W**

- wire wrap
  - cards for PDC modules, 205
  - card rack for PDC modules, 208
  - expansion slot boards, 320, 333
- wiring circuits, on breadboards, 11
- wiring circuits, on expansion slot boards, 323-327, 335-337
- wiring circuits, on wire wrap cards
  - ADC module, 207-208
  - CDI module, 191-196
  - CMS module, 257-263
  - FVM module, 298-304