

Index

Adler, 607	gain, 123, 379, 422, 424
admissible	polynomial, 366, 406
bordering, 413	
decomposition, 217	
gains, 402	
Aitken, 28, 176	Campbell, 619
all-pass free, 203	formulas, 619
Anderson, 288	Carlin, 383, 607
antiresonance frequency, 532	Cauchy index, 13, 15
	Cauchy’s theorem, 379, 390, 512
	Cauchy–Binet, 2, 3, 160, 204, 205, 479
	Cauer, 107
	Cauer-1, 87, 426
Bézout theorem, 170	Cauer-2, 87
back-end impedance, 345	characteristic
Badcr, 107	denominator, 197
Barabaschi, 619	impedance, 518, 525
Belevitch	Chebychev gain, 361
description, 289–292	Chen, 383
polynomial representation, 435	coefficient of coupling, 104
Bennett, 428	Collin, 523
BIBO	Collins, 570
stability, 24, 28, 506–509	compatible impedances, 455
Bittanti, 288	complex normalization, 309, 393–395
Bliss, 524	Coppel, 107
Bode, 383	Cramer’s rule, 613
Boltzmann’s constant, 399	crossover radian frequency, 422
Bosma, 607	current source, 593
Bott, 75	
Bott–Duffin	D-doublet, 460
cycle, 72	Darboux, 9
synthesis, 58, 73	Darlington, 332
bounded-input, bounded-output, 24	2-port reciprocal, 409
bounded-real, 131, 433	doubly-minimal, 295
discrete, 241	equivalent, 293–353
lemma, 246, 255	equivalents, 296
broadband matching, 333, 368	pair, 293, 294, 303, 306, 369, 429
double, 352–367, 383	reactance 2-port reciprocal, 402
single, 337–352, 464	reciprocal, 296
Brockett, 176	Descartes’ Rule of Signs, 11, 12
Brune, 75	dielectric layers, 551
cycle, 42, 53, 54, 57, 319	diplexer
section, 53, 58, 319	design, 406
synthesis, 46–55, 226	high-pass, 423
Butterworth	low-pass, 423
design, 408	maximally flat, 425

- diplexer (cont.)
 - power complementary, 419
 - reactance-ladder, 421–422
 - realization, 408, 420
- displacement current, 482
- distortionless transmission, 418
- double-minimality, 203
- driving-point impedance, 61, 116
- Duffin, 75
- Duffin’s theorem, 72
- dynamical system, 16
- eigenvalues, 4–6
- elliptic gain, 361
- embedding 2n-port, 573
- equi-ripple property, 541
- essential
 - embedding, 218
 - singularity, 502, 515
- Euclid’s algorithm, 416
- excess noise temperature, 400
- exchangeable power, 400, 401
 - gain, 591
- Fano, 383
- Feldtkeller relationship, 297
- Fettweis, 570
- Fialkow, 143
- filter
 - antimetric, 297–309, 439
 - characteristic function, 297
 - insertion-loss, 108–116, 309
 - low-pass elliptic, 312
 - symmetric, 297–309, 439
 - TEM-line, 535–538, 547–552
- Foster, 40, 107
 - function, 46, 53, 72, 81, 82, 92, 307, 311, 370, 411, 448, 531
 - preamble, 48, 54, 64, 128
 - reactance theorem, 82, 83
- Fujisawa, 143
- Fujisawa’s theorem, 127–128
- gain bandwidth restrictions, 366
- Gantmacher, 28, 176, 480
- Gardner, 428
- Garloff, 480
- Garloff–Wagner Theorem, 466
- Garver, 638
- Gatti, 619
- Goursat, 524
- Guillemin, 288
- Gunning, 570
- gyrator, 172–175, 177–180
 - extraction, 265–278
 - ideal, 266, 402
 - polarities, 148, 584
- Hadamard product, 466, 469, 470, 474
- Hamiltonian, 21
- Haus, 607
- Helton, 383
- hermitian solution, 19
- Hines, 638
- Ho, 176
- holomorphic function, 235
- Horn, 607, 638
- Hurwitz, 419
 - test, 471
- hybrid description, 595
- incident energy, 147
- irreducible form, 197
- Jacobi’s
 - formula, 199
 - theorem, 2, 4, 292
- Jaumann
 - realization, 302
 - structure, 303
 - synthesis, 302
- Johnson, 607, 638
- joint diagonalization, 5
- Kailath, 28
- Kaplan, 607
- Kawakami, 638
- Kirchoff’s voltage law, 76
- Kreyszig, 42
- ladder
 - Cauer, 95
 - high-pass, 423
 - LC, 116, 370
 - low-pass, 127, 135, 423, 428
 - low-pass LC, 307
 - low-pass reactance, 125–142
 - reactance, 108, 116–125, 358, 364
 - realization, 421
 - standard, 140
 - transformerless, 367
- Lancaster, 107, 288
- Laplace transforms, 31, 32, 144, 497, 507, 608
- Laurent expansion, 36
- left-inverse, 181
- linear time-invariant, 592
- Linnenberg, 570
- Liu, 524
- lossless
 - passive 1-port, 79–81
 - reciprocal 2-port, 318
 - reciprocal 2n-port, 588, 627
 - transmission line, 507
- Lyapunov, 19, 22
- Lyapunov’s lemma, 19

- MacDuffee, 176, 606
- magnetic
 - coupling, 102–107
 - flux density, 483
- magnitude-complementary crossover network, 417
- Marden, 480
- Marston, 570
- matrix
 - adjugate, 205
 - admittance, 157, 431, 432, 452, 602, 610, 615
 - chain, 573
 - characteristic impedance, 490
 - coefficient, 188, 430, 489
 - compound, 2
 - controllability, 172
 - cross-ratio, 576–580
 - diagonal, 3, 495
 - elementary polynomial, 192, 219, 239, 415
 - Foster, 304, 314, 405
 - Foster admittance, 457
 - Foster impedance, 283
 - gyrator, 574
 - Hamiltonian, 261
 - hermitian, 5, 18, 147, 581
 - hermitian nonnegative-definite, 149
 - Hurwitz, 477, 478
 - hyperdominant, 488
 - immittance, 149, 385
 - impedance, 285, 336, 432, 450, 491
 - loop impedance, 619
 - lower triangular, 605
 - maximum-modulus, 150
 - minimum hermitian part, 150–153
 - minimum-phase polynomial, 561
 - nonsingular, 162, 167
 - normalized scattering, 266
 - observability, 172
 - orthogonal, 181, 253, 260
 - para-hermitian, 242
 - para-hermitian skew, 462
 - para-hermitian-positive, 180–194, 405
 - paraunitary, 181, 202, 211, 219–225, 269
 - paraunitary regular, 188
 - paraunitary symmetric, 414
 - Pauli spin, 575, 576
 - polynomial, 7, 181, 182, 557
 - polynomial Toeplitz, 556, 567
 - positive-definite, 184
 - rational, 7, 162, 192, 241, 405, 415
 - reactance-signature, 248
 - regular-paraunitary, 179, 186, 187, 203, 213, 223, 231, 233, 249, 278, 292, 414, 453
 - residue, 286, 305, 314, 450, 454, 459
 - scattering, 147, 154, 177, 224, 253, 307, 409, 432, 492, 552, 558, 562, 598, 620
 - signature, 248
 - skew-para-hermitian, 257
 - skew-symmetric, 243, 283, 583
 - square nonsingular, 572
 - square polynomial, 263
 - square-root, 493, 498
 - stability, 22
 - structure, 171
 - switching, 621
 - symmetric, 229
 - symmetric nonnegative-definite, 260
 - symmetric paraunitary, 354
 - symmetric positive-definite, 191
 - symmetric regular-paraunitary, 274
 - symmetric unitary, 631
 - tri-diagonal, 471
 - tuner impedance, 465
 - unit triangular, 604
 - unitary, 4, 588
- maximally flat, 422
- maximum passband attenuation, 550
- maximum-modulus, 59–66, 110, 267, 462, 553, 564, 566, 568
- McMillan degree, 159, 208
 - rational matrix, 159–172
 - regular-paraunitary rational matrix, 164
 - scattering matrix, 291
- Mean Value Theorem, 9
- MFDIPLX, 425
- microwave band, 481
- mid-series, 127
- mid-shunt, 127
- minimum
 - immittance, 61, 67, 68, 71
 - lag, 114
 - passband gain, 540
 - phase, 114, 115, 345, 373, 374
 - phase (Wiener–Hopf), 413
 - polynomial, 264
 - reactance, 65, 310, 350, 405, 435, 464
 - reactance p.r., 407
 - Real-Part Theorem, 43, 45
 - resistance, 53, 61, 65
 - stopband attenuation, 550
 - susceptance, 65, 128, 140
- Mirsky, 288, 524
- monotonicity, 64
- multiplexer
 - losses, 402
 - lossless reciprocal, 409
 - n-port, 409
 - phase, 408
- n-Port
 - passive synthesis, 177
 - synthesis, 194, 219
 - synthesis minimal passive reciprocal, 250
- Newcomb, 28, 288

- non-Foster, 303, 310, 313, 315, 320, 327, 331, 333, 429, 456, 462
- non-paraunitary, 339
- non-tight embeddings, 226–239
- nonnegative-definite, 4, 492
 - symmetric, 243
- normal rank, 180, 292
- normalization, 429
- Oono, 288
- Oono Yasuura algorithm, 181–185
- open-circuit transfer coefficient, 454
- optimal power gains, 538
- Ostrowski, 28
- Papoulis, 524
- parahermitian, 436
 - skew, 243
- parahermitian-positive function
 - rational, 534
- parametric representation, 204
- paraunitary
 - embedding, 218
 - regular, 158
- partial fraction, 39
- passive
 - 1-port, 33–37
 - 1-port synthesis, 43
 - 2-port, 291
 - devices, 620
 - multiplexers, 402
 - n-ports, 144
 - reciprocal 2-port, 454
- passivity, 29
- Pauli, 309
- permeability, 483
- permittivity, 483
- phasor, 108, 630
 - steady state, 156
- Pillai, 428, 480
- Piloty’s Theorem, 448
- Pippard, 107
- Plonsey, 523, 570
- polynomial
 - annihilating, 168
 - Butterworth, 343, 389
 - decomposition, 295
 - elementary, 197
 - Hurwitz, 183, 200, 201, 209, 221, 294, 388, 415, 529, 556
 - indicial, 331
 - parahermitian-positive, 209, 534
 - real, 411, 416, 419
 - Tchebycheff, 541–552
- port numbers, 177
- positive-definite, 4
- positive-real functions, 37–42
- power gain, 109, 113
- principal minors, 471
 - leading, 477
- principal square-root, 498
- Puckett, 619
- Puiseux expansions, 521
- quarter-wave frequency, 532
- rank of a matrix, 1
- rational
 - 2-variable function, 560
 - function, 45
 - non-paraunitary, 560
- RCLM network, 76
- RCLMG, 173
- reactance, 177–180
 - 2-port, 289–292
 - 2-port equalizer lumped reciprocal, 435
 - 2-port reciprocal, 455
 - extraction, 240–254
- real nonsingular matrix, 495
- reciprocity, 172–175
- reflected energy, 147
- reflection coefficient, 108, 155, 345
- Regalia, 428
- regular all-pass, 114, 203, 209, 212, 293, 295, 307, 343, 349, 414, 417, 419, 420, 463
- regular-paraunitary, 181, 219, 223, 245, 246, 250, 289, 356, 358, 414, 416, 432, 434, 435, 531, 553
 - symmetric, 457
- Representation Theorem, 373
- residue, 80
- resistance, 177–180
- resistance extraction, 194–219
- resistive impedance load, 536
- Rhodes, 570
- Riccati Equation, 16–22, 260
- Richard, 75, 570
- Richards, 332
 - formula, 65
 - section, 325
 - theorem, 70
- Riemann–Lebesgue Lemma, 505, 513
- right-inverse, 227
- Rolle’s Theorem, 8, 9, 12, 473, 479
- Rossi, 570
- Routh, 107
- Routh’s
 - test, 95, 96, 470
 - theorem, 86, 87, 471, 472
- Rudin, 570
- Sard, 401
- Scanlan, 401
- Schaug–Pettersson, 606

- Schoeffler, 480
- Schur
 - decomposition, 517
 - product, 469
- Schwarz inequality, 150
- Scott, 524
- self-gyrator coupling, 173
- Shekel, 619
- shunt capacitance, 308
- Siegel, 607
- single frequency tunable, 575
- singular value, 4
 - decomposition, 4
- skew-parahermitian, 159
- skew-symmetric, 174
- Smith–McMillan
 - canonic form, 197, 219, 220, 232, 276
 - decomposition, 220
 - form, 198, 221
- special-Foster, 315, 317–319
- special-Hurwitz, 30, 40, 131
- spectral radius, 242
- Spiegel, 524
- stability, 384, 392, 393
 - marginal, 30
 - short-circuit, 385
- stabilizable, 17
 - pair, 23
- stable, 19, 20
 - open-circuit, 385
 - short-circuit, 385
- standard
 - embedding, 202
 - equalizer, 364
- state-variable representation
 - minimal, 264
- steady-state, 392, 393
 - phasors, 497
- Stewart, 28
- Storer, 309
- Stratton, 523
- strictly-Hurwitz, 30, 121, 424, 466, 468
- strictly-positive, 467
- Sturm chain, 14
- Sturm’s theorem, 474
- surface impedance, 483, 484
- Sylvester’s
 - inequality, 172
 - law of inertia, 6
 - law of nullity, 2
 - theorem of inertia, 236
- synthesis 2-port, 448
- Takagi’s theorem, 588
- Tee equal capacitance, 465
- Telegrapher’s Equations, 486
- Tellegen, 176
- Tellegen’s Theorem, 76, 78, 79, 268
- TEM
 - 2-port ideal, 525
 - line transducer, 489–493
- theory of equations, 8
- Thevenin impedance, 334, 368, 397
- tight bordering, 195
- Titchmarsh, 607
- transducer power gain, 111, 115, 120, 156, 297, 333, 396, 432, 447, 534
- transformer
 - 2-port, 52
 - 2-winding, 102–107
 - broadband, 546, 547
 - ideal, 266, 366, 402
 - TEM-line, 535, 538
- transformerless
 - synthesis, 60
- transforms, 29
- transient performance, 497
- transmission
 - lines multiconductor, 481
 - lines TEM, 481
 - zeros, 125, 291, 310, 312, 337, 371, 502, 552
- transverse planes, 490
- Turnbull, 607
- type
 - B section, 326
 - C section, 317, 326
 - D section, 317, 326
 - E section, 317, 326
- uniform
 - boundedness, 453
 - dissipation factor, 101
- unitary, 518
- upper-triangular, 518
- voltage generator, 611
- Watanabe, 142, 143
- weighting pattern, 23
- Wiener–Hopf, 181, 186, 199
 - factor, 186
- Wiener-Hopf
 - factor, 557
- Winter, 480
- Wohlers, 480
- Yarman, 383
- Yasuura, 288
- Youla, 28, 143, 176, 288, 309, 332, 383, 401, 428, 480, 570, 607, 619, 638
- Zadeh, 619
- zero signatures, 233
- zero-state, 23
- Zobel, 86, 107