

Contents

	<i>Preface</i>	page xiii
	<i>Acknowledgments</i>	xv
1	Linear and Nonlinear Circuits	1
	1.1 Basic Definitions	1
	1.2 Linearity and the Separation of Effects	3
	1.3 Nonlinearity: The Lack of Superposition	8
	1.4 Properties of Nonlinear Systems	12
	1.5 Example of a Static Transfer Nonlinearity	26
	1.6 Example of a Dynamic Transfer Nonlinearity	36
	1.7 Summary	44
	1.8 Exercises	44
	References	45
2	Basic Nonlinear Microwave Circuit Analysis Techniques	47
	2.1 Mathematical Representation of Signals and Systems	48
	2.2 Time-Domain Circuit Analysis	54
	2.3 Frequency-Domain Circuit Analysis	66
	2.4 Envelope-Following Analysis Techniques	82
	2.5 Summary	89
	2.6 Exercises	90
	References	90
3	Linear Behavioral Models in the Frequency Domain: S-parameters	93
	3.1 Introduction	93
	3.2 S-parameters	93
	3.3 Wave Variables	94
	3.4 Geometrical Interpretation of S-parameters	97
	3.5 Nonlinear Dependence on Frequency	98
	3.6 S-parameter Measurement	98
	3.7 S-parameters as a Spectral Map	101
	3.8 Superposition	101
	3.9 Time Invariance of Components Described by S-parameters	102
	3.10 Cascadability	104
		ix

3.11	DC Operating Point: Nonlinear Dependence on Bias	106
3.12	S-parameters of a Nonlinear Device	106
3.13	Additional Benefits of S-parameters	109
3.14	Limitations of S-parameters	111
3.15	Summary	111
3.16	Exercises	112
	References	113
4	Nonlinear Frequency Domain Behavioral Models	115
4.1	Introduction and Overview	115
4.2	Signals and Spectral Maps on a Simple Harmonic Frequency Grid	117
4.3	Time-Invariant Large-Signal Spectral Maps	119
4.4	Large-Signal Behavioral Modeling Framework in Wave-Space	122
4.5	Cascading Nonlinear Behavioral Model Blocks	124
4.6	Spectral Linearization	125
4.7	Application: Optimum Load for Maximum Power Transfer	141
4.8	Small-Signal Limit of X-Parameters	143
4.9	Two Large Signals	144
4.10	Memory	159
4.11	Causes of Memory	167
4.12	Summary	176
4.13	Exercises	177
	References	178
5	Linear Device Modeling	181
5.1	Introduction: Linear Equivalent Circuit Models of Transistors	181
5.2	Linear Equivalent Circuit of a FET	182
5.3	Measurements for Linear Device Modeling	185
5.4	On-Wafer Measurements and Calibration	187
5.5	The Device	190
5.6	Intrinsic Linear Model	199
5.7	Bias-Dependence of Linear Models	212
5.8	Summary	215
5.9	Exercises	215
	References	216
6	Nonlinear Device Modeling	218
6.1	Introduction	218
6.2	Transistor Models: Types and Characteristics	219
6.3	Charge Modeling	239
6.4	Inadequacy of Quasi-Static Large-Signal Models	258
6.5	Symmetry	262
6.6	Self-Heating and Trapping: Additional Dynamical Phenomena	269

6.7	NVNA-Enabled Characterization and Nonlinear Device Modeling Flows	275
6.8	Summary	292
6.9	Exercises	293
	References	294
7	Nonlinear Microwave CAD Tools in a Power Amplifier Design Example	301
7.1	Nonlinear Device Modeling in RF/Microwave Circuit Design	301
7.2	Computer-Aided Power Amplifier Design Example	316
7.3	Summary	334
	References	335
	<i>Appendix</i>	337
	<i>Index</i>	340